

The material we have covered so far this semester is summarized (but NOT limited to) below:


- Understand the basic operation of a BJT:
 - Cutoff, saturation, active. Analyze a circuit for all current equations and voltages (current relationships)
 - Make sure to be able to take a Thevenin Equivalence and use Resistance Reflection Rules.
- Understand the bias point concept for linear amplification.
- Be able to separate the DC and AC analysis for a circuit containing a BJT.
- Be able to analyze a circuit (with or without cap in it) containing a BJT for DC operation.
- Be able to draw a small-signal model of a BJT circuit.
- Analyze a small-signal circuit to find overall gain, midband gain, input resistance, and output resistance.
- Determine ω_L or f_L .

Use $|V_{BE}|=0.7$, $\beta=100$, ignore r_o .

The 0.25A current source is not ideal and may have a voltage drop across it.

(a) Solve the circuit for the DC values. (assume capacitors act as open). Find all currents and voltages

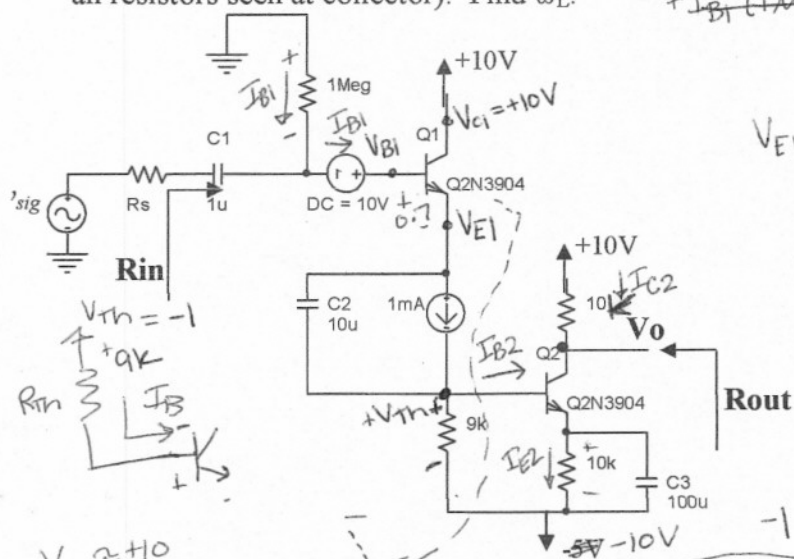(b) Solve the circuit for midband gain, V_o/v_{sig} , R_{in} (ignore R_s), and R_{out} (include all resistors seen at collector). Find ω_L .



$$I_E \approx 1mA \quad I_C = \alpha I_E = 0.99mA$$

$$I_B = \frac{I_E}{\beta} = \frac{1mA}{101} \approx 10\mu A$$

$$+I_B(1M\Omega) - 10 + V_{BE} = 0$$

$$V_{BE} = +10 - I_B(1M\Omega) = 0V$$

$$V_{E1} = V_{B1} - V_{BE} = -0.7V$$

$$V_{C1} = +10$$

$$\Rightarrow V_{C1} > V_{B1} > V_{E1} \text{ ACTIVE}$$

$$V_{th} = 1mA(9k) - 10 = -10 - 9 = -1V$$



$$I_B = \frac{I_E}{\beta + 1}$$

$$-1 - I_B(9k) - 0.7 - I_E(10k) + 10 = 0$$

$$\frac{(10 - 1 - 0.7)}{\frac{9k}{101} + 10k} = I_E$$

$$I_E = 0.8mA$$

$$I_B = 8\mu A \quad I_C = 0.79mA$$

$$V_o = -g_{m2} V_{\pi 2}(10k)$$

$$r_{\pi 2} = \frac{V_T}{I_B} = \frac{25mV}{8\mu A}$$

$$r_{\pi 2} = 3125, g_{m2} = \beta / r_{\pi 2} = 32mS$$


$$r_{\pi 1} = \frac{25mV}{10\mu A} = 2500, g_{m1} = 40mS$$

$$V_{\pi 2} = V_1 \frac{(r_{\pi 2} || 9k)(\beta + 1)}{(r_{\pi 2} || 9k)(\beta + 1) + r_{\pi 1}}$$

$$= 0.99V$$

$$V_o = -g_{m2}(0.99)(0.66)V_{sig}(10k)$$

$$\frac{V_o}{V_{sig}} = 209 V/V$$

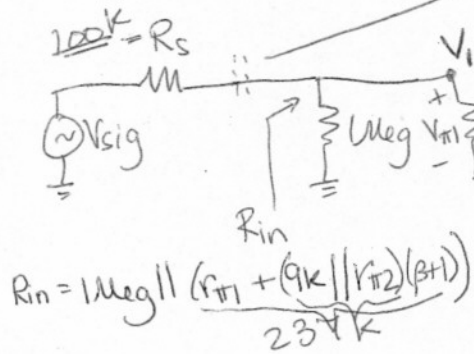

$$R_{in} = 100k || (1M || (r_{\pi 1} + (9k || (r_{\pi 2})(\beta + 1))))$$

$$R_{in} \approx 192k$$

$$V_i = V_{sig} \frac{R_{in}}{R_{in} + 100k} \approx 0.66 V_{sig}$$

The material we have covered so far this semester is summarized (but NOT limited to) below:


- Understand the basic operation of a BJT:
 - Cutoff, saturation, active. Analyze a circuit for all current equations and voltages (current relationships)
 - Make sure to be able to take a Thevenin Equivalence and use Resistance Reflection Rules.
- Understand the bias point concept for linear amplification.
- Be able to separate the DC and AC analysis for a circuit containing a BJT.
- Be able to analyze a circuit (with or without cap in it) containing a BJT for DC operation.
- Be able to draw a small-signal model of a BJT circuit.
- Analyze a small-signal circuit to find overall gain, midband gain, input resistance, and output resistance.
- Determine ω_L or f_L .

Use $|V_{BE}|=0.7$, $\beta=100$, ignore r_o .

The 0.25A current source is not ideal and may have a voltage drop across it.

(a) Solve the circuit for the DC values. (assume capacitors act as open). Find all currents and voltages

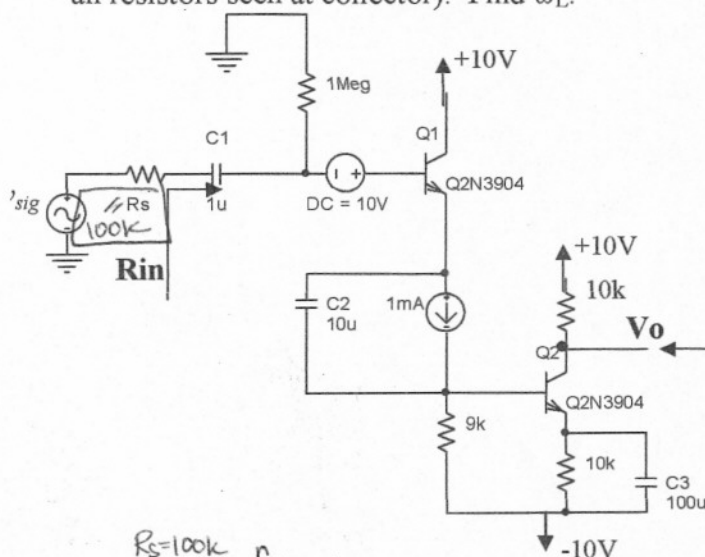(b) Solve the circuit for midband gain, V_o/v_{sig} , R_{in} (ignore R_s), and R_{out} (include all resistors seen at collector). Find ω_L .




$r_{\pi 1} = 2500$, $g_{m1} = 40m$
 $r_{\pi 2} = 3125$, $g_{m2} = 32m$

$C_1 \Rightarrow \frac{1}{C_1(R_s + R_{in})} = \frac{1}{1\mu(100k + 192k)} = 3.4 \frac{rad}{sec}$

$C_2 \Rightarrow \frac{1}{C_2 \left[\left(\frac{r_{\pi 1} + 1M || 100k}{\beta + 1} \right) + (9k || r_{\pi 2}) \right]}$
 $= \frac{1}{10\mu(925 + 2320)} \approx 31 \frac{rad}{sec} \approx 5Hz$

$C_3 \Rightarrow \frac{1}{C_3 \left[10k || \left[r_{\pi 2} + 9k || \left(\frac{r_{\pi 1} + 1M || 100k}{\beta + 1} \right) \right] \right]}$
 $= \frac{1}{C_3 [10k || 39]} = 257 \frac{rad}{sec} \approx 41Hz$


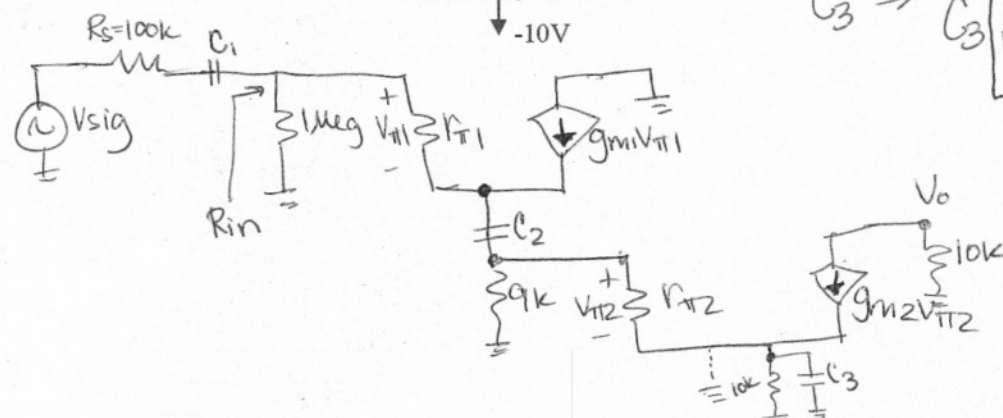


2. Use $|V_{BE}|=0.7$, $\beta=100$. Use $g_{m1}=1\text{mA/V}$, $g_{m2}=2\text{mA/V}$, $g_{m3}=4\text{mA/V}$, $r_{o3}=100\text{k}$. Find V_o/V_{sig} , R_{out} (ignore $r_{\pi2}=\frac{\beta}{g_{m2}}=\frac{50\text{k}}{2\text{mA}}=25\text{k}$ on the right), R_{in} (ignore 50 from signal source).

$$R_{in} = 100 + \frac{r_{\pi2}}{\beta+1} = 100 + \frac{50\text{k}}{101} = 595$$

$$R_{out} = 20\text{k} \parallel r_{o3} = 16.7\text{k}$$
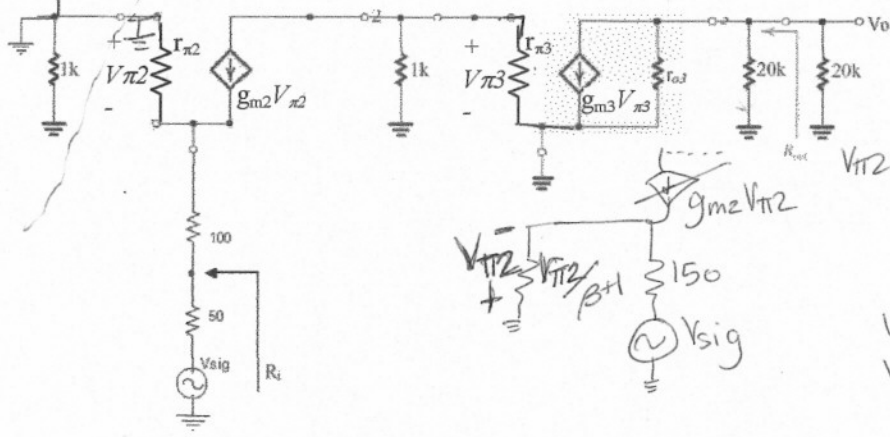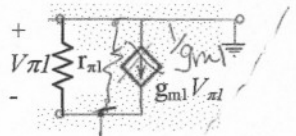
$$r_{\pi3} = \frac{100}{4\text{mA}} = 25\text{k}$$



$$V_{out} = -g_{m3} V_{\pi3} (r_{o3} \parallel 20\text{k} \parallel 20\text{k}) = -4\text{m} (9091) V_{\pi3}$$

$$V_{\pi3} = -g_{m2} V_{\pi2} (1\text{k} \parallel r_{\pi3})$$

$$V_{\pi3} = -2\text{m} (962) V_{\pi2}$$

$$V_{\pi2} = \frac{-V_{sig} (\frac{r_{\pi2}}{\beta+1})}{\frac{r_{\pi2}}{\beta+1} + 150} = \frac{-V_{sig} (495)}{495 + 150}$$



$$= -0.77 V_{sig}$$

$$\frac{V_{out}}{V_{sig}} = -4\text{m} (9091) (-2\text{m}) (962) (-0.77)$$

$$= -54\text{V/V}$$

$$V_{\pi2} = \frac{-V_{sig} (r_{\pi2})}{r_{\pi2} + 150(\beta+1)} = -0.77 V_{sig}$$

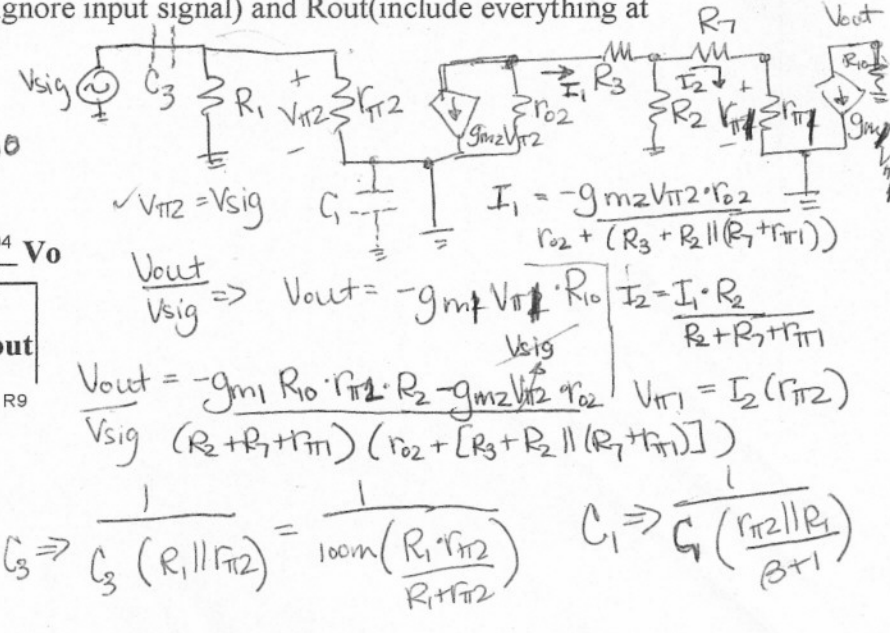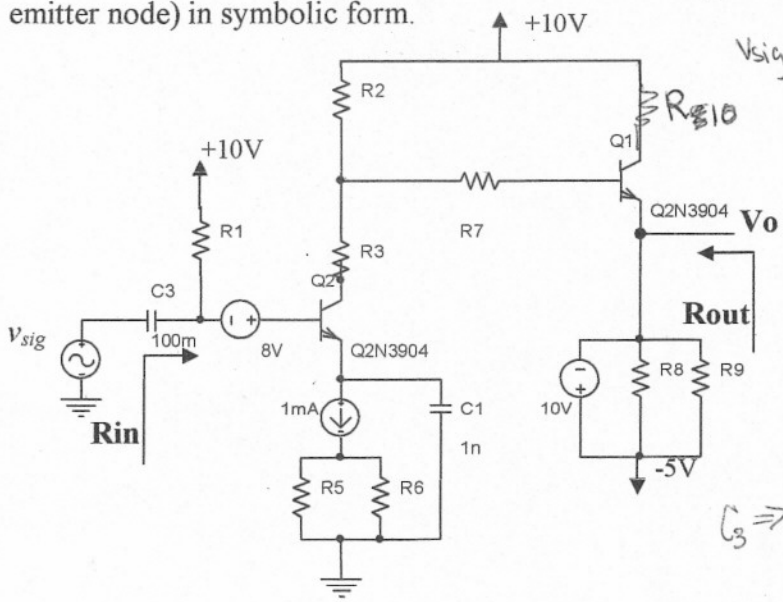3. Draw the small-signal equivalent circuit. Find R_{in} (ignore input signal) and R_{out} (include everything at emitter node) in symbolic form.



$$V_{\pi2} = V_{sig}$$

$$I_1 = \frac{-g_{m2} V_{\pi2} \cdot r_{o2}}{r_{o2} + (R_3 + R_2 \parallel (R_7 + r_{\pi1}))}$$

$$\frac{V_{out}}{V_{sig}} \Rightarrow V_{out} = -g_{m1} V_{\pi1} \cdot R_{10} \cdot \frac{R_2}{R_2 + R_7 + r_{\pi1}}$$

$$V_{out} = \frac{-g_{m1} R_{10} \cdot r_{\pi2} \cdot R_2 - g_{m2} V_{\pi2} \cdot r_{o2}}{(R_2 + R_7 + r_{\pi1}) (r_{o2} + [R_3 + R_2 \parallel (R_7 + r_{\pi1})])}$$

$$C_3 \Rightarrow \frac{1}{C_3 (R_1 \parallel r_{\pi2})} = \frac{1}{100\text{m} (\frac{R_1 \cdot r_{\pi2}}{R_1 + r_{\pi2}})}$$

$$C_1 \Rightarrow \frac{1}{C_1 (\frac{r_{\pi2} \parallel R_1}{\beta+1})}$$