

150 pts Lab #2 Notebook Grading

THE FOLLOWING ITEMS ARE REQUIRED:

- Student's work reproducible from notebook.
- Title and date for each lab section.
- Written in ink.
- Student signed every page.
- Student dated every page.

30 pts PRE-LAB:

10 pts (1a)

6 pts Design a circuit to produce $V_{out} = V_{in}$.

10 pts (2)

6 pts Design a non-inverting amplifier to produce a gain of 101 V/V.

4 pts Build the non-inverting amplifier on your breadboard.

10 pts (2a)

5 pts Description of slew-rate.

5 pts Description of clipping.

30 pts EXPERIMENT 1:

5 pts 1.

1 pt Measurement of V_{out} .

1 pt Measurement of current through the 1k "load" resistor.

3 pts Describe in detail where the additional current comes from.

15 pts 2.

10 pts Created Bode magnitude plot.

5 pts Rough sketch of the Bode magnitude plot with the following points marked:
low-frequency value in the flat section, "corner" frequency (f_c), and the downward slope.

5 pts 3.

Comparison of measured f_c and expected f_c .

5 pts 4.

Verification that $V_{out} \sim V_s$ for a reasonable frequency.

50 pts EXPERIMENT 2:

15 pts (1b) Verification of gain (should be 101 V/V) for a low-frequency value.

5 pts (1c) -3dB point.

5 pts (1e) 2 measurements beyond f_c and the slope of the frequency response curve.

5 pts (1f)

2 pts Measurement of the phase shift at f_c .

3 pts Comparison of the theoretical phase-shift (-45°) to your measured phase-shift.

5 pts (1g)

1 pt Measurement of the gain at $5f_c$.

1 pt Measurement of the gain and phase-shift at $10f_c$.

1 pt Comparison of theoretical gain decrease (factor of 2) to your measured gain decrease.

2 pts Comparison of theoretical phase-shift of -90° at $10f_c$.

5 pts (2a)

1 pt Sketch of the triangular waveform and indication of the slewing on the sketch.

1 pt Measurement of the slope of the triangular waveform.

3 pts Comparison of measured slew-rate to the slew-rate on the data sheet.

5 pts (2b)

1 pt Value for f_{max} .

1 pt Measurement of the output voltage (V_{pp}) at f_{max} .

3 pts Comparison of f_{max} to the theoretical value of f_{max} .

5 pts (3a)

1 pt Sketch of the clipping waveform and indication of the clipping on the sketch.

1 pt Measurements of the clipping levels L_+ and L_- .

3 pts Comparison of the data-sheet clipping levels to your measured clipping values.

40 pts EXPERIMENT 3

25 pts 1.

10 pts Circuit built correctly.

15 pts Circuit works.

8 pts 2. Description of how the volume-control works.

7 pts 3. How much current is being pulled away from the power-supply.