
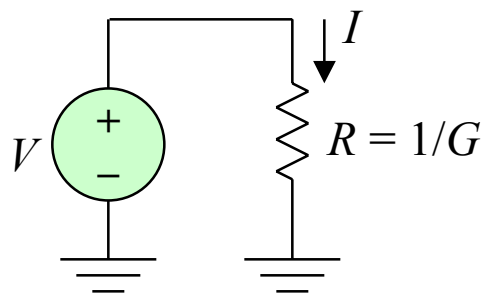



Small-Signal Concepts


ECE 3110

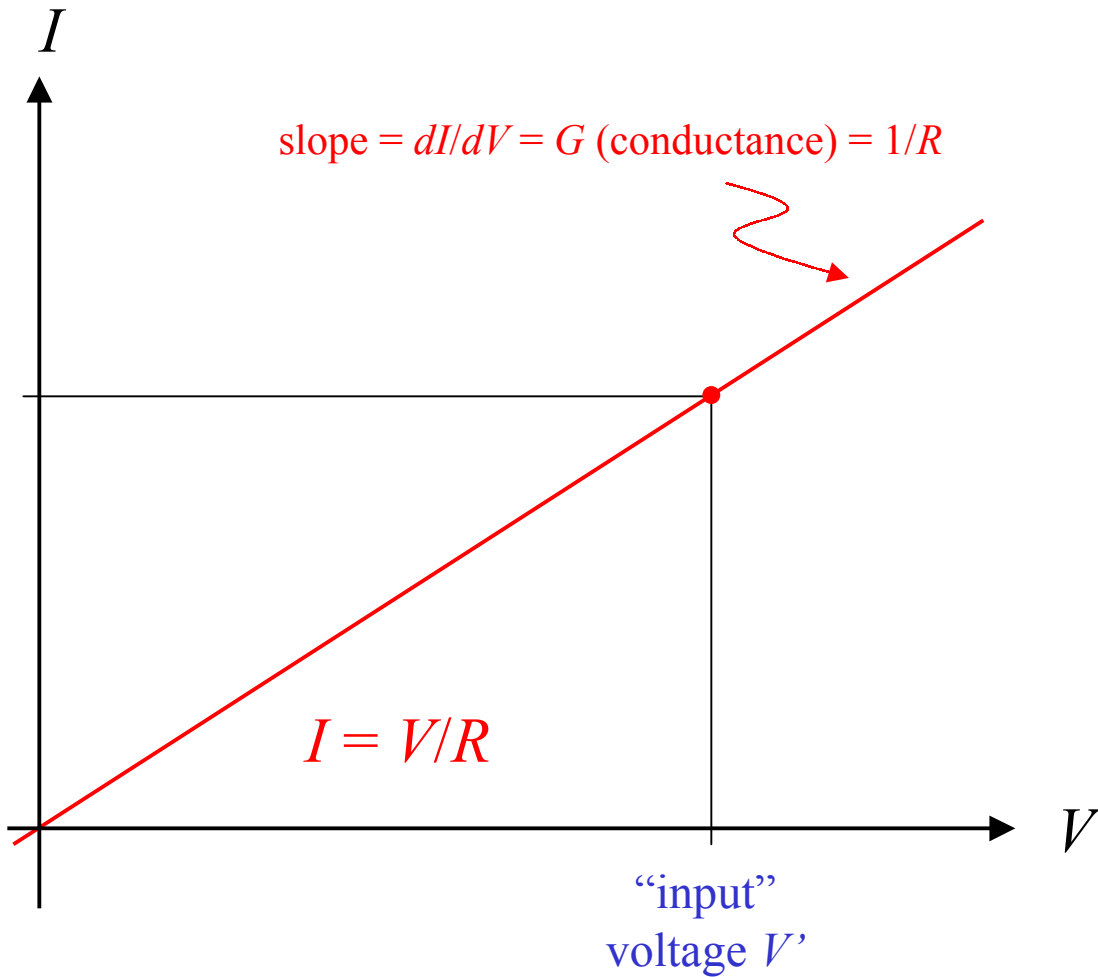


“output” current I




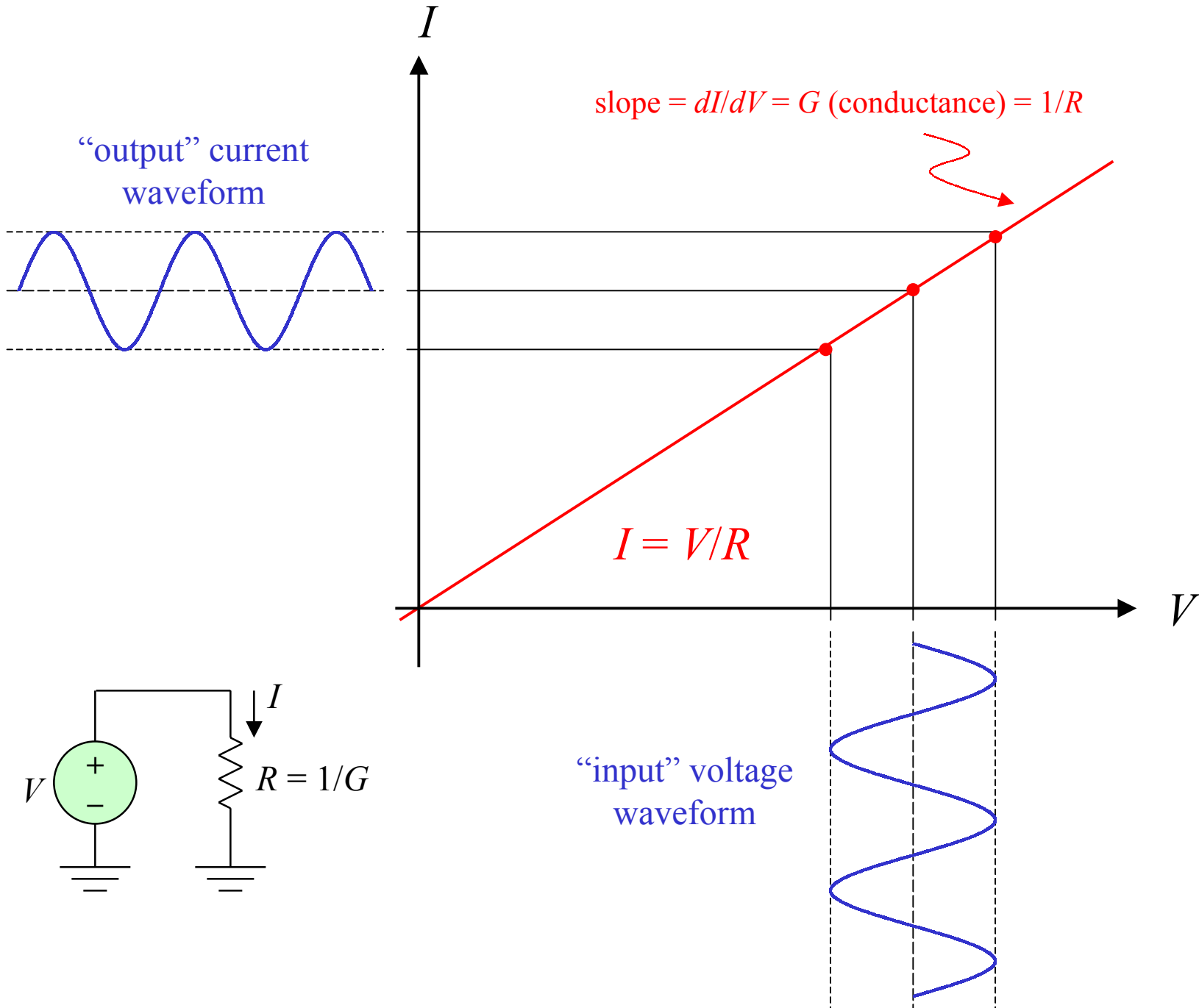


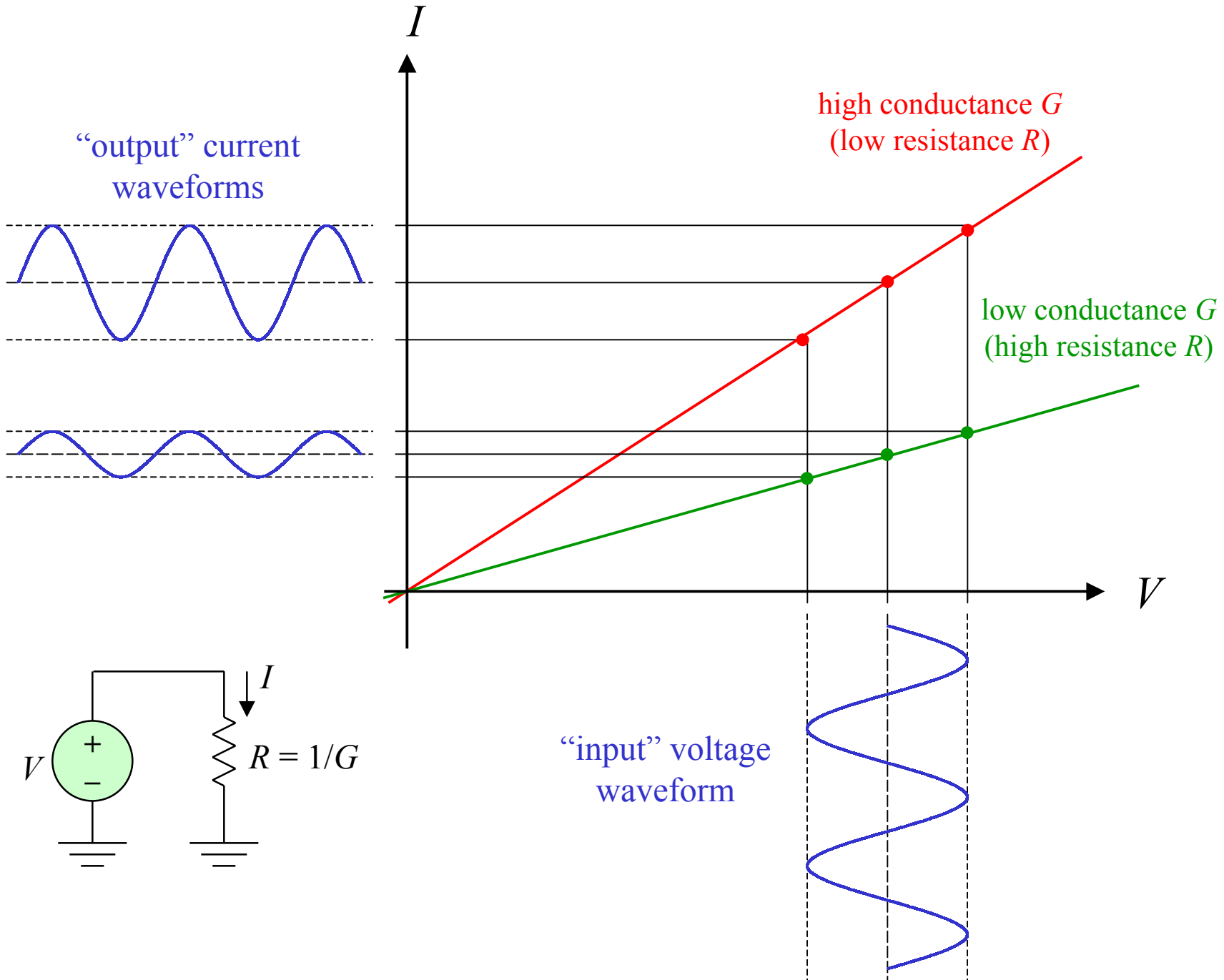

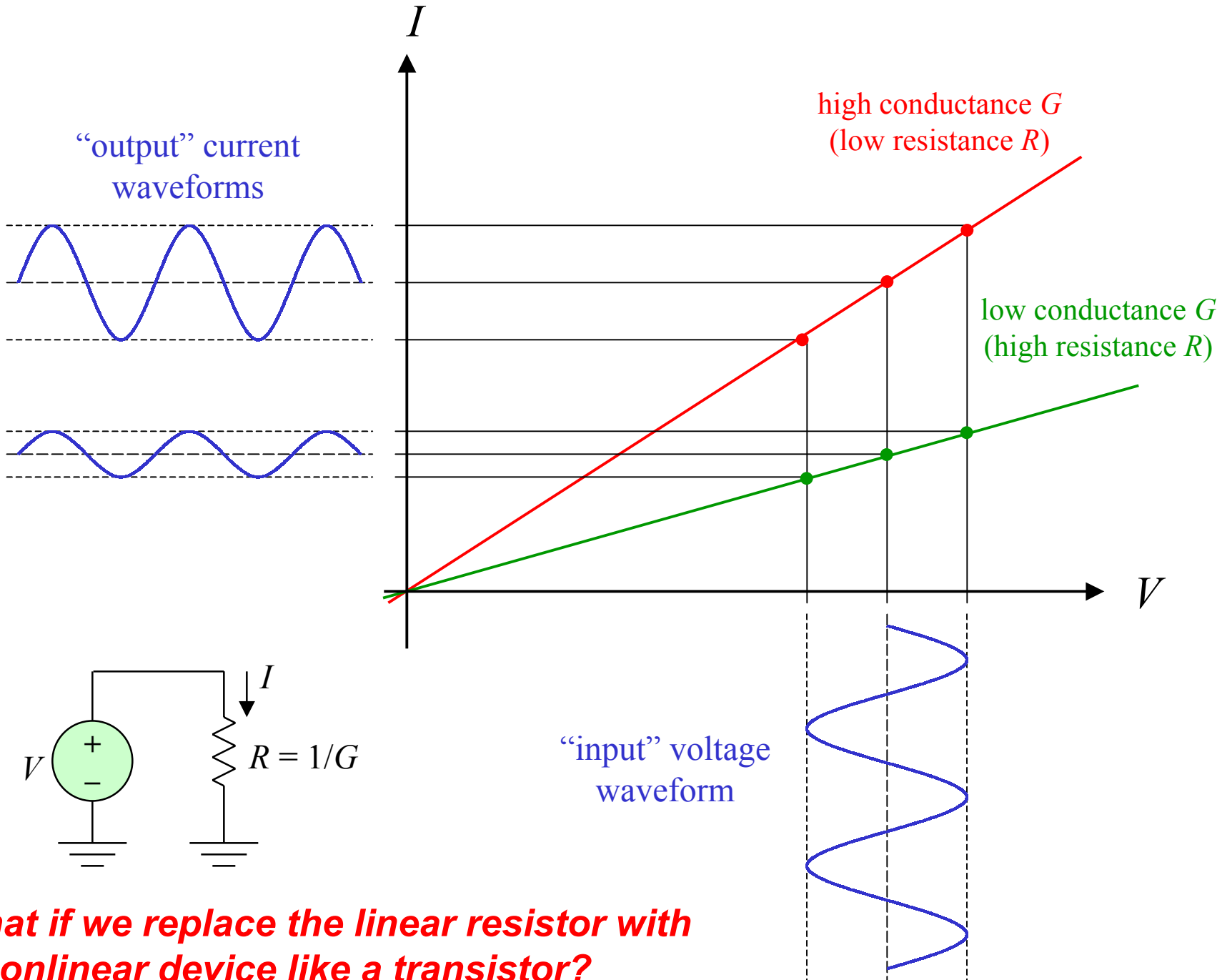


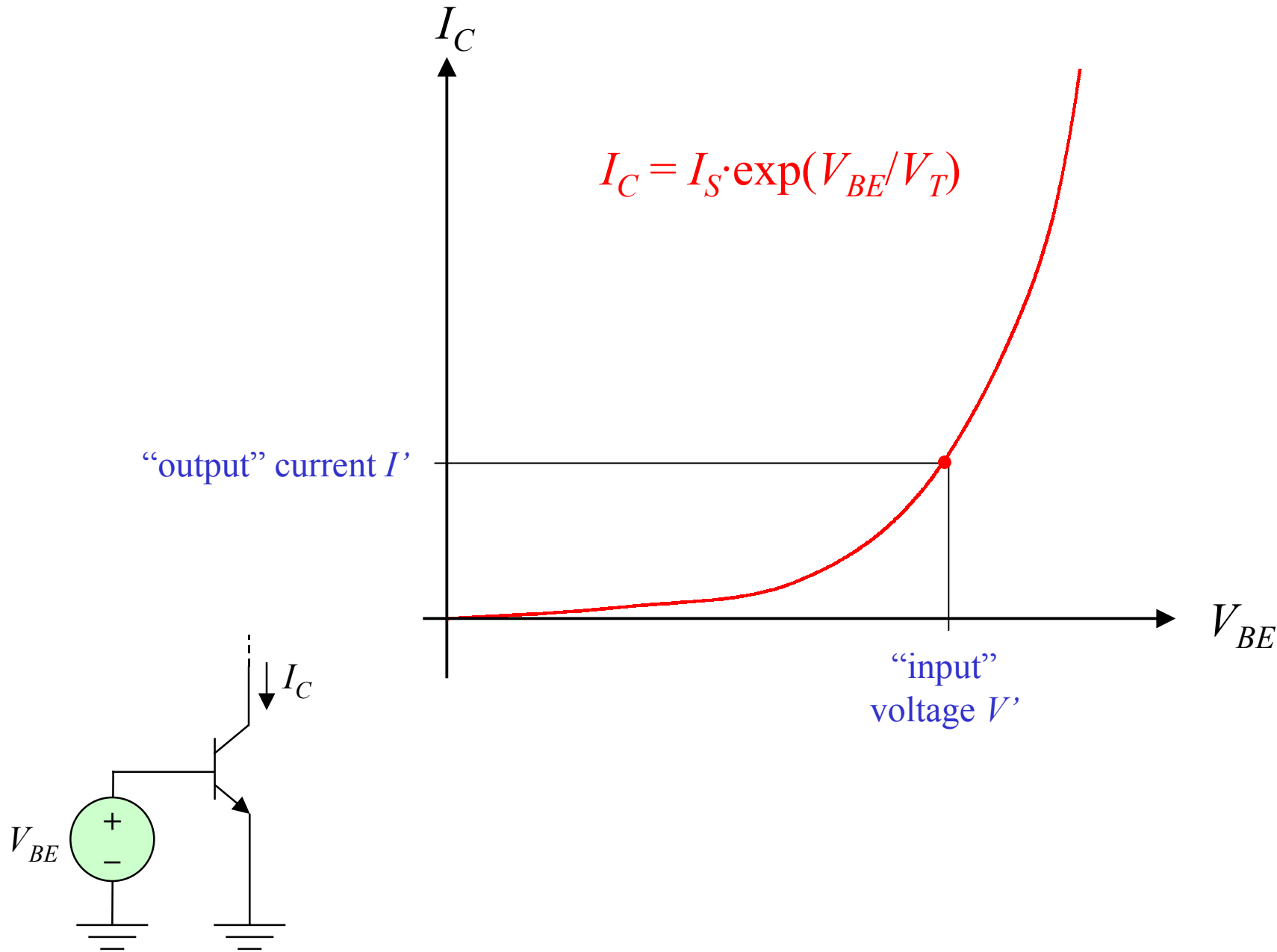
What if we replace the linear resistor with a nonlinear device like a transistor?



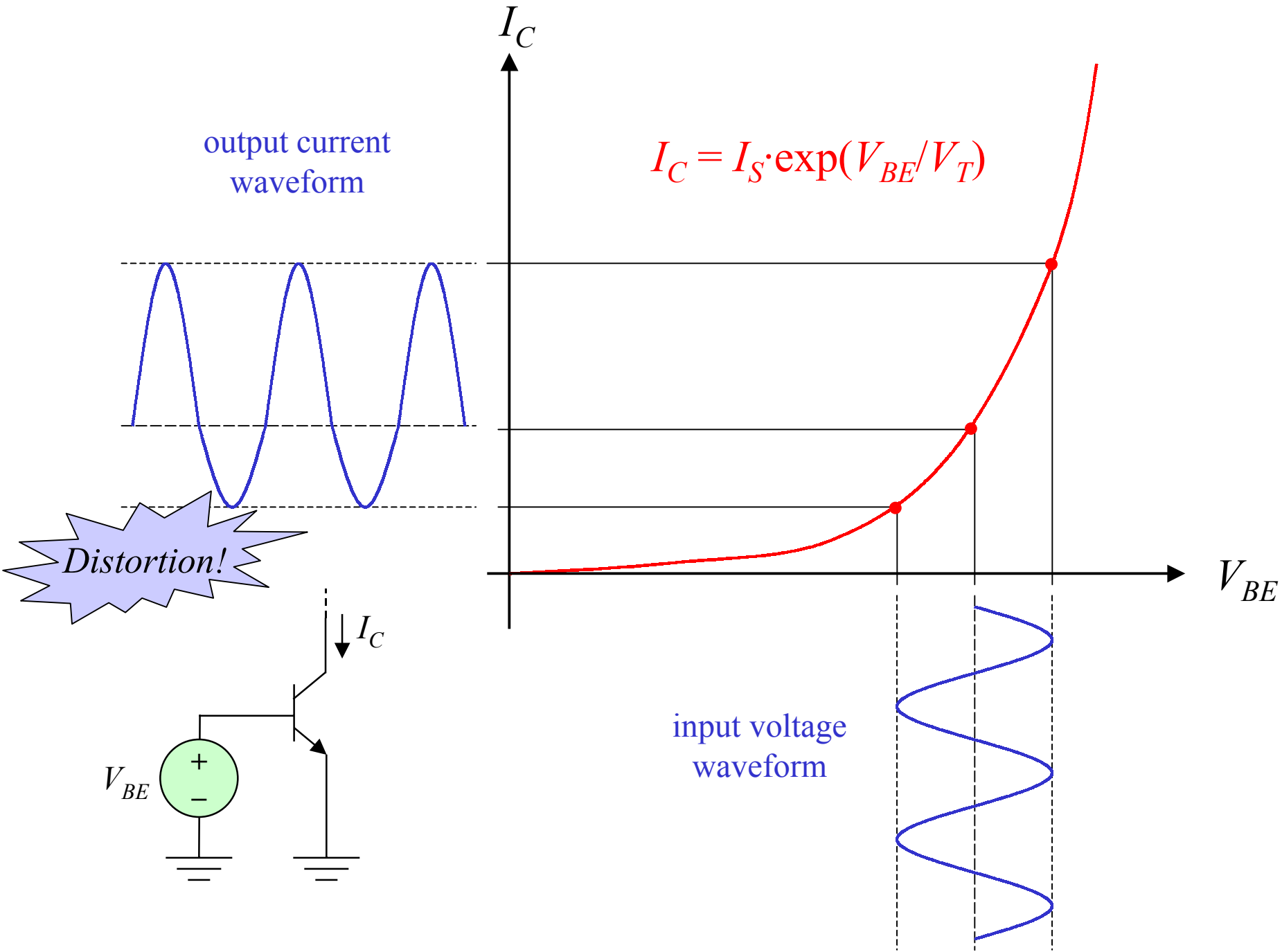

Distortion can be managed if signal swing is kept sufficiently small


output current waveform

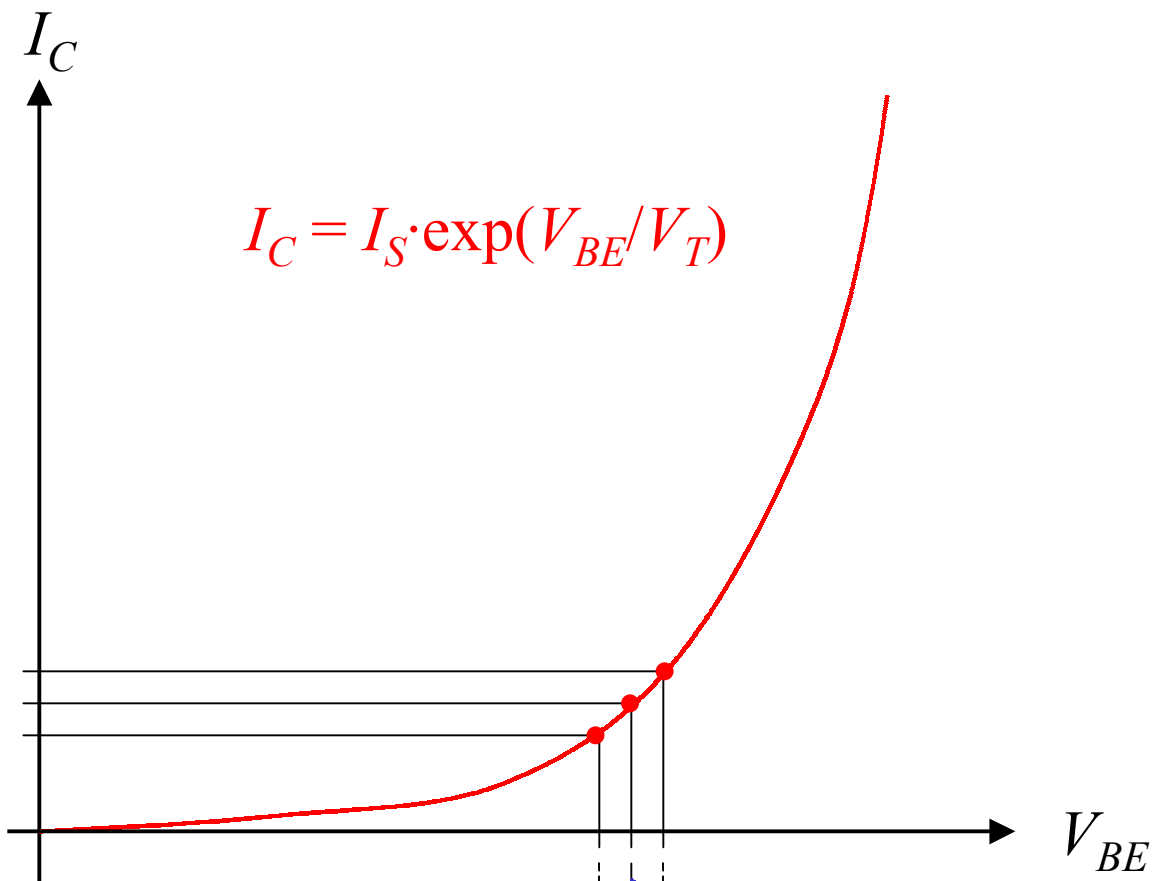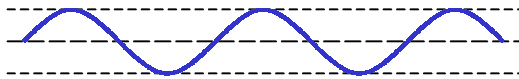



$$I_C = I_S \cdot \exp(V_{BE}/V_T)$$


V_{BE}


input voltage waveform

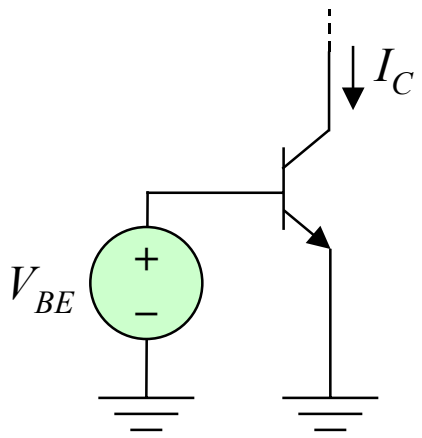

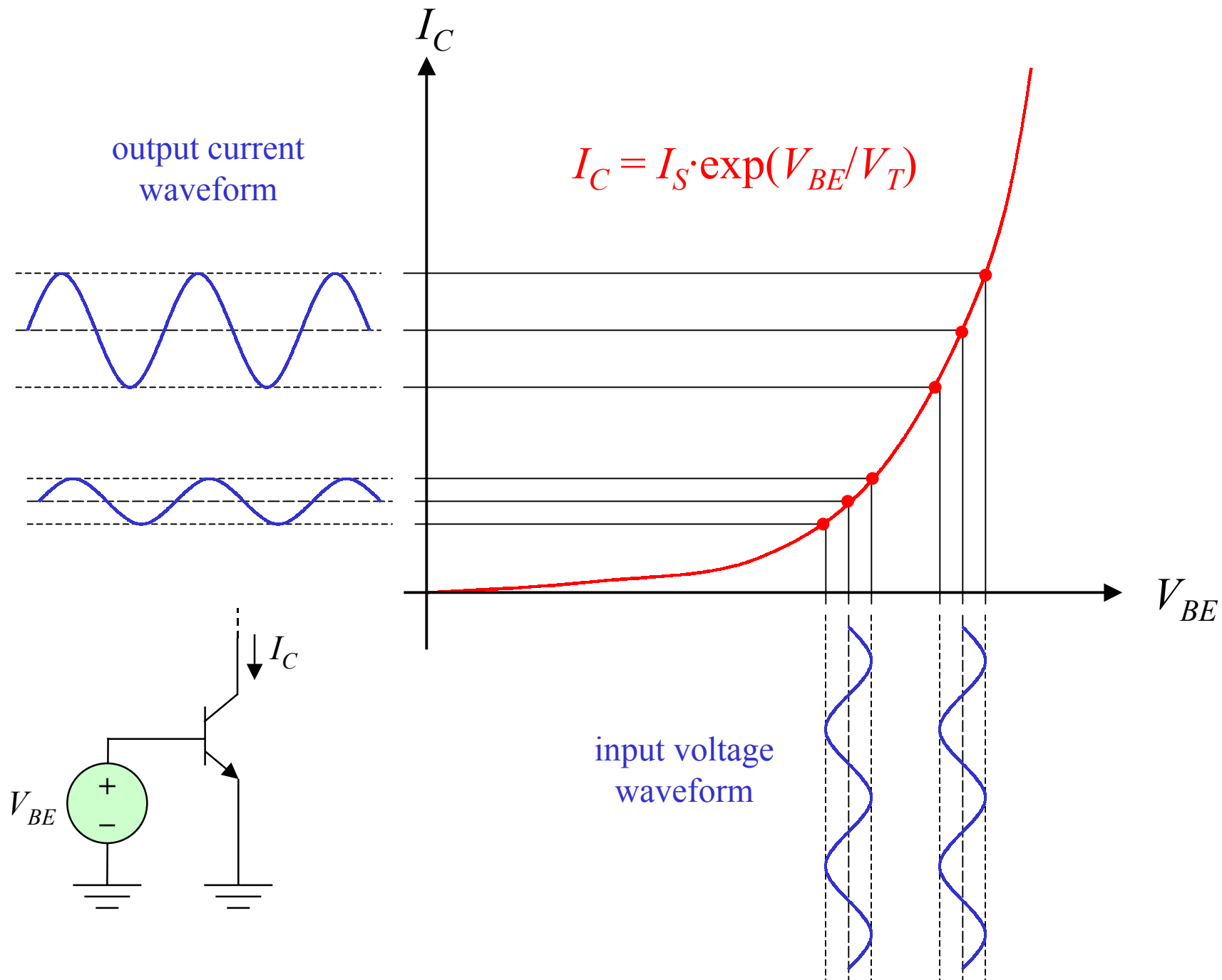

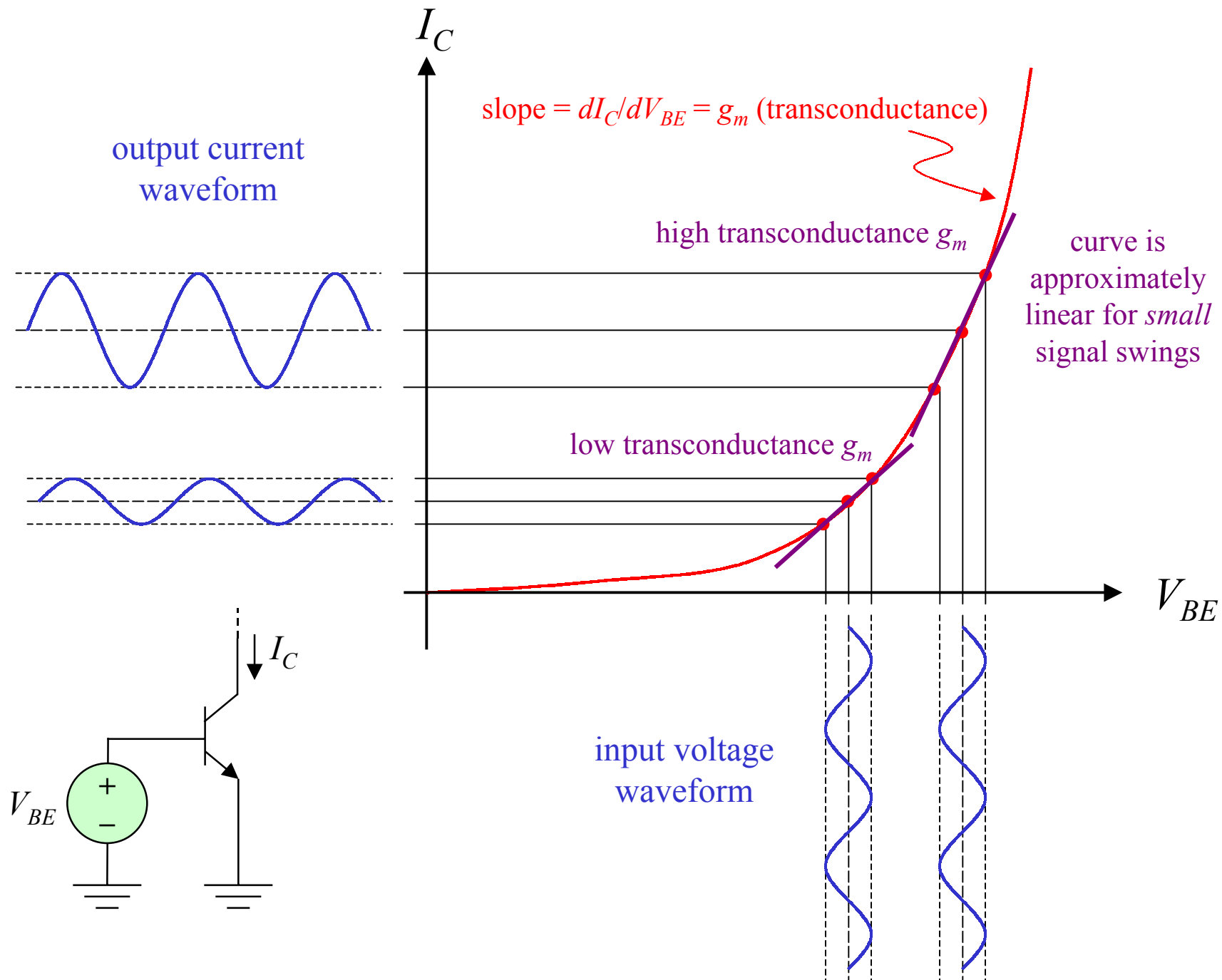

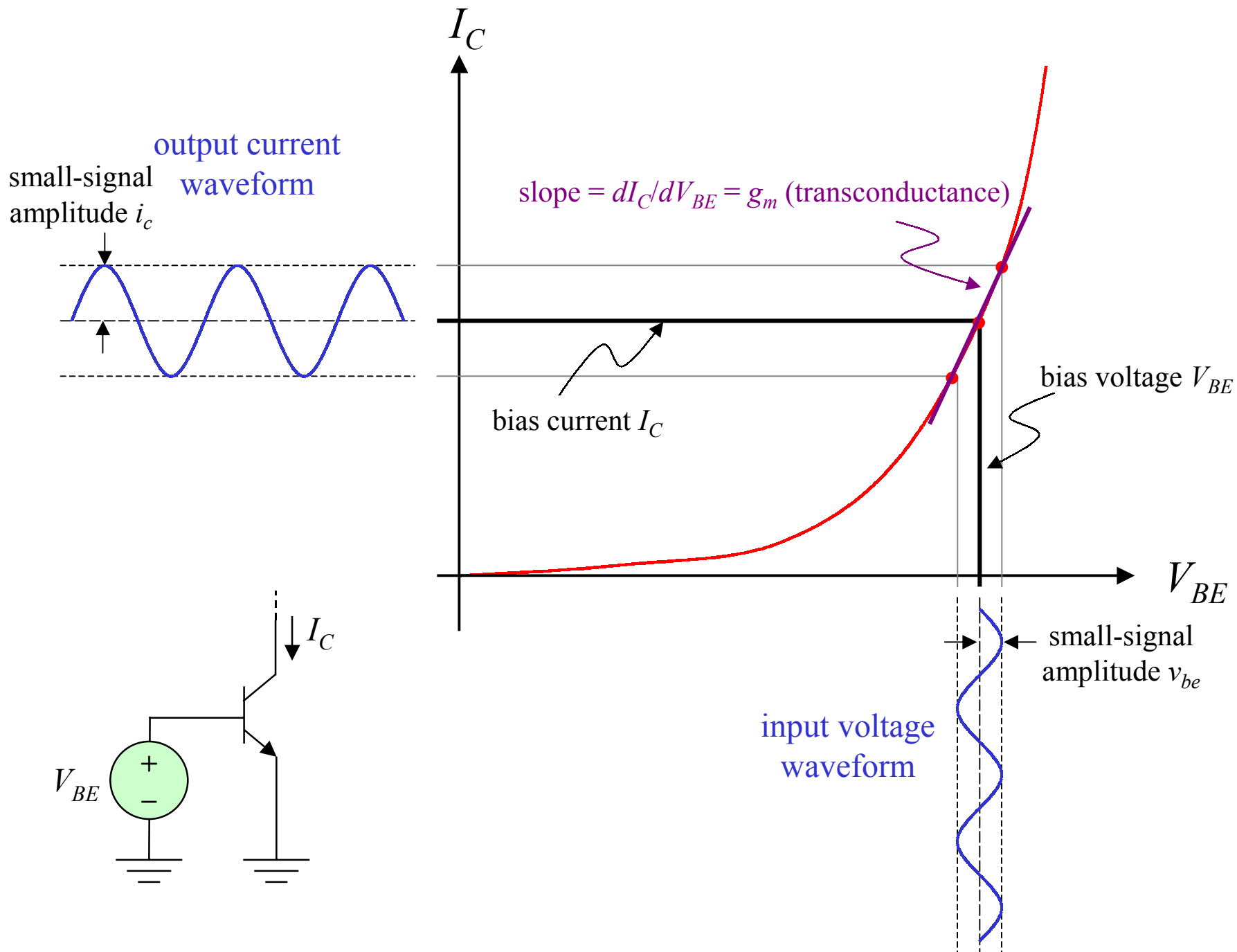

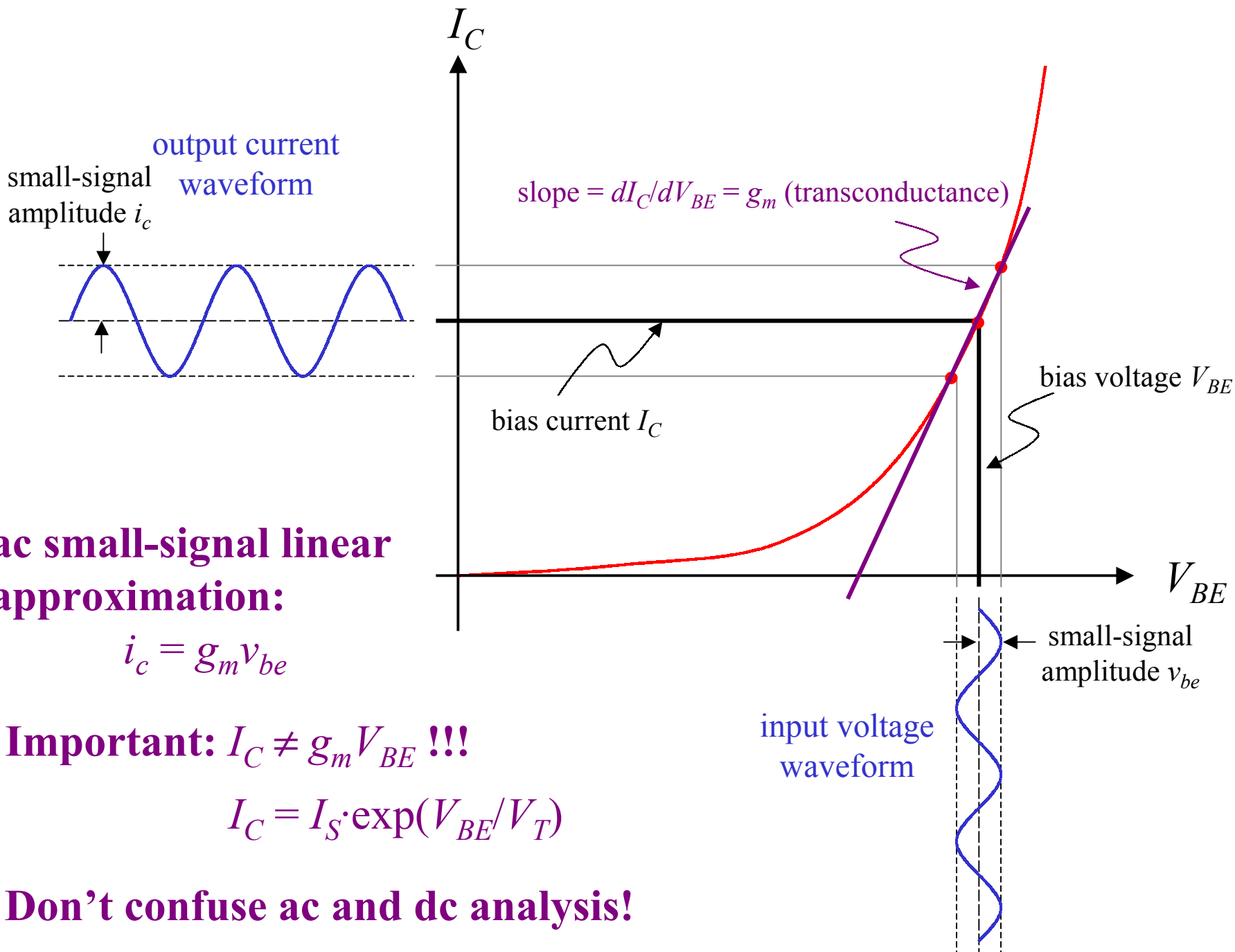

ac small-signal linear approximation:

$$i_c = g_m v_{be}$$

Important: $I_C \neq g_m V_{BE}$!!!

$$I_C = I_S \cdot \exp(V_{BE}/V_T)$$

Don't confuse ac and dc analysis!