


① Calculate

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} \quad \Gamma_g = \frac{R_g - Z_0}{R_g + Z_0}$$

Time delay from  $z=0$  to  $l$

$$\tau = l/v_p$$

Voltage incident on the line

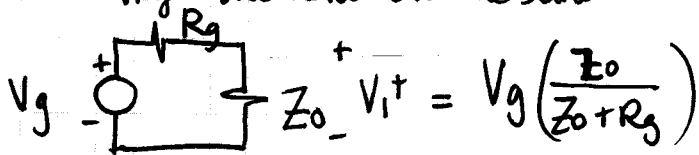


All other voltages


$$V_1^- = V_1^+ \Gamma_L \quad V_2^+ = \Gamma_g V_1^-$$

$$V_2^- = V_2^+ \Gamma_L \quad \dots$$

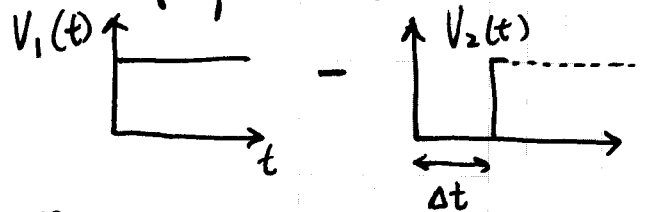② Observe that the pulse is the sum of two step functions...



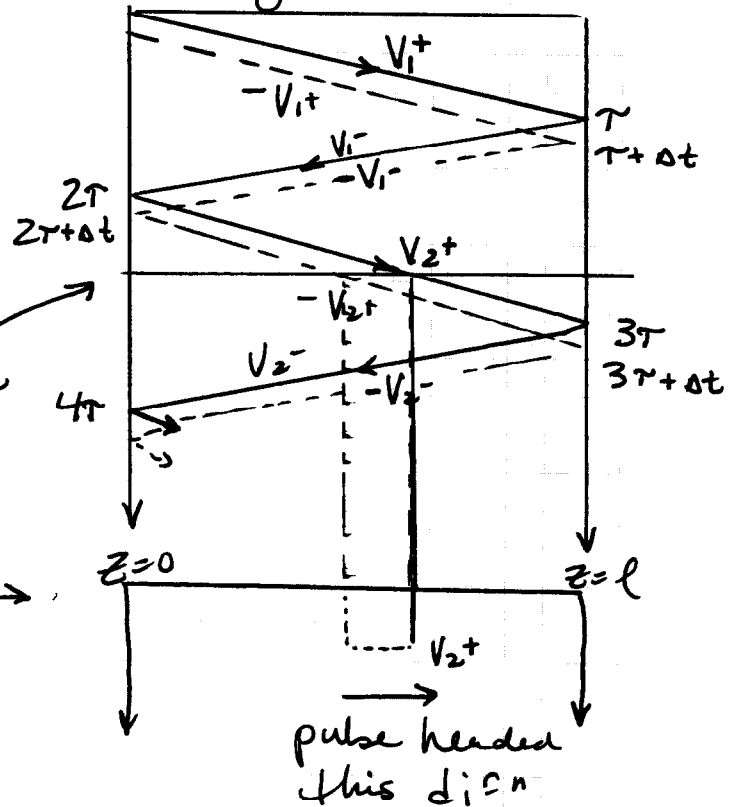③ Draw a bounce diagram showing  $V_1(t)$  &  $V_2(t)$




④ Find voltage @  $t = 2.5\tau$  on the line

Note use of solid & dashed lines to show leading & lagging edge of pulse.
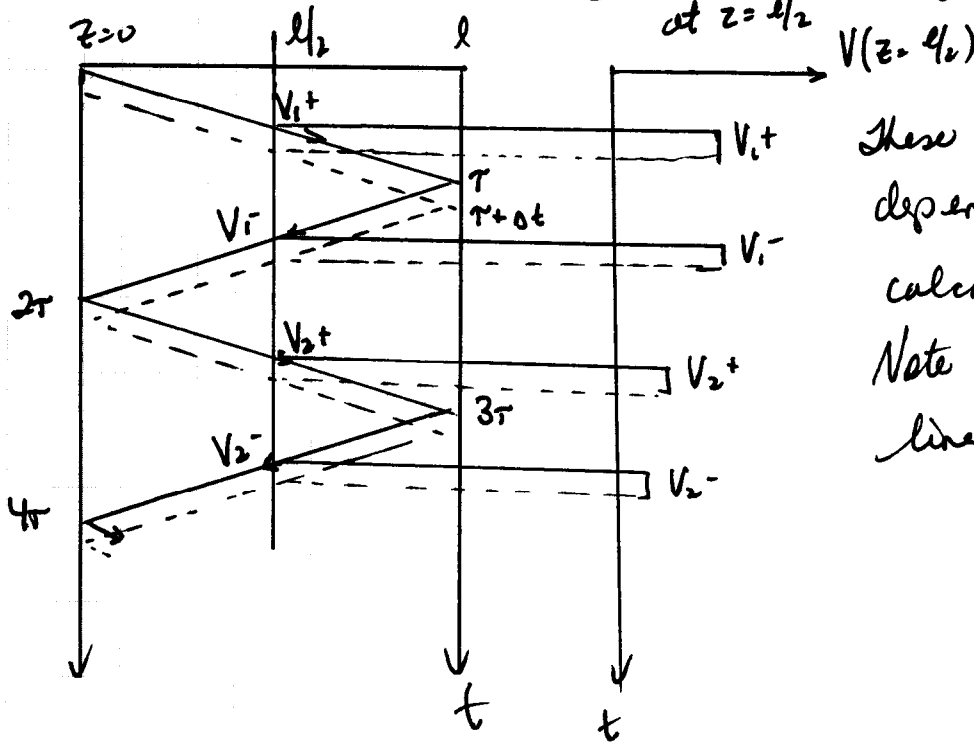
## PULSED TRANSIENTS (2)


⑤ Find the voltage as a function of time at  $z = l/2$



These may be  $\oplus$  or  $\ominus$  depending on your calculations.

Note solid, dashed lines

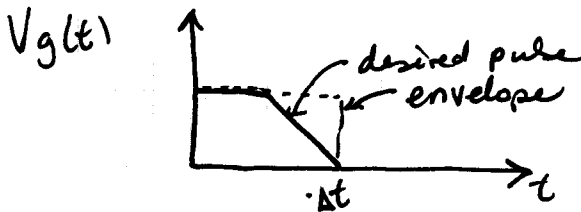
Now, if pulse has a shape, use an envelope as shown




Solve the problem as above for the rectangular envelope (pulse width  $\Delta t$ ).

Then redraw, using the solid & dashed lines to guide you

Part ④ Becomes:

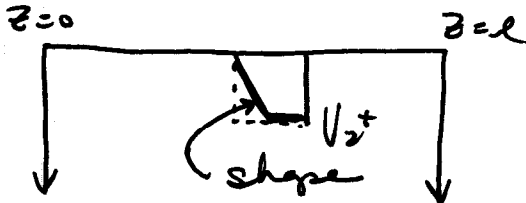

Part ⑤ Becomes

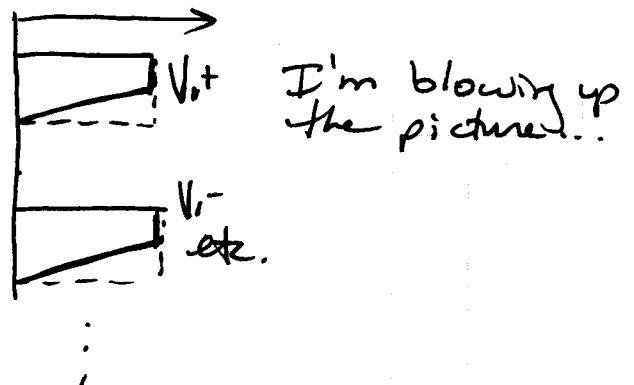

I'm blowing up the picture...