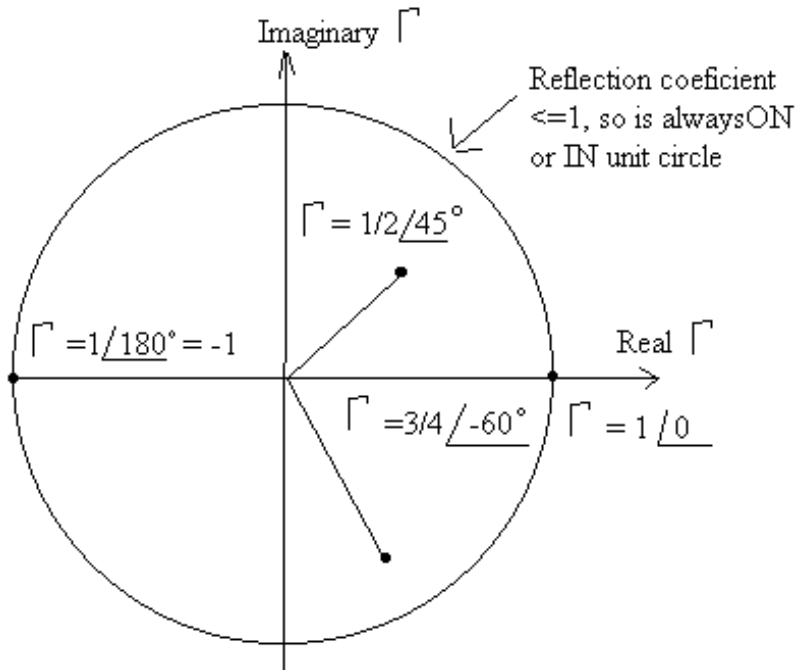


## ECE 3300 SMITH CHARTS

### Smith Chart Circles:

A Smith chart is a graphical representation of the complex reflection coefficient,  $\Gamma$



### Smith Chart for Reflection Coefficient and Load Impedance:

Reflection Coefficient and Load ( $Z_L$ ) are directly related:



$$\Gamma = (Z_L / Z_0 - 1) / (Z_L / Z_0 + 1) = (z_L - 1) / (z_L + 1)$$

OR

$$Z_L / Z_0 = z_L = (1 + \Gamma) / (1 - \Gamma) \leftarrow \text{This is NORMALIZED load impedance}$$

$$z_L = r_L + j x_L$$

The real and imaginary parts of  $z_L$  are functions of  $\Gamma$ , and these functions can be plotted on the same chart. Remember  $|\Gamma| \leq 1$ .

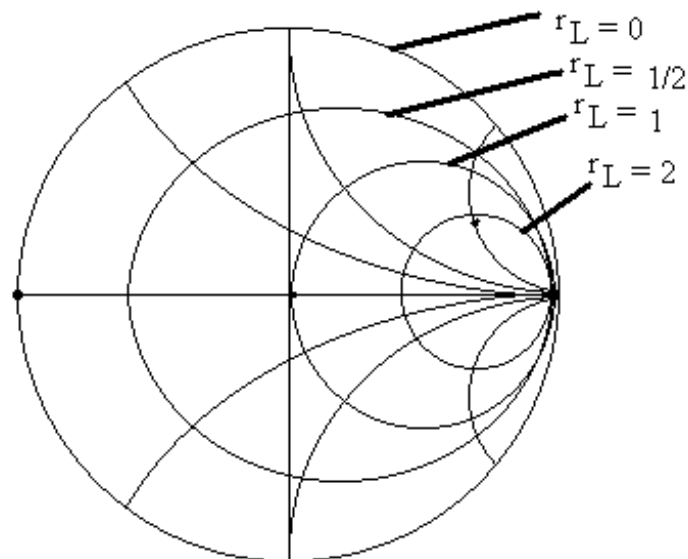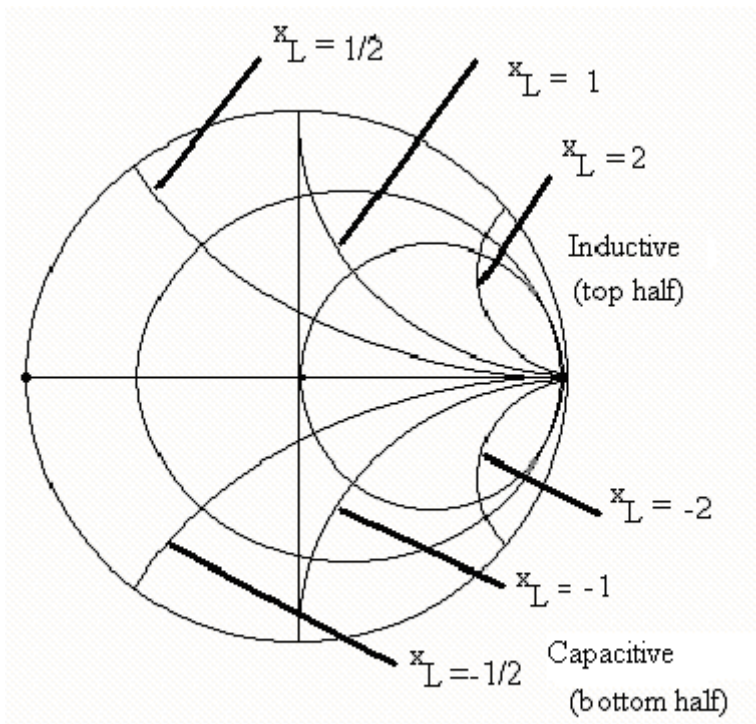

Example: Given  $Z_L$ , find  $\Gamma$  using Smith Chart

See transparencies (Copies to be made available in copy room)

How to find  $\Gamma$  :

- 1) Find Normalized load Impedance,  $z_L = Z_L / Z_0 = r_L + j x_L$
- 2) Find intercept of semicircles for  $r_L$  and  $x_L$  and PLOT  $z_L$
- 3) Draw line from center of smith chart to (or through)  $z_L$
- 4) Read angle of  $\Gamma$  from outside of Smith chart
- 5) Measure  $|\Gamma|$  with a protractor and compare to line on bottom of smith chart labeled "Ref. Coeff. E or  $\Gamma$ "

$Z_0 = 100 \text{ ohms}$

$Z_L = \text{open circuit}$

- 1)  $z_L = \infty = \infty + j 0$
- 2) PLOT (far right)
- 3) Draw Line through  $z_L$ . Read  $\angle 0$
- 4) Measure using a protractor (or this one is obviously =1)  $|\Gamma| = 1$   
 $\Gamma = 1 \angle 0$  (which is what we expect for an open circuit)

$Z_L = \text{short circuit}$

- 1)  $z_L = 0 = 0 + j 0$
- 2) PLOT (far left)
- 3) Draw Line through  $z_L$ . Read  $\angle 180^\circ$
- 4) Measure using a protractor (or this one is obviously =1)  $|\Gamma| = 1$   
 $\Gamma = 1 \angle 180^\circ = -1$  (which is what we expect for an short circuit)

$Z_L = 100 + j 0 \text{ ohms}$

- 1)  $z_L = Z_L / Z_0 = 1 + j 0$
- 2) PLOT (center of smith chart)
- 3) Draw Line through  $z_L$ . Not so easy ...  $\angle ?$
- 4) Measure using a protractor (or this one is obviously =0)  $|\Gamma| = 0$   
 $\Gamma = 0 \angle ?$  (which is what we expect for a matched load)

$Z_L = 100 + j 100 \text{ ohms}$

- 1)  $z_L = Z_L / Z_0 = 1 + j 1$
- 2) PLOT (top right quadrant)
- 3) Draw Line through  $z_L$ . about  $\angle 63^\circ$
- 4) Measure using a protractor  $|\Gamma| = 0.45$   
 $\Gamma = 0.45 \angle 63^\circ$

$$\Gamma = (z_L - 1) / (z_L + 1) = (0+j1) / (2+j1) = 1 \angle 90^\circ / 2.236 \angle 26.56^\circ = 0.45 \angle 63.43^\circ$$

How do you find load impedance if given  $\Gamma$ ?

- 1) Plot  $\Gamma$
- 2) Read  $z_L = z_L + j z_L$
- 3) Unnormalize:  $Z_L = z_L * Z_0$

**Admittance vs. Impedance:**

Admittance  $y_L = 1 / z_L$

$$\Gamma = (z_L - 1) / (z_L + 1) = (1/y_L - 1) / (1/y_L + 1) = - (y_L - 1) / (y_L + 1) = 180 \text{ out of phase}$$

Steps to find  $\Gamma$  from  $y_L$ :

- 1) Find normalized  $y_L = Z_0 / Z_L = g_L + jb_L$
- 2) Plot it (Using same curves  $g=r$  and  $b=x$ )
- 3) "Transform it through the origin" ... Rotate 180 degrees = draw a line of equal length through the origin. Now you have found  $z_L$
- 4) Read  $\Gamma$  as before

EXAMPLE (See transparencies)

### Input Impedance:

$$Z_{in} = Z_0 [1 + \Gamma e^{-j2\beta l}] / [1 - \Gamma e^{-j2\beta l}]$$

$$z_{in} = Z_{in} / Z_0 = [1 + \Gamma e^{-j2\beta l}] / [1 - \Gamma e^{-j2\beta l}]$$

Define reflection coefficient at the input (NOT  $\Gamma_g$ ) as the reflection coefficient looking into the load from the input location.  $\Gamma_1 = \Gamma_L \angle -2\beta l$

This represents moving  $2\beta l$  radians towards the generator.

You can convert this distance to degrees, and read it off the outer circles on the Smith Chart (notice DIRECTION to the generator is marked)

OR  $2\beta l = 2(2\pi / \lambda) l = 4\pi (l / \lambda)$  This has been normalized for you on the outside circle around the Smith Chart. Observe that if  $l = \lambda$ , this represents 2 complete rotations around the Smith Chart.  $L = \lambda/2$  represents one complete rotation.

Does this make sense? For a Transmission line of length  $L = \lambda/2$ , traveling from generator to the load and back would represent a phase shift of 360 degrees ... one complete rotation.

$$\text{Then } z_{in} = [1 + \Gamma_1] / [1 - \Gamma_1]$$

How to find  $Z_{in}$  :

- 1) Normalize  $z_L = Z_L / Z_0$
- 2) Plot  $z_L$ . This also gives you  $\Gamma_L$ .
- 3) Rotate  $\Gamma$  distance  $l$  (given in wavelengths) TOWARDS the generator.
- 4) Read  $z_{in}$  and  $\Gamma_1$
- 5)  $Z_{in} = z_{in} * Z_0$

EXAMPLE (see transparencies)

### Standing Wave Ratio:

To read SWR from the Smith Chart:

- 1) PLOT  $z_L$

- 2) Draw a circle through it.
- 3) Read SWR from real axis to right ( $SWR \geq 1$ )

EXAMPLE (See transparencies)

**Voltage Minima and Maxima:**

To read Voltage maxima off Smith Chart:

- 1) PLOT  $z_L$
- 2) First Voltage maximum occurs on right side of real axis. First Voltage minimum occurs on left side of real axis.

EXAMPLE (See transparencies)