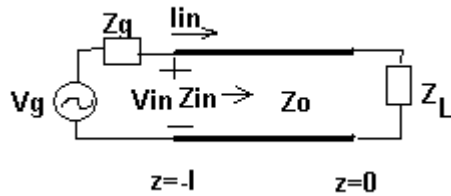


ECE3300 Lossless Transmission Lines



Given: V_g, Z_g

The line is a Coax. Given $a, b, \epsilon_r, \sigma, \mu, \sigma_c, \mu_c$

1. Which Voltage Variable describes: (Not all variables are shown on the picture.)

_____ = Total Voltage at the Input Terminal

_____ = Total Voltage at the Output Terminal

_____ = Total Voltage at the Generator

_____ = Total Voltage anywhere on the line

_____ = Forward-traveling voltage on the line

_____ = Negative-traveling voltage on the line

_____ = Magnitude of the reflected voltage

2. Which Impedance? (Z_{in}, Z_o, Z_L , other)

_____ = Total voltage at the input terminal / Total current at the input terminal

_____ = Forward-traveling voltage anywhere / Forward-traveling current anywhere


_____ = Negative-traveling voltage / Negative-traveling current

_____ = Forward-traveling voltage at the load / Forward-traveling current at the load

_____ = Total voltage at the load / Total current at the load

3. What is the voltage reflection coefficient? What is it a function of?

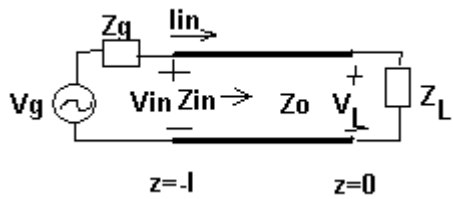4. If $V_o^- = 4 \angle \pi$ volts, sketch the reflected wave at the load as a function of time.



Answers:


1. V_{in} , V_L , V_g , $V(z)$, V_o^+ , V_o^- , $|V_o^-|$
2. Z_{in} , Z_o , Z_o , Z_o (anywhere! Even at the load), Z_L
3. $\Gamma = V_o^- / V_o^+$

Function of Z_o and Z_L

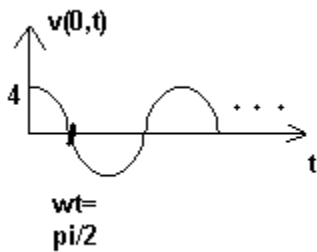4. $V_o^- = 4 \angle \pi = 4 e^{j\beta z + 0}$

$$V_o(z,t) = 4 \cos(\omega t + \beta z + 0)$$

$$V_o(0,t) = 4 \cos(\omega t + \beta 0 + 0)$$



Sketch: