# ECE 3600 Exam 1 given: Fall 08

(The space between problems has been removed.)

Write Legibly! This part of the exam is Closed book, Closed notes, No Calculator.

- (41 pts) Questions If I can't read what you've written or you answer is ambiguous, I'll assume you don't know.
- Electric Utilities have been forced to break up into two separate companies responsible for: a.
   b.
- 2. Give the two largest sources of energy used to produce electricity in the US. List the largest first.

2.

- 3. The Gadsby power plant (which we visited) uses what source of energy?
- 4. Give the approximate efficiency of a Rankin-cycle steam turbine power plant, regardless of the source of heat.
- 5. a) Why can't a wind turbine's coefficient of performance be 100%?
  - b) What two things can be controlled to maximize the coefficient of performance?
- Some power sources are used to supply base loads and some are used to supply peak loads.
  a) What is a "base load".
  - b) What is a "peak load".

1.

- c) The Gadsby power plant (which we visited) is used to supply what type of load?
- 7. a) \_\_\_\_\_ is the letter used for Magnetic Flux Density
  - b) \_\_\_\_\_ is the letter used for Magnetic Field Intensity
  - c) \_\_\_\_\_ is the letter used for Magnetic Permeability
  - d) How are these three things related to one another (give an equation)?
  - e) Name the common magnetic curve shown at right.
  - f) Label the axes on the figure shown at right.
- 8. List the 4 common long-distance high-voltage transmission line voltages given in your text.
- 9. What is bundling?
- 10. What insulates the wires from one another in an overhead transmission line?
- 11. A type of wire used in transmission lines has a steel core. What is it called (name or abbreviation)?
- 12 What is special about a transmission line that is loaded at 1 SIL?

## The following problems were handed out to the student after finishing the closed-book part.

This part of the exam is open book, open notes. You <u>MUST</u> show work to get credit. Show the correct units for each value. Assume  $f := 60 \cdot Hz$  for all problems and normal abc sequence for all  $3\phi$ 

- 1. (20 pts)  $R_L$ , &  $C_L$  together are the load in the circuit shown. The voltmeter measures 180 V, the ammeter measures 10 A, and the wattmeter measures 1440 W. Find the following:
  - a) The value of the load resistor.  $R_{\rm L}$  = ?
  - b) The apparent power. |S| = ?
  - c) The complex power. S = ?
  - d) The power factor. pf = ?
  - e) The power factor is: i) leading ii) lagging (circle one)



f) The two components of the load are in a box which cannot be opened. Add (draw it) another component to the circuit above which can correct the power factor (make pf = 1). Show the correct component in the correct place and <u>find its value</u>. This component should not affect the real power consumption of the load.



• A

480·V

3¢ source

 $V_{AB}$ 

All  $\mathbf{Z} := (30 + 12 \cdot \mathbf{j}) \cdot \Omega$ 

B = 0

2 (10 pts) Three impedances of  $\mathbf{Z}_{Load} = |\mathbf{Z}_{Load}| \frac{1-20^{\circ}}{2}$  are Y-connected to 3-phase lines.

$$arg(\mathbf{Z}_{Load}) = -20 \cdot deg$$

- a) What is the phase angle between  $I_A$  and  $V_{AB}$ ? Hint: a drawing of phasors will be very helpful.
- b) Circle one  $I_A$  leads  $V_{AB}$   $I_A$  lags  $V_{AB}$
- c) If the same load were connected in  $\Delta$ , how does that change the phase angle between I<sub>A</sub> and V<sub>AB</sub>?
- 3. (19 pts) Find the following:
  - a) The line current that would be measured by an ammeter.
  - b) The power consumed by the three-phase load.
  - c) The value of Y-connected impedances that would result in exactly the same line currents and same pf.

$$Z_{V} = ?$$

d) The value of Y-connected capacitors that would correct the pf.

## Exam 1, problem 4 is N/A so this is Exam 2, problem 2 given: Fall 08

2. (12 pts) A model of a 2:1 step-down transformer is shown below. The transformer is loaded with  $\mathbf{Z}_{\mathbf{L}} := (4 + 2 \cdot \mathbf{j}) \cdot \mathbf{c}$ . Find the power efficiency,  $\eta$ . 2:1 Ideal transformer



#### **Answers**

Closed-book part

- 1. a. Generation b. Transmission/distribution
- 2. 1. Coal 2. Nuclear 3. Natural Gas (partial credit if listed as #2)
- 3. Natural Gas 4. 35 40%
- 5. a) Can't stop the wind entirely or the air won't get out of the way. b) Blade pitch angle and rotational speed
- 6. a) The electrical load which nearly constant.
  - b) The electrical load above the base load which fluctuates from hour to hour. c) peak

7. a) Bb)  $\mu$ c) Hd) B =  $\mu \cdot H$ e) B-H curve or Hysteresis curvef) x-axis: Hy-axis:8. 115·kV230·kV345·kV500·kV765·kV4 of these9. Multiple wires per phase

- 10. Air (and distance) 11. ACSR, Aluminum Conductor, Steel Reinforced
- 12 The transmission line VARS = 0. It doesn' t change the pf.  $V_S = V_R$  if R = 0

### Open-book part

- 1. a)  $14.4 \cdot \Omega$  b)  $1.8 \cdot kVA$  ;c)  $(1.44 1.08 \cdot j) \cdot kVA$  d) 0.8 e) i) leading, because the load is capacitive f) Add an inductor in parallel with load 79.6 · mH 2. a)  $I_A \log V_{AB}$  by  $10^\circ$ b)  $I_A \log V_{AB}$ c) No change
- c)  $(10+4.j) \Omega$  d)  $91.5.\mu F$
- Exam 2, Problem 2 89%
- ECE 3600 Exam 1 Fall 08 p2