


(31 pts) Questions This part of the exam is **Closed book, Closed notes, No Calculator.**

**Write Legibly!** If I can't read what you've written or your answer is ambiguous, I'll assume you don't know.

1. What is the most energy-efficient type of common power plant? Hint: It's also one of the oldest.
2. Name 3 sources of electrical power for the grid which do not produce greenhouse gasses by normal operation.
3. Describe how a combined-cycle, natural gas, power plant works and achieves its high efficiency?
4. Express power lost using the following:  $P_{in}$  and  $\eta$
5. Why do transformers have a maximum voltage rating?  
That is, what bad thing are you trying to limit by limiting the voltage?
6. Why do transformers have a maximum current rating?
7. When accounting for the non-ideal characteristics of a power transformer, which of the following is the most important (least often neglected)?

magnetization reactance      core losses      winding losses      leakage reactance

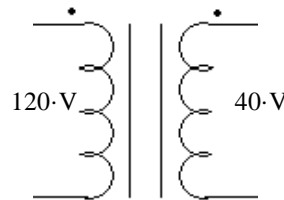
8. You have a 120/40-V, 480-VA transformer.  
Can you use this transformer to transform 120 V to 80 V? If yes, show the connections and compute the new VA rating.



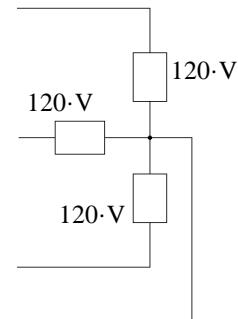9. a) How many single-phase transformers are required to transform 3-phase power. Give the minimum number.  
b) Show how these single-phase transformers might be connected between the source (shown at left below) and a load (shown at right). Do not create an unbalanced load for the source.

480V, 3-phase

- A \_\_\_\_\_  
B \_\_\_\_\_  
C \_\_\_\_\_  
N \_\_\_\_\_



- c) What is the required turns ratio of the transformers you showed above. Since you don't have a calculator, you may show a mathematical expression instead of a number.
10. a) When analyzing a power system using the per-unit system, which, if any, of the bases should be constant throughout the system?  
b) For those bases that change from place to place throughout the system, which is the primary one that changes and what type of part causes the changes?

**The following problems were handed out to the student after finishing the closed-book part.**

This part of the exam is **open book, open notes.** You **MUST** show work to get credit. Show the correct units for each value. Assume voltage and current values are RMS and  $f := 60\text{-Hz}$ . Assume normal abc sequence and balanced conditions for all 3 $\phi$ .

1. (20 pts) A single-phase, 240-V source is connected to two loads. The source provides 2400W and 12A. Load 1 consumes 1500W at a power factor of 0.6.

In order to find the following, you may have to make some assumptions. If you do, be sure to clearly state your assumption in such a way that I can tell that you know what the other assumption might be.

- a) Find the complex power (both P and Q) consumed by load 2.
- b) Load 2 can be modeled as 2 parts. Draw a model and find the values of the parts.

