



**The following problems were handed out to the student after finishing the closed-book part.**

1. (20 pts) A transformer is rated at 240V / 60V, 360VA.

The following measurements are taken in a standard short-circuit test:  $V = 20\text{-V}$   $P = 12\text{-W}$

The following measurements are taken in a standard open-circuit test:  $I = 500\text{-mA}$   $P = 24\text{-W}$

Draw the standard non-ideal transformer model and find the values or reactances of all the components. You may neglect  $R_m$  and  $X_m$  when finding the other two components.

2. (20 pts) The parameters of a 4:1 step-down transformer are shown below.

The transformer is loaded with  $Z_L := (5 + 3j)\cdot\Omega$  and the secondary current is  $I_2 := 4.8\text{-A}$


$R_m := 2\cdot k\Omega$   $R_s := 4\cdot\Omega$   $X_m = ?$   $X_s := 8\cdot\Omega$

a) draw the model with the load connected. Label parts, voltages and currents as needed for the rest of the problem.

b) Find the primary, source voltage. Magnitude only.  $|V_S| = ?$

c) The primary, source voltage provides VARs  $Q_S := 140\text{-VAR}$  Find  $X_m$

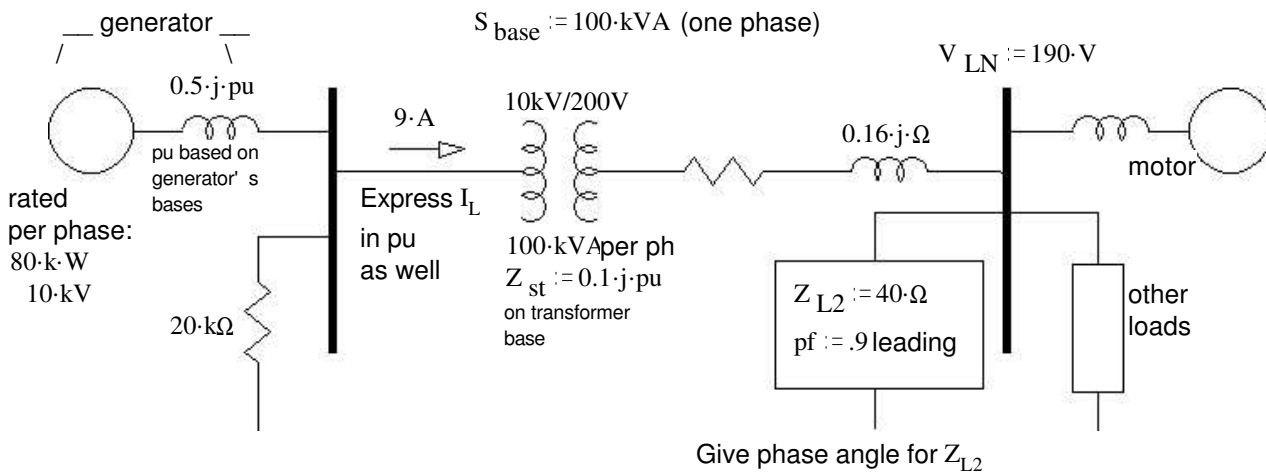3. (18 pts) A one-line, per-phase diagram is shown below. Using the  $S_{base}$  given, draw a per-phase, per-unit diagram. Include pu values for **all** the values given in the drawing below. All voltages are line-to-neutral.



4. (20 pts) You have a 3-phase, Y-connected, synchronous generator with synchronous reactances of  $2\Omega$ /phase. The magnitude of the back EMF is 380V, the magnitude of the line current is 80A and it lags the phase voltage by  $30^\circ$ .

$X_s := 2\cdot\Omega$   $E_A := 380\text{-V}$   $I_L := 80\text{-A}$   $\theta := 30\text{-deg}$  with  $I_L$  lagging  $V_\phi$



a) Draw a phasor diagram of this situation.

b) Find the line voltage this generator is connected to, magnitude only. Hint: It's a geometry problem.

c) Find the power angle,  $\delta$ .

**Answers**

**Closed-book part**

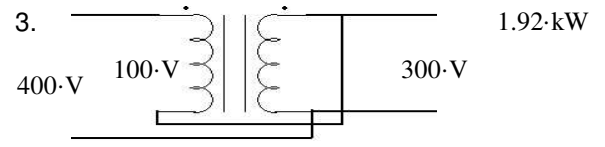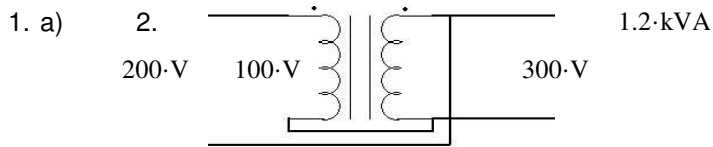

4. yes  $\Delta$ , to reduce third-harmonic currents.

5. Core losses      Nonlinearities, esp. in the currents      Requires more windings so that the core flux can be less  
 Sets voltage limits      3rd harmonic currents      Requires larger, heavier cores      3 of these

6. a)  $S_{base}$        $V_{base}$        $I_{base}$        $Z_{base}$       b)  $S_{base}$       c)  $V_{base}$       Transformers

d)  $I_{base} = \frac{S_{base}}{V_{base}}$        $Z_{base} = \frac{V_{base}}{I_{base}}$

7.  $0^\circ < \delta < 90^\circ$       8.  $\frac{3600\text{-rpm}}{\text{any\_integer}}$       3600-rpm      1800-rpm      1200-rpm      900-rpm      720-rpm      etc..

**Open-book part**

