

ECE 3600 Exam 2 given: Fall 11

(The space between problems has been removed.)

Write Legibly! This part of the exam is **Closed book, Closed notes, No Calculator.**

(22 pts) Questions If I can't read what you've written or your answer is ambiguous, I'll assume you don't know.

1. The voltage regulation of a transformer is often specified as %VR. Of the four values given below, circle the best %VR that could be a specification for a transformer.


a) 2%

b) 50%


c) 98%

d) 120%

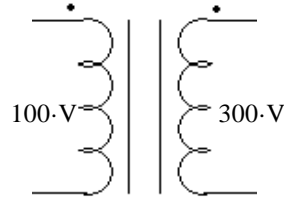2. You have a 100/300-V, 600-VA transformer. Can you use this transformer to transform 200 V to 300 V? If yes, show the connections and compute the new VA rating.



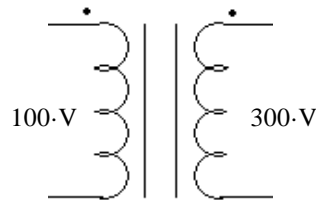3. You have a 100/300-V, 600-VA transformer.
- a) Can you use this transformer to transform 320 V to 240 V? If yes, show the connections and compute the maximum power that can be transformed at these voltages.



4. Is it desirable for at least one side of a 3-phase transformer to be wired in a certain way? yes no
If yes, which way and why? circle one

5. The B-H curve causes a number of problems. Name at least 3.

6. a) List the bases of a per-unit system.

- b) When analyzing a power system, which, if any, of these bases should be constant throughout the system?

- c) For those bases that change from place to place throughout the system, which is the primary one that changes and what type of part causes the changes?

- d) Show how to find the remaining bases from those listed in parts b) and c).

ECE 3600 Exam #2 Fall 2011

Arn Stolp

Scores:

Questions _____ / 22 pts

7. The power angle of a synchronous generator is limited to what range of values?

Prob 1 _____ / 20 pts

Prob 2 _____ / 20 pts

Prob 3 _____ / 18 pts

8. a) List at least 3 different synchronous motor speeds in the US, in rpm.

Prob 4 / 20 pts

Total _____ / 100 pts

The following problems were handed out to the student after finishing the closed-book part.

ECE 3600 Exam 2 Fall 11 p2

1. (20 pts) A transformer is rated at 240V / 60V, 360VA.

The following measurements are taken in a standard short-circuit test: $V = 20\text{-V}$ $P = 12\text{-W}$

The following measurements are taken in a standard open-circuit test: $I = 500\text{-mA}$ $P = 24\text{-W}$

Draw the standard non-ideal transformer model and find the values or reactances of all the components. You may neglect R_m and X_m when finding the other two components.

2. (20 pts) The parameters of a 4:1 step-down transformer are shown below.

The transformer is loaded with $Z_L := (5 + 3j)\Omega$ and the secondary current is $I_2 := 4.8\text{-A}$


$$R_m := 2\text{-k}\Omega \quad R_s := 4\text{-}\Omega \quad X_m = ? \quad X_s := 8\text{-}\Omega$$

a) draw the model with the load connected. Label parts, voltages and currents as needed for the rest of the problem.

b) Find the primary, source voltage. Magnitude only. $|V_S| = ?$

c) The primary, source voltage provides VARs $Q_S := 140\text{-VAR}$ Find X_m

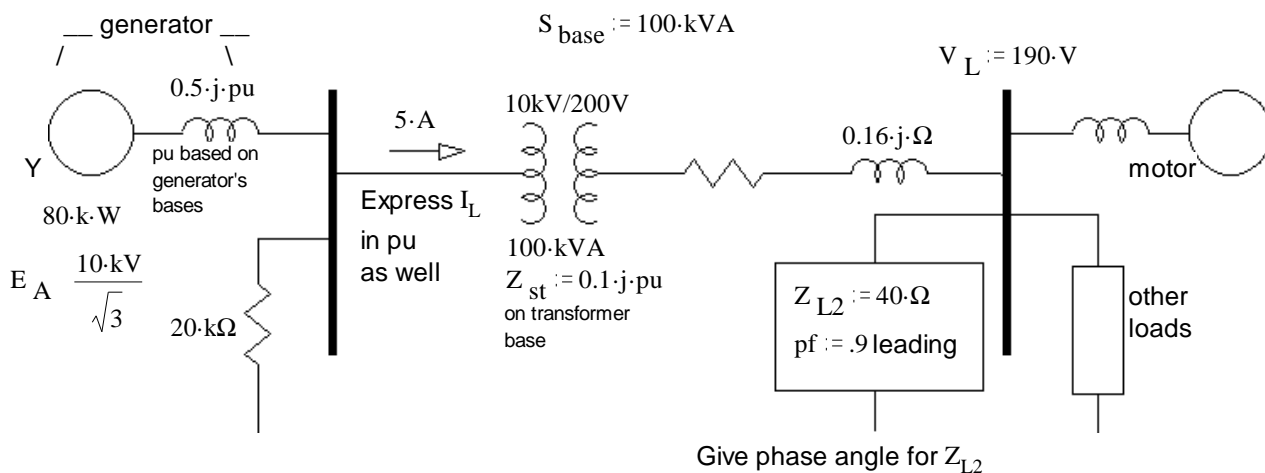3. (18 pts) A one-line, per-phase diagram is shown below. Using the S_{base} given, draw a per-phase, per-unit diagram. Include pu values for all the values given in the drawing below. E_A voltages are line-to-neutral.



4. (20 pts) You have a 3-phase, Y-connected, synchronous generator with synchronous reactances of $2\Omega/\text{phase}$. The magnitude of the back EMF is 380V, the magnitude of the line current is 80A and it lags the phase voltage by 30° .

$$X_s := 2\text{-}\Omega \quad E_A := 380\text{-V} \quad I_L := 80\text{-A} \quad \theta := 30\text{-deg} \quad \text{with } I_L \text{ lagging } V_\phi$$

a) Draw a phasor diagram of this situation.




b) Find the line voltage this generator is connected to, magnitude only. Hint: It's a geometry problem.

c) Find the power angle, δ .





ECE 3600 Exam 2 Fall 11 p2

Answers

Closed-book part

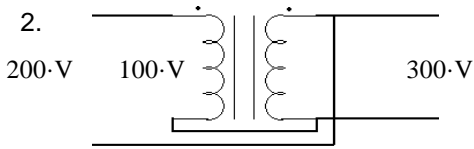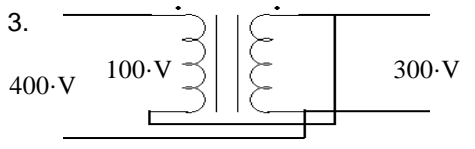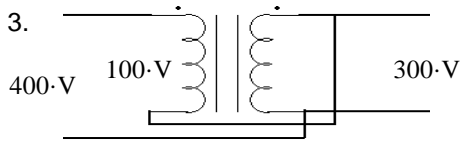1. a)  1.2·kVA
2.  1.92·kW
3.  1.92·kW
4. yes Δ , to reduce third-harmonic currents.
5. Core losses Nonlinearities, esp. in the currents Requires more windings so that the core flux can be less
Sets voltage limits 3rd harmonic currents Requires larger, heavier cores 3 of these
6. a) S_{base} V_{base} I_{base} Z_{base} b) S_{base} c) V_{base} Transformers
- d) $I_{\text{base}} = \frac{S_{\text{base}}}{\sqrt{3} \cdot V_{\text{base}}}$ $Z_{\text{base}} = \frac{V_{\text{base}}^2}{S_{\text{base}}}$
7. $0^\circ < \delta < 90^\circ$ 8. $\frac{3600\text{-rpm}}{\text{any_integer}}$ 3600·rpm 1800·rpm 1200·rpm 900·rpm 720·rpm etc..

Open-book part

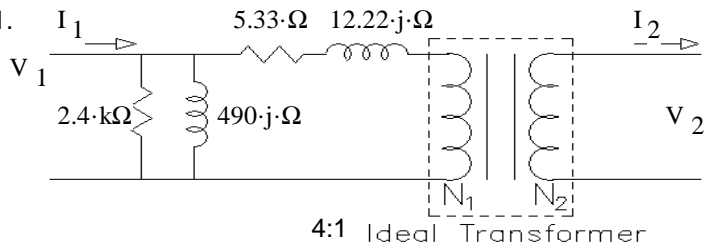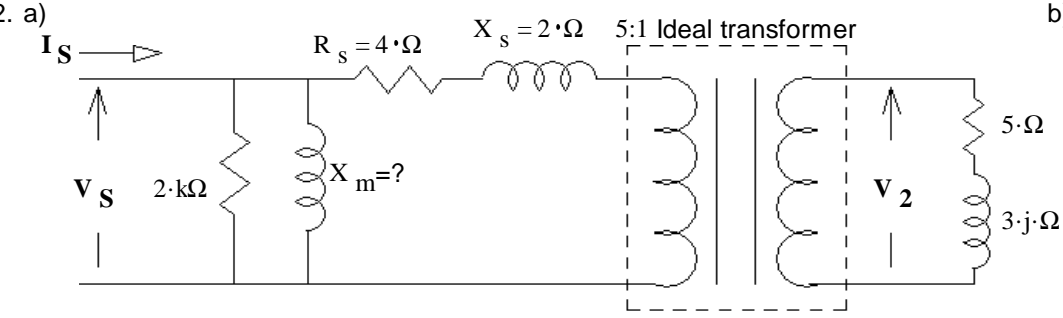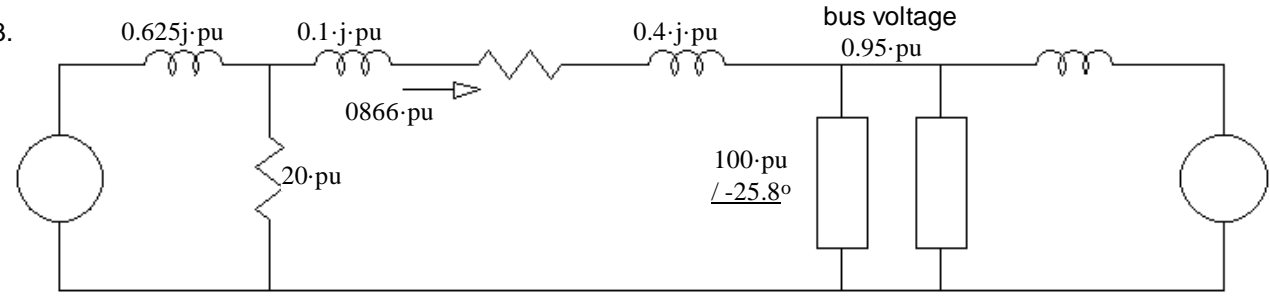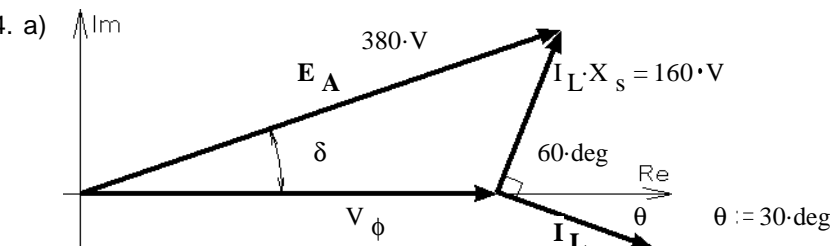1.  4:1 Ideal Transformer
2. a)  b) 121.1·V c) 247·Ω
3. 
4. a)  b) 474.3·V c) 21.39·deg