


ECE 3600 Final, given: Fall 2019

Write Legibly! If I can't read what you've written or your answer is ambiguous, I'll assume you don't know.

(70 pts) **Questions** This part of the exam is **Closed book, Closed notes, No Calculator**.

Wrong answers may cost up to 3 times what a right answer is worth. Blanks cost the same as the right answer was worth.

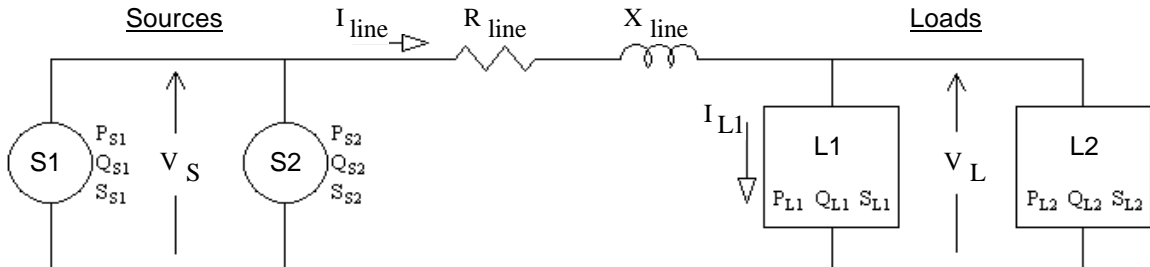1. Consider the single-phase system below. There are two sources, labeled S1 and S2 and two loads, labeled L1 and L2. All the variables shown or referred to in the questions are scalar or magnitudes of complex numbers. The same should be true of your answers.



Example) Is there a simple relationship between all the real powers above?

NO YES

If yes, express that relationship in a mathematical way.

$$P_{S1} + P_{S2} = P_{Rline} + P_{L1} + P_{L2} \quad \text{OR} \quad P_{S1} + P_{S2} = I_{line}^2 \cdot R_{line} + P_{L1} + P_{L2} \quad (\text{Only one answer is necessary})$$

Note: You are not being asked for FORMULAs. You are being asked to express basic concepts in a mathematical way.

a) Is there a simple relationship between all the reactive powers above? NO YES

If yes, express that relationship in a mathematical way.

b) Is there a simple relationship between all the apparent powers above? NO YES

If yes, express that relationship in a mathematical way.

c) Is there a simple relationship between all the power factors above? NO YES

If yes, express that relationship in a mathematical way.


d) Express I_{line} in terms of source real and/or reactive powers and V_S . (Please remember that these variables are all scalar or magnitudes.)

e) Express I_{line} in terms of load real and/or reactive powers and V_L .

f) Express I_{L1} in terms of load real and/or reactive powers and V_L .

g) Express the efficiency in terms of real and/or reactive powers.

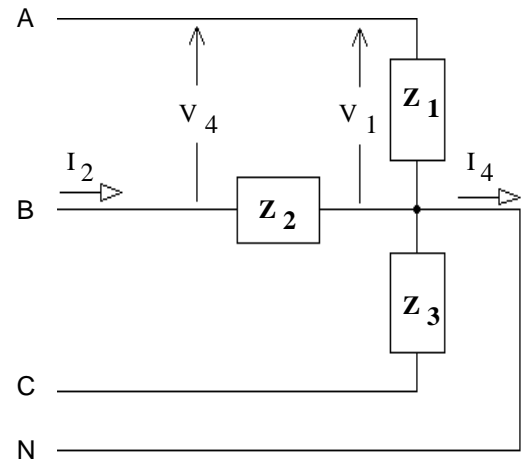2. Consider the balanced three-phase load shown. Except for the Z 's, all the variables shown or referred to in the questions are scalar or magnitudes of complex numbers. The same should be true of your answers. Where possible, express answers mathematically.



a) If this is a balanced load, what can be said about the Z 's?

b) What is the value V_4 ? (may be expressed in terms of V_1)

c) What is the value I_4 ? (may be expressed in terms of I_2)

d) Is one of the voltages shown also known as the line voltage? NO YES
If yes, which one?


e) Is one of the currents shown also known as the line current? NO YES
If yes, which one?

f) Is this load connected Y or Δ ?

g) Could we find an equivalent load connected the other way (Δ if now Y, or Y if now Δ)? NO YES
If yes what Z values should be used? Finish one of these two expressions:

$$Z_{\Delta} = \quad \text{OR} \quad Z_Y =$$

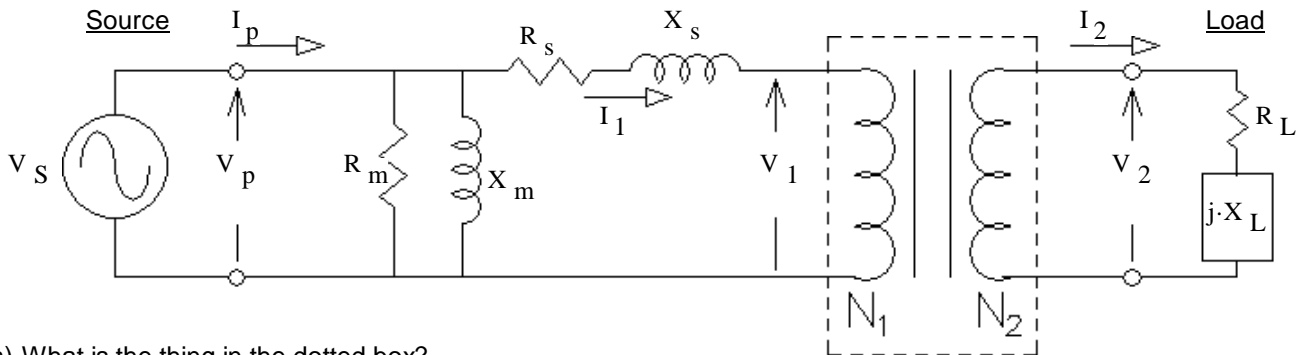3. A source and load are connected to a model of a non-ideal transformer as shown. All the variables shown or referred to in the questions are scalar or magnitudes of complex numbers. The same should be true of your answers. Where possible, express answers mathematically.




a) What is the thing in the dotted box?

b) What is the relationship between V_1 and V_2 ?


c) What is the relationship between I_1 and I_2 ?

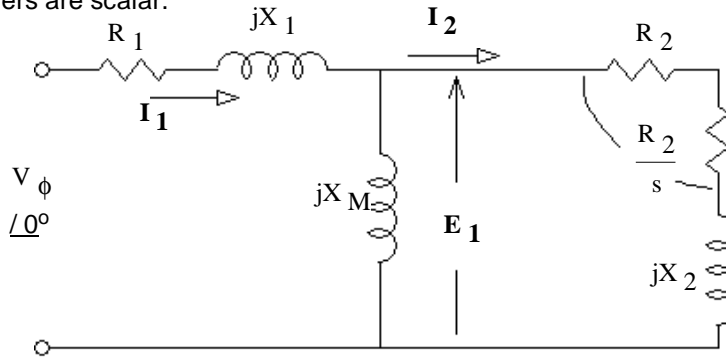5. The following questions pertain to a 3-phase induction motor. A model of one phase is shown. Bold variables are complex, all others are scalar.



a) What is the variable "s" called?

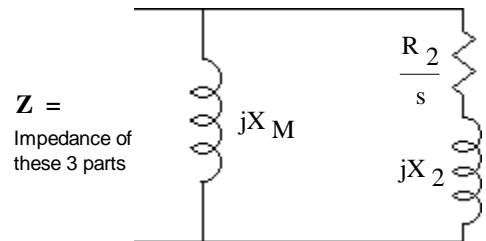b) A partial schematic is shown at right. Find (write) an expression for the combined impedance, Z .



c) Write an expression for E_1 in terms of V_ϕ and the impedances given or found above.

d) Write an expression for $|I_2|$ in terms of E_1 and the impedances given or found above.

e) Express the stator-copper-loss of this 3 ϕ motor in terms given or found above.

f) Express the rotor-copper-loss in terms given or found above.

g) Express the air-gap power in terms given or found above.

h) Express the power converted to mechanical power in terms given or found above.

Problems Closed Book, Closed notes except for those given in class for Exam 1, 2, and final, Calculators OK, Show all work to receive credit. Circle answers, show units, and round off reasonably

1. (32 pts) A 345 kV transmission line has the following length and line parameters. $S := \text{siemens}$
 $len := 150 \cdot \text{km}$ $r := 0.08 \cdot \frac{\Omega}{\text{km}}$ $x := 0.76 \cdot \frac{\Omega}{\text{km}}$ $g := 0 \cdot \frac{S}{\text{km}}$ $y := 5 \cdot 10^{-6} \cdot \frac{S}{\text{km}}$

a) Choose the most appropriate model for this transmission line and draw it, including the impedance and/or admittance value(s). Add a 3ϕ load at the receiving end of the transmission line.

The line voltage at the **source** is 345kV. The line current from the **source** (I_S) is 250A and it **leads** the line-to-neutral voltage by 15° .

b) Find the line current in your model, I_{Line} (not I_S) in a complex-number form. $I_{\text{Line}} = ?$

c) Find the load phase voltage, V_R , magnitude and phase. $V_R = ?$

d) What is the line voltage at the load (magnitude)?

e) What is the "power angle" (δ)?

1, continued f) Find the impedance of one phase of the load, assuming Y-connected.

g) Find the power consumed by the entire load.

h) Find the power factor of the load.

2. (36 pts) A 1.5-hp, separately excited dc motor runs at 60% overall efficiency (includes power needed for the field) when operated at full load. Both the armature and field are hooked to a single 200 V source. The rotational losses are proportional to the motor speed. Other important information is given below.

$$\eta := 60\% \quad V_T := 200 \cdot V \quad n_{fL} := 900 \cdot \text{rpm} \quad R_A := 3 \cdot \Omega \quad R_F := 250 \cdot \Omega \quad 1 \cdot \text{hp} = 745.7 \cdot W$$

a) Find the power converted from electrical to mechanical, $P_{\text{conv}} = ?$

b) Find the rotational losses, $P_{\text{rot}} = ?$

2, continued c) Find the no-load armature current. Show the algebra needed to find I_A from the basic equations.

The rotational losses are proportional to the motor speed.

Hint 1: This also means that the rotational losses are proportional to E_A , like this:

$$P_{\text{rot}2} = P_{\text{rot}1} \cdot \frac{E_{A2}}{E_{A1}}$$

Hint 2: This turns out to be amazingly easy to calculate, no quadratic required.

d) The full-load speed is given above as n_{fl} . Find the no-load shaft speed.

e) The mechanical load on the shaft is reduced so $P_{\text{out}} := 1 \cdot \text{hp}$. Find the new shaft speed.

Show the algebra needed to find E_A from the basic equations. (Yeah, algebra is a prerequisite for Engineering.)

Hints: This is NOT trivial to calculate, algebra and quadratic required.

Remember $P_{\text{conv}} := P_{\text{out}} + P_{\text{rot}}$ and, P_{rot} is dependent on speed as described above.

Note: Check your answer, it's easy to do.

3. (22 pts) A 1/2-hp, 120-V, 60-Hz, single-phase, capacitor-run, induction motor has two windings set 90° apart in the motor housing. The windings are NOT the same. At Startup, winding 1 draws 6 A at 30°lag. Winding 2 in series with an 80-μF capacitor draws 4.5 A at 35°lead.

$$V_T := 120 \cdot V \quad \mathbf{I}_1 := 6 \cdot A \cdot e^{-j \cdot 30 \cdot \text{deg}} \quad \mathbf{I}_2 := 4.5 \cdot A \cdot e^{j \cdot 35 \cdot \text{deg}} \quad C := 80 \cdot \mu\text{F} \text{ in series with win}$$

- a) Find the impedance of winding 1 and winding 2 without the capacitor. Find both in rectangular form.

- b) If the capacitor were disconnected from winding 2 and placed in series with winding 1 instead, find the new phase angle difference and the new current magnitudes. Did anything improve?

- c) There will be one other major change in the motor startup with this new configuration. We didn't directly discuss this in class, but you can figure it out if you understand how the startup works. What will be different?

Answers Questions

1. a) $Q_{S1} + Q_{S2} = I_{line}^2 \cdot X_{line} + Q_{L1} + Q_{L2}$ b) NO c) NO d) $I_{line} = \frac{\sqrt{(P_{S1} + P_{S2})^2 + (Q_{S1} + Q_{S2})^2}}{V_S}$

e) $I_{line} = \frac{\sqrt{(P_{L1} + P_{L2})^2 + (Q_{L1} + Q_{L2})^2}}{V_L}$ f) $I_{L1} = \frac{\sqrt{(P_{L1})^2 + (Q_{L1})^2}}{V_L}$ g) $\eta = \frac{P_{L1} + P_{L2}}{P_{S1} + P_{S2}}$
OR $\eta = \frac{P_{L1} + P_{L2}}{P_{L1} + P_{L2} + P_{Rline}}$


2. a) $Z_1 = Z_2 = Z_3$ b) $\sqrt{3} \cdot V_1$ c) 0 d) V_4 e) I_2 f) Y

g) $Z_{\Delta} = 3 \cdot Z_Y$ OR $3 \cdot Z_1$ either answer $Z_Y = \frac{Z_{\Delta}}{3}$


3. a) Ideal transformer b) $\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$ d) $R_{eq} = R_L \cdot \left(\frac{N_1}{N_2}\right)^2$ $X_{eq} = X_L \cdot \left(\frac{N_1}{N_2}\right)^2$

e) $I_1 = \frac{V_p}{\sqrt{\left[R_s + R_L \cdot \left(\frac{N_1}{N_2}\right)^2\right]^2 + \left[X_s + X_L \cdot \left(\frac{N_1}{N_2}\right)^2\right]^2}}$ OR $\frac{V_p}{\sqrt{(R_s + R_{eq})^2 + (X_s + X_{eq})^2}}$

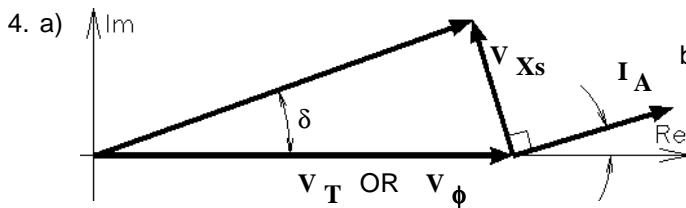f) $P_S = \frac{V_p^2}{R_m} + I_1^2 \cdot (R_s + R_{eq})$ g) $Q_S = \frac{V_p^2}{X_m} + I_1^2 \cdot (X_s + X_{eq})$ h) $I_p = \frac{\sqrt{P_S^2 + Q_S^2}}{V_p}$ i) $\eta = \frac{I_1^2 \cdot R_{eq}}{P_S}$



b) generator c) - d)

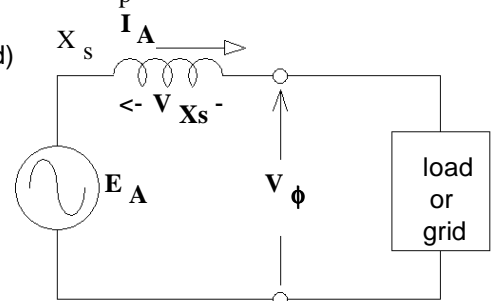

OR
e) $E_A = V_{\phi} + V_{Xs} = V_{\phi} + I_A \cdot j \cdot X_s$

5. a) The slip

b) $Z = \frac{1}{\frac{1}{j \cdot X_m} + \frac{1}{\left(\frac{R_2}{s} + j \cdot X_2\right)}}$ c) $E_1 = V_{\phi} \cdot \frac{Z}{R_1 + j \cdot X_1 + Z}$


d) $|I_2| = \frac{|E_1|}{\sqrt{\left(\frac{R_2}{s}\right)^2 + X_2^2}}$

e) $P_{SCL} = 3 \cdot [(|I_1|)^2 \cdot R_1]$ f) $P_{RCL} = 3 \cdot [(|I_2|)^2 \cdot R_2]$

g) $P_{AG} = 3 \cdot [(|I_2|)^2 \cdot \frac{R_2}{s}]$

h) $P_{conv} = (1 - s) \cdot P_{AG} = P_{AG} - P_{RCL}$

Problems

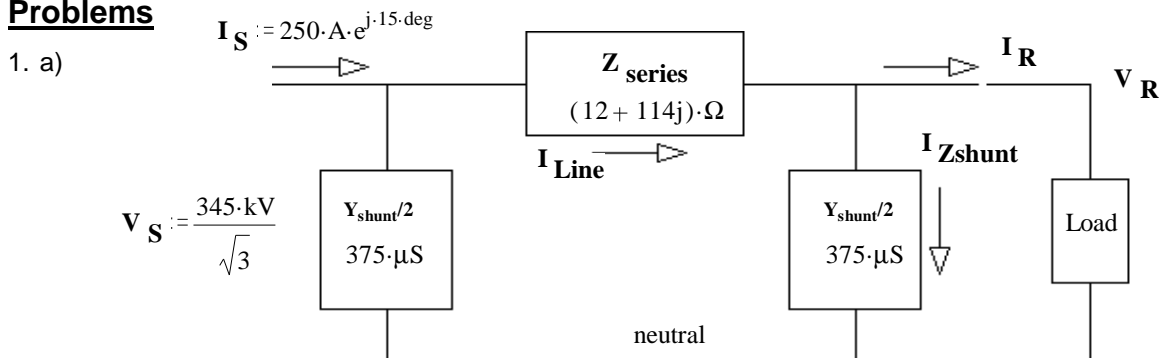

b) $241.7 \cdot A \angle -2.369^\circ$

c) $197.1 \cdot kV \angle -7.995^\circ$

d) $341.3 \cdot kV$

e) 7.995°

f) $(785.1 + 163.9 \cdot j) \Omega$
 $802.0 \cdot \Omega \angle 11.79^\circ$

g) $142.2 \cdot MW$

h) 0.979

2. a) $1.486 \cdot kW$ b) $367.9 \cdot W$ c) $2.109 \cdot A$ d) $999.3 \cdot \text{rpm}$ OR $104.6 \cdot \frac{\text{rad}}{\text{sec}}$ e) $935.6 \cdot \text{rpm}$ OR $97.98 \cdot \frac{\text{rad}}{\text{sec}}$

3. a) $17.32 + 10 \cdot j \Omega$ $21.84 + 17.86 \cdot j \Omega$ b) Angle difference is much closer to the ideal of 90° .

c) It will start spinning in the opposite direction

Currents are both less and closer in value