


# ECE 3600 Final Exam Information

You may write more on this sheet. You may also use Exam 1, 2 & 3 Information sheets

## Transmission Lines

		Units			Units
line length:	len, d	m or km		stick to the same unit length for all parameters miles may also be used	
Resistance per unit length:	r	$\frac{\Omega}{m}$ or $\frac{\Omega}{km}$			
Inductance per unit length:	l	$\frac{H}{m}$ or $\frac{H}{km}$	OR	Inductive reactance per unit length:	x $\frac{\Omega}{m}$ or $\frac{\Omega}{km}$
Capacitance per unit length:	c	$\frac{F}{m}$ or $\frac{F}{km}$	OR	Admittance per unit length:	y $\frac{S}{m}$ or $\frac{S}{km}$
Conductance to ground:	g	$\frac{S}{m}$ or $\frac{S}{km}$		Common assumption:	$g = 0 \cdot \frac{S}{km}$

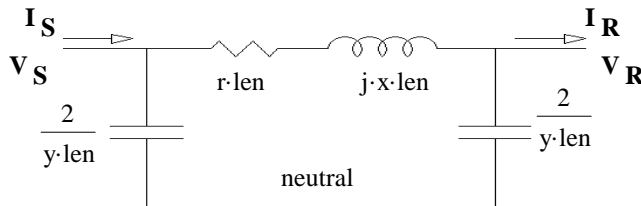Medium-length Lines:  
80 - 240 km  
(50 to 150 miles)




## Power Flow

Admittance Matrix

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

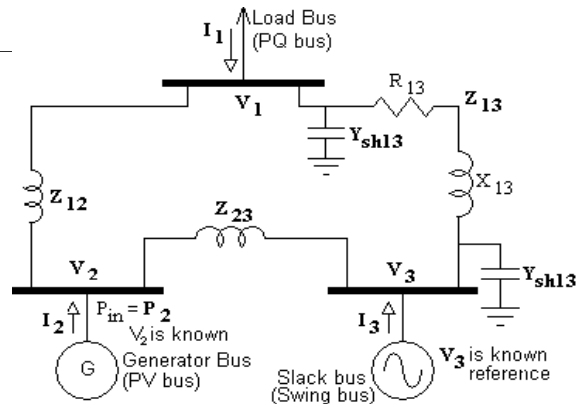$Y_{nn} = \sum$  of all admittances connected to bus n  
 $Y_{mn} = -$  admittance connected between buses n & m  
 $m \neq n$



## Faults

Symmetrical faults Just analyze on a normal per-phase basis

Unsymmetrical Faults

$$\begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \cdot \begin{bmatrix} V_{A0} \\ V_{A1} \\ V_{A2} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 240^\circ & 120^\circ \\ 1 & 120^\circ & 240^\circ \end{bmatrix} \cdot \begin{bmatrix} V_{A0} \\ V_{A1} \\ V_{A2} \end{bmatrix}$$

$$\begin{bmatrix} V_{A0} \\ V_{A1} \\ V_{A2} \end{bmatrix} = \frac{1}{3} \cdot \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \cdot \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \frac{1}{3} \cdot \begin{bmatrix} 1 & 1 & 1 \\ 1 & 120^\circ & 240^\circ \\ 1 & 240^\circ & 120^\circ \end{bmatrix} \cdot \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix}$$

Pre-Fault Setup Find pre-fault  $V_T$  and  $I_{gen}$ .  $E''_A = V_T - I_{gen} \cdot Z''_g$

Circuits are on the back of this sheet

It can be helpful to find  $E_{ThA}$  and all the Thevenin impedances


Line to line (LL),  
ground not involved  
 $Z_f$  may be 0

Double line to  
ground (DLG)  
 $Z_f$  may be 0

Single line to  
ground (SLG)  
 $Z_f$  may be 0

Double line open  
 $V_A = 0$

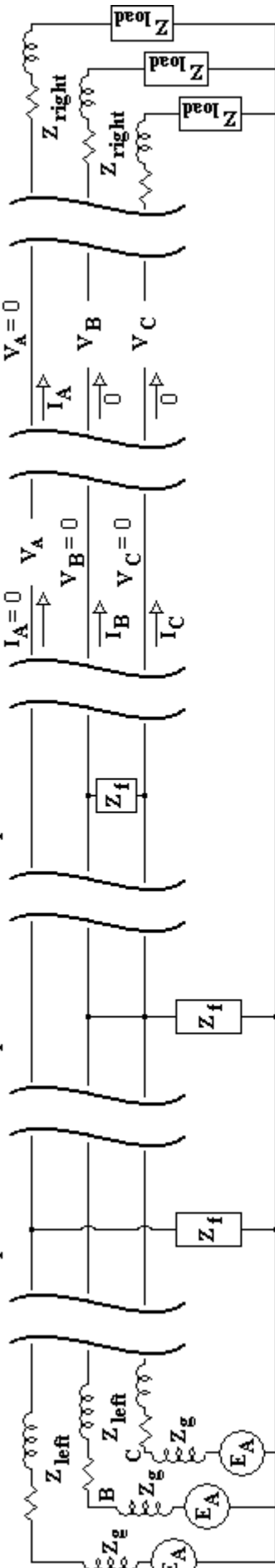Single line open  
 $I_A = 0$   
 $V_B = 0$   
 $V_C = 0$



$$I_C = I_{A1} j\sqrt{3} = -I_B$$


$$I_{A0} = I_{A1} = I_{A2}$$

$$V_A = 3V_{A1}$$

$$I_{A0} = 0$$
  

$$V_{A0} = 0$$
  
 NOT connected to anything

$$I_A = 3I_{A1}$$

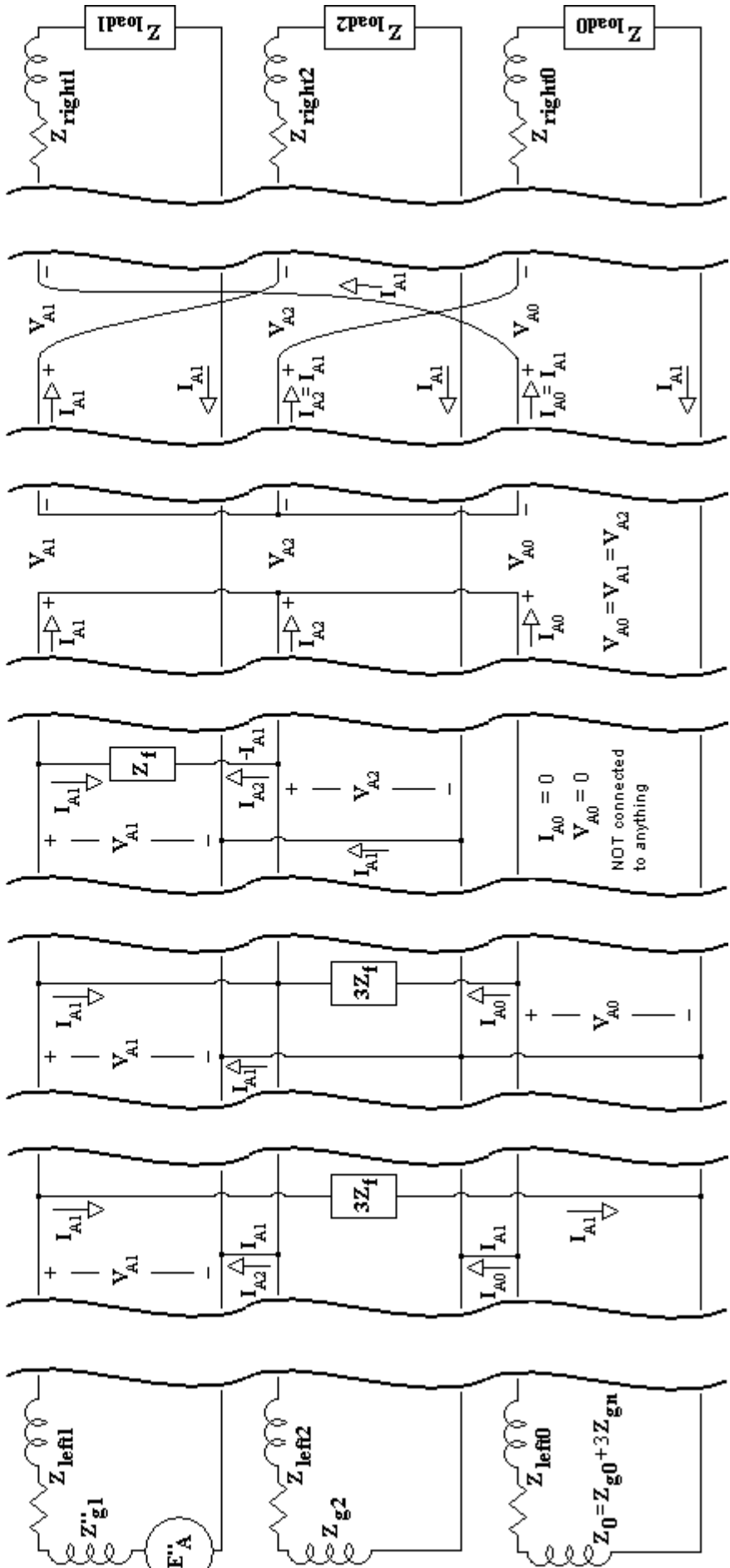

Positive sequence

Negative sequence

Zero sequence