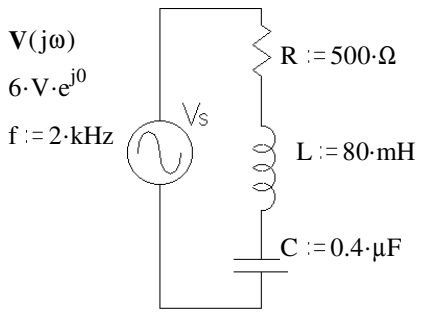


ECE 3600 Phasor Examples

A. Stolp
9/3/08
rev

Ex 1. Find V_R , V_L , and V_C in polar phasor form. $f := 2 \cdot \text{kHz}$



$$\omega := 2 \cdot \pi \cdot f \quad \omega = 1.257 \cdot 10^4 \frac{\text{rad}}{\text{sec}}$$

$$Z_L := j \cdot \omega \cdot L \quad Z_L = 1.005j \cdot \text{k}\Omega$$


$$Z_C := \frac{1}{j \cdot \omega \cdot C} \quad Z_C = -0.199j \cdot \text{k}\Omega$$

$$Z_{eq} := R + j \cdot \omega \cdot L + \frac{1}{j \cdot \omega \cdot C} \quad Z_{eq} = 500 + 806.366j \cdot \Omega$$

$$\sqrt{500^2 + 806^2} = 948.491$$

$$\text{atan}\left(\frac{806}{500}\right) = 58.187 \cdot \text{deg}$$

$$Z_{eq} = 948.5 \Omega / 58.2^\circ$$

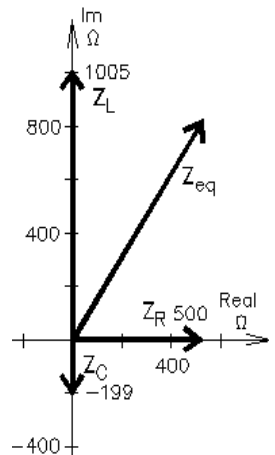

find the current: $I := \frac{6 \cdot V \cdot e^{j0}}{Z_{eq}}$

magnitude: $\frac{6 \cdot V}{948.5 \Omega} = 6.326 \cdot \text{mA}$

angle: $0 \cdot \text{deg} - 58.2 \cdot \text{deg} = -58.2 \cdot \text{deg}$

$$I = 6.326 \text{mA} / -58.2^\circ$$

find the magnitude

find the angle

$$V_R := I \cdot R \quad 6.326 \cdot \text{mA} \cdot 500 \cdot \Omega = 3.163 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + 0 \cdot \text{deg} = -58.2 \cdot \text{deg}$$

$$V_R = 3.163 \text{V} / -58.2^\circ$$

$$V_L := I \cdot Z_L \quad 6.326 \cdot \text{mA} \cdot 1005 \cdot \Omega = 6.358 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + 90 \cdot \text{deg} = 31.8 \cdot \text{deg}$$

$$V_L = 6.358 \text{V} / 31.8^\circ$$

$$V_C := I \cdot Z_C \quad 6.326 \cdot \text{mA} \cdot (-199) \cdot \Omega = -1.259 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + (90) \cdot \text{deg} = 31.8 \cdot \text{deg}$$

$$V_C = -1.259 \text{V} / 31.8^\circ$$

OR: $6.326 \cdot \text{mA} \cdot (199) \cdot \Omega = 1.259 \cdot \text{V}$

$$-58.2 \cdot \text{deg} + (-90) \cdot \text{deg} = -148.2 \cdot \text{deg}$$

$$V_C = 1.259 \text{V} / -148.2^\circ$$

OR, you can also find these voltages directly, using a voltage divider. I.E. to find V_C directly:

$$V_C := \frac{\frac{1}{j \cdot \omega \cdot C}}{R + j \cdot \omega \cdot L + \frac{1}{j \cdot \omega \cdot C}} \cdot 6 \cdot \text{V} = \frac{1}{R \cdot (j \cdot \omega \cdot C) + j \cdot \omega \cdot L \cdot (j \cdot \omega \cdot C) + 1} \cdot 6 \cdot \text{V} = \frac{1}{R \cdot (j \cdot \omega \cdot C) - \omega^2 \cdot L \cdot C + 1} \cdot 6 \cdot \text{V}$$

$$= \frac{1}{(1 - \omega^2 \cdot L \cdot C) + j \cdot \omega \cdot R \cdot C} \cdot 6 \cdot \text{V} \quad (1 - \omega^2 \cdot L \cdot C) = -4.053 \quad j \cdot \omega \cdot R \cdot C = 2.513j$$

$$= \frac{6 \cdot \text{V}}{-4.053 + 2.513j} \cdot \frac{(-4.053 - 2.513j)}{(-4.053 - 2.513j)} = \frac{6 \cdot \text{V} \cdot (-4.053 - 2.513j)}{(-4.053)^2 + 2.513^2}$$

$$6 \cdot \text{V} \cdot (-4.053 - 2.513j) = -24.318 - 15.078j \cdot \text{V}$$

$$(-4.053)^2 + 2.513^2 = 22.742$$

$$= \left(\frac{-24.318}{22.742} - \frac{15.078j}{22.742} \right) \cdot \text{V} = -1.069 - 0.663j \cdot \text{V}$$


magnitude: $\sqrt{1.069^2 + 0.663^2} = 1.258$

angle: $\text{atan}\left(\frac{-0.663}{-1.069}\right) = 31.81 \cdot \text{deg}$

but this is actually in the third quadrant, so modify your calculator's results:


$$31.81 \cdot \text{deg} - 180 \cdot \text{deg} = -148.19 \cdot \text{deg}$$

$$= 1.258 \text{V} / -148.2^\circ$$

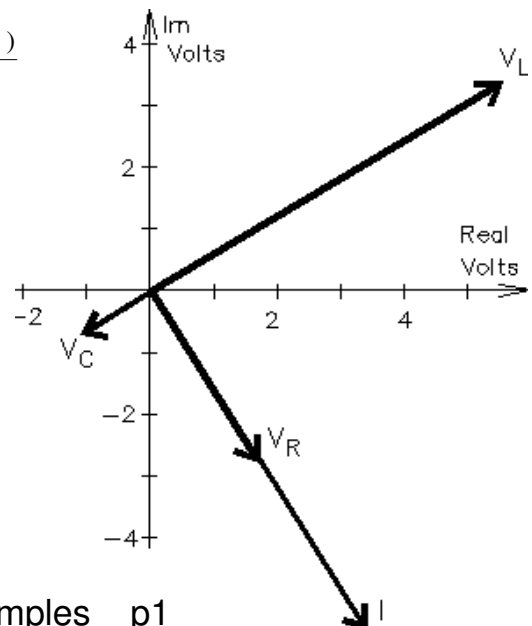

ECE 3600 Phasor Examples p2

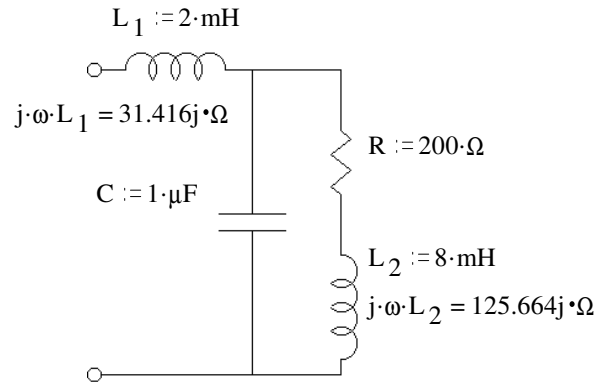Ex 2. a) Find Z_{eq} . $f := 2.5 \cdot \text{kHz}$ $\omega := 2 \cdot \pi \cdot f$ $\omega = 1.571 \cdot 10^4 \frac{\text{rad}}{\text{sec}}$



Left branch

$$Z_L := \frac{1}{j \cdot \omega \cdot C} \quad Z_L = -63.662j \cdot \Omega$$

Right branch

$$Z_R := j \cdot \omega \cdot L_2 + R \quad Z_R = 200 + 125.664j \cdot \Omega$$

$$Z_{eq} := j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + \frac{1}{\frac{1}{j \cdot \omega \cdot C}}} = j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C} = j \cdot \omega \cdot L_1 + \frac{R + j \cdot \omega \cdot L_2}{1 + j \cdot \omega \cdot C \cdot (R + j \cdot \omega \cdot L_2)}$$

$$= j \cdot \omega \cdot L_1 + \frac{R + j \cdot \omega \cdot L_2}{1 - \omega^2 \cdot C \cdot L_2 + j \cdot \omega \cdot C \cdot R}$$

Sometimes it's worth simplifying a little before putting in numbers.

$$Z_{eq} = 31.416j \cdot \Omega + \frac{(200 + 125.664j) \cdot \Omega}{-0.974 + 3.142j} \cdot \left(\frac{-0.974 - 3.142j}{-0.974 - 3.142j} \right) = 31.416j \cdot \Omega + \frac{(200 + 125.664j) \cdot (-0.974 - 3.142j)}{0.974^2 + 3.142^2}$$

$$= 31.416j \cdot \Omega + \frac{((200 \cdot (-0.974)) - 125.664 \cdot (-3.142)) + (125.664 \cdot (-0.974) - 200 \cdot 3.142) \cdot j}{0.974^2 + 3.142^2} \cdot \Omega$$

$$= 31.416j \cdot \Omega + \frac{(200.036288 - 750.796736j) \cdot \Omega}{10.82084} = 31.416j \cdot \Omega + 18.486 \cdot \Omega - 69.384j \cdot \Omega = 18.486 - 37.968j \cdot \Omega$$

$$\sqrt{18.49^2 + 37.97^2} = 42.233 \quad \text{atan}\left(\frac{-37.97}{18.49}\right) = -64.036 \cdot \text{deg} \quad Z_{eq} = 42.24 \Omega \angle -64.04^\circ$$

b) $V_{in} := 12 \cdot V \cdot e^{j20 \cdot \text{deg}}$ Find I_{L1}, V_C $I_{L1} := \frac{V_{in}}{Z_{eq}} = \frac{12 \cdot V}{42.24 \cdot \Omega} = 284.091 \cdot \text{mA}$ $20 \cdot \text{deg} - (-64.04) \cdot \text{deg} = 84.04 \cdot \text{deg}$

$$I_{L1} = 284 \text{mA} \angle 84.04^\circ = 284 \cdot \text{mA} \cdot e^{j84.04 \cdot \text{deg}} \quad I_{L1} = 29.485 + 282.569j \cdot \text{mA}$$

$$V_C := I_{L1} \cdot (18.486 - 69.384j) \cdot \Omega \quad 284 \cdot \text{mA} \cdot \sqrt{18.486^2 + 69.384^2} \cdot \Omega = 20.392 \cdot V$$

$$84.04 \cdot \text{deg} + \text{atan}\left(\frac{-69.384}{18.486}\right) = 8.959 \cdot \text{deg} \quad V_C = 20.4 V \angle 8.96^\circ$$

To find V_C directly:

$$V_C := \frac{\frac{1}{R + j \cdot \omega \cdot L_2}}{j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + \frac{1}{j \cdot \omega \cdot C}}} \cdot V_{in} = \frac{1}{j \cdot \omega \cdot L_1 \cdot \left(\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C \right) + 1} \cdot V_{in} = \frac{1}{\frac{j \cdot \omega \cdot L_1}{R + j \cdot \omega \cdot L_2} - \omega^2 \cdot L_1 \cdot C + 1} \cdot V_{in}$$

$$= \frac{1}{\frac{j \cdot \omega \cdot L_1}{R + j \cdot \omega \cdot L_2} - \omega^2 \cdot L_1 \cdot C + 1} \cdot V_{in} = \frac{1}{\frac{j \cdot \omega \cdot L_1 \cdot (R - j \cdot \omega \cdot L_2)}{R^2 + (\omega \cdot L_2)^2} - \omega^2 \cdot L_1 \cdot C + 1} \cdot V_{in}$$

$$= \frac{1}{\left[\frac{\omega^2 \cdot L_1 \cdot L_2}{R^2 + (\omega \cdot L_2)^2} - \omega^2 \cdot L_1 \cdot C + 1 \right] + j \cdot \frac{\omega \cdot L_1 \cdot R}{R^2 + (\omega \cdot L_2)^2}} \cdot V_{in} = \frac{12 \cdot V \cdot e^{j20 \cdot \text{deg}}}{0.58816 \cdot e^{j11.039 \cdot \text{deg}}} = \frac{12 \cdot V}{0.58816} \angle 20 - 11.039^\circ$$

$$= 20.4 V \angle 8.96^\circ \quad \text{Same}$$

ECE 3600 Phasor Examples p3

Ex 2. Continued Find I_{L2} .

$$Z_R := R + j \cdot \omega \cdot L_2$$

$$Z_R = 200 + 125.664j \cdot \Omega \quad \sqrt{200^2 + 125.664^2} = 236.202 \quad \text{atan}\left(\frac{125.664}{200}\right) = 32.142 \cdot \text{deg}$$

$$I_{L2} = \frac{20.4 \cdot V \cdot e^{j \cdot 8.96 \cdot \text{deg}}}{236.202 \cdot \Omega \cdot e^{j \cdot 32.142 \cdot \text{deg}}} = \frac{20.4 \cdot V}{236.202 \cdot \Omega} \quad / \underline{8.96 - 32.142}^\circ = 86.4 \text{mA} \quad \underline{-23.18}$$

Or, directly by Current divider: $I_{L2} := \frac{1}{j \cdot \omega \cdot C + \frac{1}{R + j \cdot \omega \cdot L_2}} \cdot I_{L1} = \frac{1}{j \cdot \omega \cdot C \cdot (R + j \cdot \omega \cdot L_2) + 1} \cdot I_{L1} = \frac{I_{L1}}{1 - \omega^2 \cdot C \cdot L_2 + j \cdot \omega \cdot C \cdot R}$

denominator: $\sqrt{(1 - \omega^2 \cdot C \cdot L_2)^2 + (\omega \cdot C \cdot R)^2} = 3.289 \quad \text{atan}\left(\frac{\omega \cdot C \cdot R}{1 - \omega^2 \cdot C \cdot L_2}\right) + 180 \cdot \text{deg} = 107.224 \cdot \text{deg}$

$$I_{L2} = \frac{284 \cdot \text{mA} \cdot e^{j \cdot 84.04 \cdot \text{deg}}}{3.289 \cdot e^{j \cdot 107.224 \cdot \text{deg}}} = \frac{284 \cdot \text{mA}}{3.289} \quad / \underline{84.04 - 107.224}^\circ = 86.4 \text{mA} \quad \underline{-23.18}$$

$$I_{L2} = 79.404 - 34.001j \cdot \text{mA}$$

How about I_C ? $I_C := \frac{V_C}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} = V_C \cdot j \cdot \omega \cdot C = 20.4 \text{V} / \underline{8.96}^\circ \cdot 0.015708 / \underline{90}^\circ \cdot \frac{1}{\Omega} = 320 \text{mA} / \underline{98.96}^\circ$

Or, directly by Current divider: $I_C := \frac{j \cdot \omega \cdot C}{j \cdot \omega \cdot C + \frac{1}{R + j \cdot \omega \cdot L_2}} \cdot I_{L1} = \frac{j \cdot \omega \cdot C \cdot (R + j \cdot \omega \cdot L_2)}{j \cdot \omega \cdot C \cdot (R + j \cdot \omega \cdot L_2) + 1} \cdot I_{L1} = \frac{-\omega^2 \cdot C \cdot L_2 + j \cdot \omega \cdot C \cdot R}{1 - \omega^2 \cdot C \cdot L_2 + j \cdot \omega \cdot C \cdot R} \cdot I_{L1}$

numerator: $\sqrt{(\omega^2 \cdot C \cdot L_2)^2 + (\omega \cdot C \cdot R)^2} = 3.71 \quad \text{atan}\left(\frac{\omega \cdot C \cdot R}{-\omega^2 \cdot C \cdot L_2}\right) + 180 \cdot \text{deg} = 122.142 \cdot \text{deg}$
 denominator is the same as above. Second quadrant

$$I_C = \frac{3.71 \cdot e^{j \cdot 122.14 \cdot \text{deg}}}{3.289 \cdot e^{j \cdot 107.224 \cdot \text{deg}}} \cdot 284 \cdot \text{mA} \cdot e^{j \cdot 84.04 \cdot \text{deg}} = \frac{3.71}{3.289} \cdot 284 \cdot \text{mA} \quad / \underline{122.14 - 107.224 + 84.04}^\circ = 320 \text{mA} / \underline{98.96}^\circ$$

This current is greater than the input current. What's going on?

The angle between I_C & I_{L2} is big enough that they somewhat cancel each other out.

Check Kirchoff's Current Law: $I_C + I_{L2} = 29.485 + 282.569j \cdot \text{mA} = I_{L1} = 29.485 + 282.569j \cdot \text{mA}$

Ex 3. a) Find Z_2 .


$$I := 25 \cdot \text{mA} \cdot e^{j \cdot 10 \cdot \text{deg}}$$

$$V_{in} := 10 \cdot V \cdot e^{j \cdot 20 \cdot \text{deg}}$$

$$Z_T := \frac{V_{in}}{I} = \frac{10 \cdot V}{25 \cdot \text{mA}} \quad / \underline{-20 - 10}^\circ = 400 \Omega / \underline{-30}^\circ$$

$$Z_T = 346.41 - 200j \cdot \Omega$$
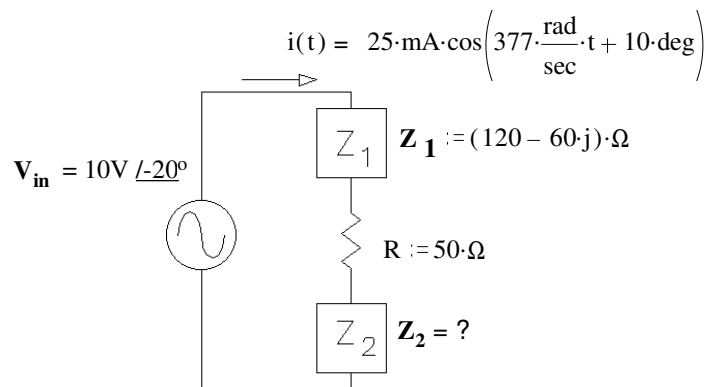
$$Z_2 := Z_T - R - Z_1 = (346.41 - 200j \cdot \Omega) - 50 \cdot \Omega - (120 - 60j \cdot \Omega) = 176.41 - 140j \cdot \Omega$$



b) Circle 1: i) The source current leads the source voltage

<--- answer, because $10^\circ > -20^\circ$.

ii) The source voltage leads the source current

ECE 3600 Phasor Examples p4


Ex 4. a) Find V_{in} in polar form.

$$I_Z := 100 \cdot \text{mA} \quad Z := (80 - 60j) \cdot \Omega$$

$$V_{in} := I_Z \cdot Z \quad V_{in} = 8 - 6j \cdot \text{V}$$

$$\sqrt{8^2 + 6^2} = 10 \quad \text{atan}\left(\frac{-6}{8}\right) = -36.87 \cdot \text{deg}$$
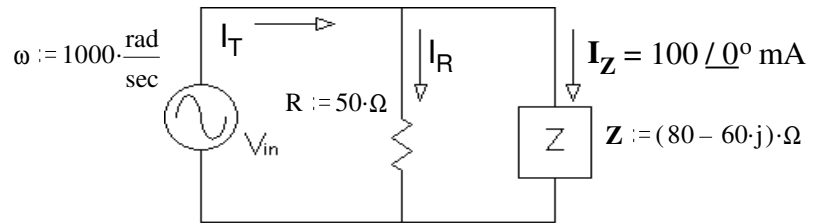
$$V_{in} = 10\text{V} \angle -36.9^\circ$$



b) Find I_T in polar form. $I_R := \frac{V_{in}}{R} = \frac{10 \cdot \text{V}}{50 \cdot \Omega} \angle -36.9^\circ = \frac{10 \cdot \text{V}}{50 \cdot \Omega} \cdot \cos(-36.9 \cdot \text{deg}) + j \cdot \frac{10 \cdot \text{V}}{50 \cdot \Omega} \cdot \sin(-36.9 \cdot \text{deg}) = 160 - 120j \cdot \text{mA}$

$$I_T := I_R + I_Z = (160 - 120j) \cdot \text{mA} + 100 \cdot \text{mA} = 260 - 120j \cdot \text{mA}$$

$$\sqrt{260^2 + 120^2} = 286.356 \quad \text{atan}\left(\frac{-120}{260}\right) = -24.78 \cdot \text{deg} \quad I_T = 286\text{mA} \angle -24.8^\circ$$

c) Circle 1: i) The source current leads the source voltage answer i), $-24.8^\circ > -36.9^\circ$ ii) The source voltage leads the source current

Ex 5. a) The impedance Z (above) is made of two components in series. What are they and what are their values?

$$Z = 80 - 60j \cdot \Omega$$

Must have a resistor because there is a real part.


$$R := \text{Re}(Z)$$

$$R = 80 \cdot \Omega$$

Must have a capacitor because the imaginary part is negative.

$$\text{Im}(Z) = -60 \cdot \Omega = \frac{-1}{\omega \cdot C} \quad C := \frac{-1}{\omega \cdot \text{Im}(Z)}$$

$$C = 16.667 \cdot \mu\text{F}$$

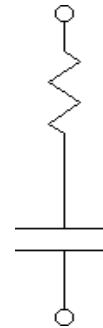

b) The impedance Z is made of two components in parallel. What are they and what are their values?

$$Z = 80 - 60j \cdot \Omega$$

Must have a resistor because there is a real part.

Must have a capacitor because the imaginary part is negative.

$$Z = \frac{1}{\frac{1}{R} + j \cdot \omega \cdot C} \quad \frac{1}{Z} = \frac{1}{(80 - 60j) \cdot \Omega} \cdot \frac{(80 + 60j)}{(80 + 60j)} = \frac{80 + 60j}{80^2 + 60^2} = \frac{80 + 60j}{10,000} \cdot \frac{1}{\Omega}$$

$$\frac{1}{Z} = 8 \cdot 10^{-3} + 6 \cdot 10^{-3}j \cdot \Omega^{-1} = \frac{1}{R} + j \cdot \omega \cdot C$$

$$\frac{1}{R} = .008 \cdot \frac{1}{\Omega}$$

$$R := \frac{1}{.008 \cdot \frac{1}{\Omega}}$$

$$R = 125 \cdot \Omega$$

$$\omega \cdot C = .006 \cdot \frac{1}{\Omega}$$

$$C := \frac{.006 \cdot \frac{1}{\Omega}}{\omega}$$

$$C = 6 \cdot \mu\text{F} \quad R = 125 \cdot \Omega$$

