

Review of Phasors

ECE 3600

A. Stolp
9/3/08
rev.

For steady-state sinusoidal response ONLY


Phasors

Time domain

$$v(t) = V_1 \cdot \cos(377 \cdot t + \theta)$$


Phasor, frequency domain
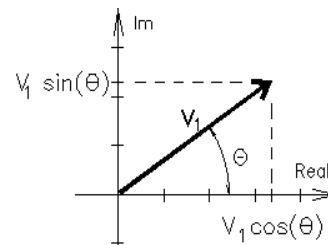
$$\mathbf{V}_1 = V_1 \cdot e^{j\theta} = V_1 \angle \theta = V_1 \cdot \cos(\theta) + j \cdot V_1 \cdot \sin(\theta)$$



Impedances,

Inductor

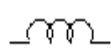

$$v_L = L \cdot \frac{d}{dt} i_L = L \cdot \frac{d}{dt} I_p \cdot e^{j(\omega t + \theta)} = j \cdot \omega \cdot L \cdot [I_p \cdot e^{j(\omega t + \theta)}]$$

$$\mathbf{V}_L(\omega) = j \cdot \omega \cdot L \cdot \mathbf{I}(\omega)$$

AC impedance

$$\mathbf{Z}_L = j \cdot \omega \cdot L$$

Capacitor



$$i_C = C \cdot \frac{d}{dt} v_C = C \cdot \frac{d}{dt} V_p \cdot e^{j(\omega t + \theta)} = j \cdot \omega \cdot C \cdot [V_p \cdot e^{j(\omega t + \theta)}]$$

$$\mathbf{I}_C(\omega) = j \cdot \omega \cdot C \cdot \mathbf{V}(\omega)$$

$$\mathbf{V}_C(\omega) = \frac{1}{j \cdot \omega \cdot C} \cdot \mathbf{I}(\omega)$$

$$\mathbf{Z}_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$$

Resistor




$$v_R = i_R \cdot R$$

$$\mathbf{V}_R(\omega) = R \cdot \mathbf{I}(\omega)$$

$$\mathbf{Z}_R = R$$

You can use impedances just like resistances as long as you deal with the complex arithmetic.
ALL the DC circuit analysis techniques will work with AC.

series:

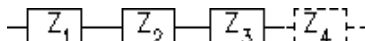


$$\mathbf{Z}_{eq} = \mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3 + \dots$$

$$f := 60 \text{ Hz}$$

$$\omega := 2 \cdot \pi \cdot f$$

$$\omega = 377 \frac{\text{rad}}{\text{sec}}$$

Example:

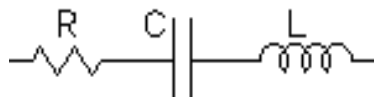

$$R := 20 \cdot \Omega$$

$$L := 80 \text{ mH}$$

$$C := 60 \cdot \mu\text{F}$$

$$j \cdot \omega \cdot L = 30.159j \cdot \Omega$$

$$\frac{1}{j \cdot \omega \cdot C} = -44.21j \cdot \Omega$$

$$\mathbf{Z}_{eq} := R + \frac{1}{j \cdot \omega \cdot C} + j \cdot \omega \cdot L = 20 \cdot \Omega - 44.21j \cdot \Omega + 30.16j \cdot \Omega = 20 - 14.05j \cdot \Omega$$

$$\sqrt{(20 \cdot \Omega)^2 + (14.05 \cdot \Omega)^2} = 24.44 \cdot \Omega$$

$$\text{atan}\left(\frac{-14.05 \cdot \Omega}{20 \cdot \Omega}\right) = -35.09 \cdot \text{deg}$$

$$\mathbf{Z}_{eq} = 24.44 \Omega \angle -35.1^\circ$$

$$\text{If: } \mathbf{V} := 120 \cdot \text{V} \cdot e^{j0 \cdot \text{deg}}$$

$$\mathbf{I} := \frac{\mathbf{V}}{\mathbf{Z}_{eq}} = \frac{120 \cdot \text{V}}{24.44 \cdot \Omega} = 4.91 \cdot \text{A} \quad \angle 0 - -35.1 = 35.1 \text{ deg}$$

$$4.91 \cdot \cos(35.1 \cdot \text{deg}) = 4.017$$

$$4.91 \cdot \sin(35.1 \cdot \text{deg}) = 2.823$$

$$\mathbf{I} = 4.017 + 2.822j \cdot \text{A}$$

slight roundoff error

Voltage divider:

$$V_{Z_n} = V_{total} \cdot \frac{Z_n}{Z_1 + Z_2 + Z_3 + \dots}$$


Eg: $V_C := V \cdot \frac{j \cdot \omega \cdot C}{Z_{eq}} = 120 \cdot V \cdot e^{j \cdot 0 \cdot \text{deg}} \cdot \frac{44.21 \cdot e^{-j \cdot 90 \cdot \text{deg}} \cdot \Omega}{24.44 \cdot e^{-j \cdot 35.1 \cdot \text{deg}} \cdot \Omega}$

$$120 \cdot V \cdot \frac{44.21 \cdot \Omega}{24.44 \cdot \Omega} = 217.07 \cdot V \quad \angle 0 + -90 - -35.1 = -54.9 \text{ deg}$$

$$V_C = 217.1V \angle -54.9^\circ \quad V_C = 124.771 - 177.604j \cdot V$$

$$217.1 \cdot \cos(-54.9 \cdot \text{deg}) = 124.8 \quad 217.1 \cdot \sin(-54.9 \cdot \text{deg}) = -177.6$$


parallel:

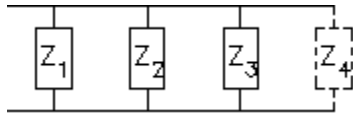

$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

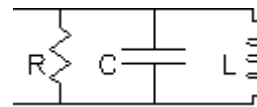Example:

f := 60-Hz $\omega := 2 \cdot \pi \cdot f$ $\omega = 377 \cdot \frac{\text{rad}}{\text{sec}}$



L := 80-mH

$j \cdot \omega \cdot L = 30.159j \cdot \Omega$

R := 20- Ω

C := 60- μF

$\frac{1}{\omega \cdot L} = 3.316 \cdot 10^{-2} \cdot \frac{1}{\Omega}$

$\frac{1}{j \cdot \omega \cdot C} = -44.21j \cdot \Omega$

$\omega \cdot C = 2.262 \cdot 10^{-2} \cdot \frac{1}{\Omega}$

$$Z_{eq} := \frac{1}{\frac{1}{R} + \frac{1}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} + \frac{1}{j \cdot \omega \cdot L}} = \frac{1}{\frac{1}{R} + j \cdot \omega \cdot C - \frac{j}{\omega \cdot L}} = \frac{1}{\frac{1}{20 \cdot \Omega} + 2.262 \cdot 10^{-2} \cdot j \cdot \frac{1}{\Omega} - 3.316 \cdot 10^{-2} \cdot j \cdot \frac{1}{\Omega}} = \frac{1}{\left(5 \cdot 10^{-2} - 1.054 \cdot 10^{-2} \cdot j\right) \cdot \frac{1}{\Omega}}$$

$$= \frac{1}{\left(5 \cdot 10^{-2} - 1.054 \cdot 10^{-2} \cdot j\right) \cdot \frac{1}{\Omega}} \cdot \frac{5 \cdot 10^{-2} + 1.054 \cdot 10^{-2} \cdot j}{5 \cdot 10^{-2} + 1.054 \cdot 10^{-2} \cdot j} = 19.149 + 4.037j \cdot \Omega$$

OR, If you want a polar result, it's actually easier to change the denominator to polar and then do polar division.

$$\sqrt{\left(5 \cdot 10^{-2} \cdot \frac{1}{\Omega}\right)^2 + \left(1.054 \cdot 10^{-2} \cdot \frac{1}{\Omega}\right)^2} = 5.11 \cdot 10^{-2} \cdot \frac{1}{\Omega} \quad \text{atan}\left(\frac{-1.054 \cdot 10^{-2} \cdot \Omega}{5 \cdot 10^{-2} \cdot \Omega}\right) = -11.9 \cdot \text{deg}$$

$$\frac{1}{5.11 \cdot 10^{-2} \cdot \frac{1}{\Omega}} = 19.569 \cdot \Omega \quad \angle 0 - -11.9 = 11.9 \text{ deg} \quad Z_{eq} = 19.57\Omega / 11.9^\circ$$

ff: $V := 120 \cdot V \cdot e^{j \cdot 0 \cdot \text{deg}}$ $I := \frac{V}{Z_{eq}} = \frac{120 \cdot V}{19.57 \cdot \Omega} = 6.132 \cdot A \quad \angle 0 - 11.9 = -11.9 \text{ deg}$

$6.132 \cdot \cos(-11.9 \cdot \text{deg}) = 6$

$6.132 \cdot \sin(-11.9 \cdot \text{deg}) = -1.264$

$I = 6 - 1.265j \cdot A$

slight roundoff error

Current divider:

$$I_{Z_n} = I_{total} \cdot \frac{\frac{1}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

Eg: $I_L := I \cdot \frac{\frac{1}{j \cdot \omega \cdot L}}{\frac{1}{R} + j \cdot \omega \cdot C + \frac{1}{j \cdot \omega \cdot L}} = I \cdot \frac{\left(\frac{1}{j \cdot \omega \cdot L}\right)}{\left(\frac{1}{Z_{eq}}\right)} = I \cdot \frac{Z_{eq}}{j \cdot \omega \cdot L}$

$$= 6.132 \cdot A \cdot e^{j \cdot -11.9 \cdot \text{deg}} \cdot \frac{19.57 \cdot e^{j \cdot 11.9 \cdot \text{deg}} \cdot \Omega}{30.159 \cdot e^{j \cdot 90 \cdot \text{deg}} \cdot \Omega}$$

$$I_L = 6.132 \cdot A \cdot \frac{19.57 \cdot \Omega}{30.159 \cdot \Omega} = 3.979 \cdot A$$

$\angle -11.9 + 11.9 - 90 = -90 \text{ deg}$

$I_L = -3.979 \cdot 10^3 j \cdot \text{mA}$

Duh...

$\frac{V}{j \cdot \omega \cdot L} = -3.979 \cdot 10^3 j \cdot \text{mA}$