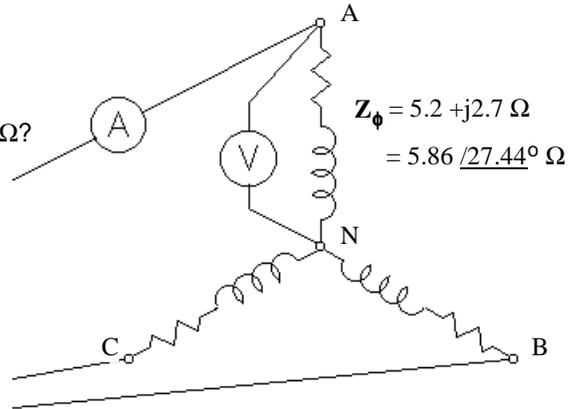


ECE 3600 homework # 4

Note: All voltages and currents are always assumed to be RMS unless said to be otherwise.

- The following are questions from p 78 of the textbook. These could be good closed-book exam questions.
 - 2.1. What types of connections are possible for three-phase generators and loads?
 - 2.2. What is meant by the term “balanced” in a balanced three-phase system?
 - 2.3. What is the relationship between phase and line voltages and currents for a wye (Y) connection?
 - 2.4. What is the relationship between phase and line voltages and currents for a delta (Δ) connection?
 - 2.5. What is phase sequence?
 - 2.7. What is a Y- Δ transform?
- Textbook 2-1. Three impedances of $4 + j3 \Omega$ are Δ -connected and tied to a three-phase 208-V power line. Find I_ϕ , I_L , P, Q, S (|S|), and the power factor of this load.
- A balanced three-phase 480-V source (three line-to-neutral voltages of 277 V) supplies a balanced three-phase inductive load. The load draws a total of 9 kW at a power factor of 0.9. Calculate the phase currents and the magnitude of the per-phase load impedances, assuming a Y-connected load. Draw a phasor diagram showing all three voltages and currents, assume V_a is 0° .
 - In order to correct the power factor, three capacitors are connected in parallel with the load impedances. Find the value of the capacitors.
- Repeat problem 3, assuming a delta-connected load.
- The voltmeter shown measures 120 V. Let this voltage be the phase reference (0°). The phase impedance is $Z_\phi = 5.2 + j2.7 = 5.86 \angle 27.44^\circ \Omega$?
 - What is V_{AB} as a phasor?
 - What would the ammeter measure?
 - What is the apparent power?
 - What is the real power?
 - Correct the power factor with capacitors connected in a delta configuration, that is, find the value of the capacitors.
- Three 230-V generators are connected in a wye configuration to generate three-phase power. The load consists of three balanced delta-connected impedances of $Z_L = 3.8 + j1.5 \Omega$.
 - An ammeter is placed in one line, what would it measure?
 - Find the total apparent power.
 - Find the total real power consumed by the load.
 - What is the phase angle between I_A and V_{AB} , assuming ABC rotation?




Answers

1. a) 2.1. Y & Δ b) 2.2. The 3 voltages are equal, the 3 currents are equal and the 3 loads are equal.


c) 2.3. $V_\phi = \frac{V_{LL}}{\sqrt{3}} = \frac{V_L}{\sqrt{3}}$ $I_\phi = I_L$ d) 2.4. $V_\phi = V_{LL} = V_L$ $I_\phi = \frac{I_L}{\sqrt{3}}$

e) 2.5. abc or acb f) 2.7. $Z_Y = \frac{Z_\Delta}{3}$ 2. 41.6A·A 72.1·A 20.8·kW
 15.6·kVAR 26.0·kVA

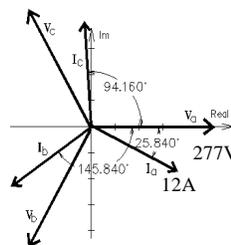3. 12·A lagging by 25.8° 23· Ω
 b) 50.2· μ F



4. 6.95A / 4.16° 69.1· Ω
 b) 16.7· μ F

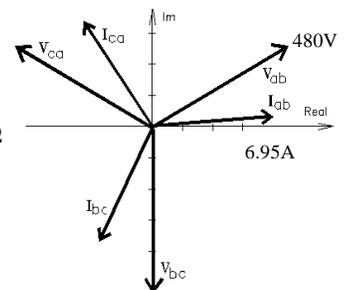

5. a) $208 \cdot V \cdot e^{j30\text{-deg}}$ b) 20.5·A c) 7.37·kVA d) 6.54·kW e) 69.5· μ F
 6. 168·A 117·kVA 108·kW -51.541°