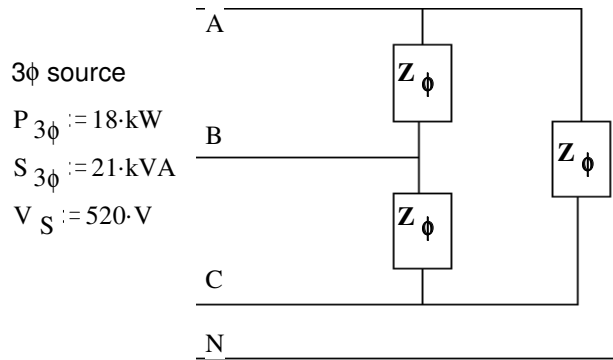



# ECE 3600 homework # 5

b

1. A 3-phase circuit is connected as shown. Find the following:
- The load power factor, assume lagging.
  - The line current.
  - The phase impedance,  $Z_\phi$
  - The value of Y-connected impedances that would result in exactly the same line currents and same pf.
  - The reactive power of each  $Z_\phi$
  - Correct the power factor with capacitors connected in a wye configuration.  $\omega := 377 \frac{\text{rad}}{\text{sec}}$



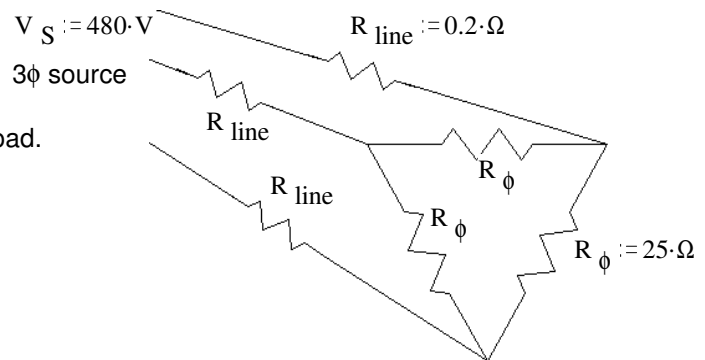2. For the three-phase circuit shown, the  $R_{\text{line}}$  resistors represent the resistance of the distribution system. Find the following:
- Total power out of the source, including line and load.
  - Line losses.
  - Distribution system efficiency.



3. Textbook 2-6
- & b) For the apparent power, just the total will be sufficient.
- For the two parts below, assume the source voltage is adjusted so that the bus voltage at the plant remains 480V and the lines each have an impedance of  $Z_{\text{line}} := (0.05 + j \cdot 0.1) \cdot \Omega$
- With the switch open, find the magnitude of the source voltage and the efficiency of the system.
  - With the switch closed, find the magnitude of the source voltage and the efficiency of the system.

## Answers

1. a) 0.857	2. a) 27·kW	3. a) 59.86·kW	b) Loads 1 & 2 are the same	c) 505.4·V
b) 23.3·A	b) 632.8·W	34.56·kVAR	Caps 0·W	96.8·%
c) 38.6·Ω ∠ 31·deg	c) 97.7%	46.04·kW	-46.06·kVAR	d) 496.0·V
d) 12.9·Ω ∠ 31·deg		34.53·kVAR	input: 105.9·kW	97.6·%
e) 3.61·kVAR		input: 105.9·kW	69.09·kVAR	
f) 106·μF		126.4·kVA	23.03·kVAR	
		152·A	108.4·kVA	
			130.4·A	