

Constant Noise Figure Circles.

We can write the noise figure of a two-port N/w as.

$$F = F_{min} + \frac{r_n}{g_s} |y_s - y_{opt}|^2 \quad - (1)$$

$r_n \rightarrow$ equivalent normalized noise resistance ($r_n = \frac{R_n}{Z_0}$)

$y_s = g_s + jb_s$, normalized ^{source} admittance $y_{opt} = g_{opt} + jb_{opt}$ -

normalized source admittance that results in minimum

(or optimum) noise figure, called F_{min}

y_s & y_{opt} can be represented in terms of reflection coefficient

Γ_s and Γ_{opt} as

$$y_s = \frac{1 - \Gamma_s}{1 + \Gamma_s} \quad y_{opt} = \frac{1 - \Gamma_{opt}}{1 + \Gamma_{opt}} \quad - (2)$$

Substituting (2) in (1) and solving we get

$$F = F_{min} + \frac{4r_n |\Gamma_s - \Gamma_{opt}|^2}{(1 - |\Gamma_s|^2) |1 + \Gamma_{opt}|^2} \quad - (3)$$

The equation (3) depends on F_{min} , r_n and Γ_{opt} . These quantities are known as noise parameters and are given by manufacturer


→ The source reflection coefficient can be varied until a minimum noise figure is read on a noise figure meter.

→ The value of F_{min} , which occurs when $\Gamma_S = \Gamma_{opt}$ can be read from the meter, and the source reflection coefficient that produces F_{min} can be determined accurately using a

mlw analyser. → The noise resistance r_n can be measured by reading the noise figure when $\Gamma_S = 0$, called $F_{\Gamma_S=0}$

$$r_n = (F_{\Gamma_S=0} - F_{min}) \frac{|1 + \Gamma_{opt}|^2}{4|\Gamma_{opt}|^2} \quad - (4)$$

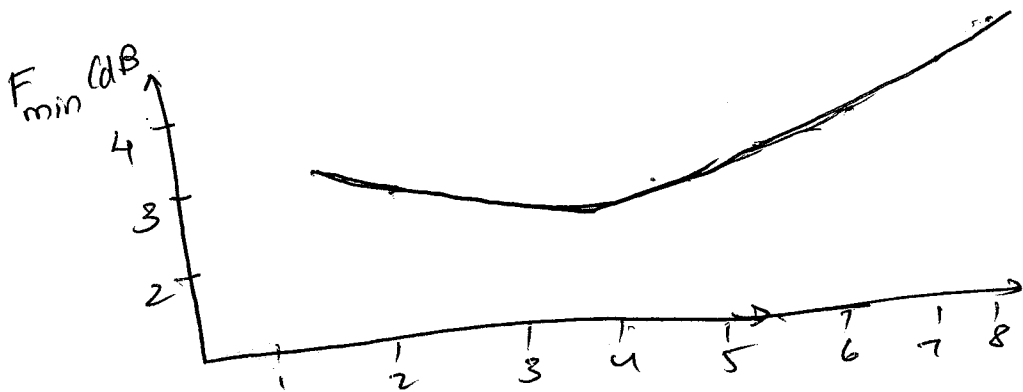F_{min} is a function of the device operating current and frequency, and there is one value of Γ_{opt} with each F_{min} . Figure shows a typical plot of F_{min} versus current for a BJT



We can use (3) to design Γ_s for a given noise figure F_i .

If we rearrange (3) in the following manner

$$\frac{|\Gamma_s - \Gamma_{opt}|^2}{1 - |\Gamma_s|^2} = \frac{F_i - F_{min}}{4g_n} |1 + \Gamma_{opt}|^2 \quad (5)$$

we notice that for a given noise figure F_i RHS of (5) is a constant. Defining the noise figure parameter

N_i as

$$N_i = \frac{F_i - F_{min}}{4g_n} |1 + \Gamma_{opt}|^2 \quad (6)$$

we can write (5) as

$$\frac{|\Gamma_s - \Gamma_{opt}|^2}{1 - |\Gamma_s|^2} = N_i \quad \left[|\Gamma_s - \Gamma_{opt}|^2 = (\Gamma_s - \Gamma_{opt})(\Gamma_s^* - \Gamma_{opt}^*) \right]$$

which when expanded gives

$$|\Gamma_s|^2 - \frac{2}{1 + N_i} \operatorname{Re}(\Gamma_s \Gamma_{opt}^*) + \frac{|\Gamma_{opt}|^2}{1 + N_i} = \frac{N_i}{1 + N_i} \quad (7)$$

This equation corresponds to the equation of a circle in the Γ_S plane, which can be expressed in the form

$$\left| \Gamma_S - \frac{\Gamma_{opt}}{1+N_i} \right|^2 = \frac{N_i^2 + N_i(1-|\Gamma_{opt}|^2)}{(1+N_i)^2}$$

For a given N_i , the center of the circle is located at

$$C_{F_i} = \frac{\Gamma_{opt}}{1+N_i} \quad - (8)$$

& radius is

$$r_{F_i} = \frac{1}{1+N_i} \sqrt{N_i^2 + N_i(1-|\Gamma_{opt}|^2)} \quad - (9)$$

Using (6) we calculate N_i for various F_i & then use (8) & (9) to obtain a family of constant noise circles in the Γ_S plane.

→ NOTE

$$\downarrow \quad F_i = F_{min}, \quad N_i = 0, \quad C_{F_{min}} = \Gamma_{opt} \quad \& \quad r_{F_{min}} = 0$$

ie center of F_{min} circle is located at Γ_{opt} with zero radius. The centers of the other noise figure circles are located along the Γ_{opt} vector.

NOTE:

→ In practical applications we observe that there is always a difference between the designed noise figure and the measured noise figure of the final amplifier.

→ This occurs because of

- 1) loss associated with the matching elements
- 2) Transistor noise figure variations from unit to unit

→ Typical NF variation can be from a fraction of a decibel to 1 dB in a narrowband design.

→ Low Noise Design

→ Tradeoff between gain, noise figure, and VSWRs.

Fig 4-3-3 (a good example of tradeoff between gain and noise figure)

→ Unilateral transistor $[S_{12} = 0]$

For gain $(G_s @ s)$

$$G_{s, \max.}, \rho_s, \zeta_s, r_s$$

In this problem maximum gain is 3 dB & minimum noise figure is 0.8 dB.

At 3dB $\Gamma_S = 0.7 \angle 110^\circ$ (F_{min} , R_n , Γ_{opt} provided)

results in a NF $F_n \approx 4\text{dB}$ & minimum NF $F_{min} = 0.8\text{dB}$ obtained
with $\Gamma_S = 0.6 \angle 40^\circ$ results in a gain of -1dB

eg: $S_{11} = 0.707 \angle -155^\circ$ $S_{12} = 0$
 $S_{21} = 5.0 \angle 180^\circ$ $S_{22} = 0.51 \angle -20^\circ$

$F_{min} = 3\text{dB}$ $R_n = 4\Omega$ $\Gamma_{opt} = 0.45 \angle 180^\circ$

Soln Design i/p & o/p matching Nlw to produce a
power gain of 16dB

$K = \infty$

$|A| = 0.3606 \rightarrow$ Transistor is unconditionally stable

$$G_{S,max} = \frac{1}{1 - |S_{11}|^2} = 3\text{dB}$$

$$G_{L,max} = \frac{1}{1 - |S_{22}|^2} = 1.31\text{dB}$$

$$G_b = |S_{21}|^2 = 13.98\text{dB}$$

$$G_{TU,max} = 3 + 1.31 + 13.98 = 18.29\text{dB} \text{ (max gain)}$$

We want 16dB gain

We can design for $G_S = 1.22\text{dB}$ & $G_L = 0.78\text{dB}$

$$g_S = ? \quad \Gamma_{g_S} = 0.5634 \angle 155^\circ \quad \Gamma_{g_L} = 0.4655 \angle 20^\circ$$

$$r_{g_S} = 0.3496$$

$$r_{g_L} = 0.2581$$

Determine 3.5dB noise figure @

$$C_{F_1} = 0.3658 \angle 180^\circ$$

$$g_{F_1} = 0.3953$$

- Draw the OS

Choose a point on the 1.22dB @ as Γ_S , the noise figure for this value would stay within 3.5dB.

- Design load side matching N/W by choosing Γ_L on the $G_v = 0.78$ dB @.

eg 4.3.1

$$S_{11} = 0.552 \angle 169^\circ$$

$$S_{21} = 1.681 \angle 26^\circ$$

$$S_{12} = 0.049 \angle 23^\circ$$

$$S_{22} = 0.839 \angle -67^\circ$$

$$F_{min} = 2.5 \text{dB}$$

$$\Gamma_{opt} = 0.475 \angle 166^\circ$$

$$R_n = 3.5 \Omega$$

Design Amplifier for minimum NF

Soln

① Calculate $K = 1.012$

$$|S_{11}| = 0.419$$

Transistor is unconditionally stable

$$\textcircled{2} \quad G_{T, \max} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1})$$

$$= 14.7 \text{ dB}$$

$$\textcircled{3} \quad \Gamma_{ms} = \frac{B_1 - \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$

$$\Gamma_{ml} = \frac{B_2 - \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

minimum NF of 2.5 dB is obtained with $\Gamma_s = \Gamma_{opt} = 0.475 \angle 166^\circ$

④ Calculate NF OS for different F_i

In this example we take $F_i = 2.5 - 3 \text{ dB}$

a) Calculate N_i using (4.3.6)

$$N_i = \frac{F_i - F_{\min}}{4r_n} |1 + \Gamma_{opt}|^2 = 0.1378$$

$$\text{b) } C_{F_i} = \frac{\Gamma_{opt}}{1 + N_i} = 0.417 \angle 166^\circ$$

$$\text{c) } \gamma_{F_i} = \frac{1}{1 + N_i} \sqrt{N_i^2 + N_i (|1 + \Gamma_{opt}|^2)} = 0.312$$

⑤ Draw gain @s Γ_s plane

$$G_A, g_a, C_a, r_a$$

$$g_a = \frac{g_a C_i^*}{1 + g_a (|S_{11}|^2 - |A|^2)}$$

$$r_a = \frac{[1 - 2K|S_{12}S_{21}|g_a + |S_{12}S_{21}|^2 g_a^2]^{1/2}}{|1 + g_a (|S_{11}|^2 - |A|^2)|}$$

⑥ ($\Gamma_L = \Gamma_{opt}^*$)

$$\Gamma_{s2} \Gamma_{opt} \quad \Gamma_L = \left(\frac{S_{22} + S_{12}S_{21}\Gamma_{opt}}{1 - S_{11}\Gamma_{opt}} \right)^* = 0.844 \angle 10.4^\circ$$

eg 4.3.2 LNA $(VSWR)_{in} < 1.8$

① Calculate $K = 1.172$

② ~~F_{min}~~ Calculate $|\Delta| = 0.151$

unconditionally stable

③ Calculate Γ_{ms} , Γ_{ml} & $G_{A,max}$

Plot values of Γ_{opt} and Γ_{ms}

eg $S_{11} = 0.6 \angle -60^\circ$ $S_{21} = 1.9 \angle 81^\circ$

$S_{12} = 0.05 \angle 26^\circ$ $S_{22} = 0.5 \angle -60^\circ$

$F_{min} = 1.6 \text{ dB}$ $R_n = 20 \Omega$ $\Gamma_{opt} = 0.62 \angle 100^\circ$

a) Assume the FET to be unilateral and design an amplifier for a maximum possible gain & a noise figure no more than 2.0 dB. Estimate error introduced in G_T due to this assumption.

b) Redesign amplifier for bilateral case

Soln

① $K = 2.778$

$|A| = 0.3713$

} unconditionally stable

$$\frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2}$$

$$U = \frac{|S_{12}| |S_{21}| |S_{11}| |S_{22}|}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$

$$-0.501 \text{ dB} < \frac{G_T}{G_{TU}} < 0.5988 \text{ dB}$$

maximum error in the gain of the amplifier will be in the order of $\pm 0.5 \text{ dB}$

② Calculate $G_{S \text{ max}} = 1.9382 \text{ dB}$

$$G_{L \text{ max}} = 1.25 \text{ dB}$$

③ $G_0 = 5.5751 \text{ dB}$

$$G_{TU \text{ max}} = 1.9382 + 1.25 + 5.5751 = 8.7627 \text{ dB}$$

③ Design $G_S = 1.5 \text{ dB} \text{ \& } 1.7 \text{ dB @ } \omega_s$

a) Calculate $g_S = \frac{G_S}{G_{S \text{ max}}}$

Calculate

$$\underline{1.5\text{dB}} \quad C_s = 0.5618 \angle 60^\circ \quad r_s = 0.2054$$

$$\underline{1.7\text{dB}} \quad C_s = 0.5791 \angle 60^\circ \quad r_s = 0.1507$$

2dB Noise figure. @

$$C_f = \frac{P_{opt}}{1+N_i} = 0.5627 \angle 100^\circ$$

$$g_f = \frac{1}{1+N_i} \sqrt{N_i^2 + N_i(1-|P_{opt}|^2)} = 0.2454$$

Bilateral Case

- Use available power gain

$$\text{For } G_A = 8_{\text{dB}}$$

$$C_a = 0.5274 \angle 64.76^\circ$$

$$R_a = 0.2339$$

~~$G_{A, \text{max}}$~~ = Draw these @s