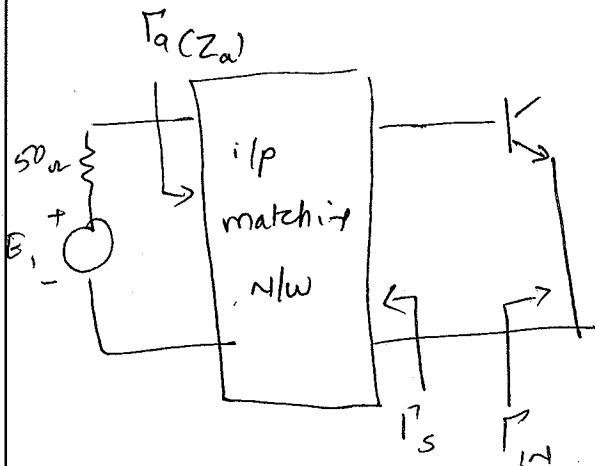


Constant VSWR circle

→ The data sheet for an amplifier usually includes the maximum allowable values of its i/p & o/p VSWR.

→ I/p VSWR \odot can be drawn on Γ_S plane & o/p VSWR \odot can be drawn on Γ_L plane.

For amplifier shown in the figure.



$$(VSWR)_{IN} = \frac{1 + |\Gamma_a|}{1 - |\Gamma_a|} \quad - (1)$$

$$|\Gamma_a| = \left| \frac{\Gamma_{IN} - \Gamma_S^*}{1 - \Gamma_{IN} \Gamma_S} \right| \quad - (2)$$

Constant values of $|\Gamma_a|$ are obtained by values of Γ_S that lie on a \odot

For designing for a given $(VSWR)_{IN}$:

① Calculate

$$C_{v_i} = \frac{\Gamma_{IN}^* (1 - |\Gamma_a|^2)}{1 - |\Gamma_a \Gamma_{IN}|^2} \quad - (3)$$

$$g_{v_i} = \frac{|\Gamma_a| (1 - |\Gamma_{IN}|^2)}{1 - |\Gamma_a \Gamma_{IN}|^2} \quad - (4)$$

In an unconditionally stable case, and in many potentially unstable case, Γ_S can be selected to Γ_{IN}^* for $(VSWR)_{IN} = 1$

Since Γ_L and Γ_{IN} as well as Γ_S and Γ_{OUT} are related by bilinear transformations it follows that circles in Γ_L plane map into \odot in the Γ_{IN} plane and circles in Γ_S plane map into circles in the Γ_{OUT} plane.

These transformations are useful to map values of Γ_L on a constant G_p circle into a circle in the Γ_S plane, where $\Gamma_S = \Gamma_{IN}^*$ and values of Γ_S on a constant G_A \odot into a \odot in the Γ_L plane where $\Gamma_L = \Gamma_{OUT}^*$

The \odot given by

$$C_i = \frac{(1 - S_{22} C_{00})(S_{11} - \Delta C_{00})^* - r_{00}^2 \Delta^* S_{22}}{|1 - S_{22} C_{00}|^2 - r_{00}^2 |S_{22}|^2}$$

& radius

$$r_i = \frac{r_{00} |S_{12} S_{21}|}{|1 - S_{22} C_{00}|^2 - r_{00}^2 |S_{22}|^2}$$

$C_{00} \rightarrow C_p$ or C_A

$r_{00} \rightarrow r_p$ or r_A

~~$C_{00} = \Gamma_{OUT}$~~ maps the values of Γ_L into a \odot in $\Gamma_S = \Gamma_{IN}^*$ plane.

~~$r_{00} = r_{OUT}$~~

III^{ly} a \odot in the Γ_S plane given by

$$|\Gamma_S - C_{ii}| = r_{ii}$$

maps into a \odot in the $\Gamma_L = \Gamma_{OUT}^*$ plane given by

$$C_o = \frac{(1 - S_{11} C_{ii})(S_{22} - \Delta C_{ii})^* - r_{ii}^2 \Delta^* S_{11}}{|1 - S_{11} C_{ii}|^2 - r_{ii}^2 |S_{11}|^2}$$

$$r_{o2} = \frac{r_{ii} |S_{12} S_{21}|}{|1 - S_{11} C_{ii}|^2 - r_{ii}^2 |S_{11}|^2}$$

2 $|\Gamma_a| = 0$ From (3) and (4) we obtain

$$C_{V_i} \Big|_{|\Gamma_a|=0} = \Gamma_{IN}^* \quad \& \quad g_{V_i} \Big|_{|\Gamma_a|=0} = 0$$

In other words, the value of Γ_{IN}^* produces $|\Gamma_a| = 0$
& consequently $(VSWR)_{IN} = 1$

$$\text{Hence } (VSWR)_{OUT} = \frac{1 + |\Gamma_b|}{1 - |\Gamma_b|} \quad - (5)$$

$$|\Gamma_b| = \left| \frac{\Gamma_{OUT} - \Gamma_L^*}{1 - \Gamma_{OUT} \Gamma_L} \right| \quad - (6)$$

The o/p ~~stab~~ VSWR θ can be drawn with

$$C_{V_o} = \frac{\Gamma_{OUT}^* (1 - |\Gamma_b|^2)}{1 - |\Gamma_b \Gamma_{OUT}|^2} \quad - (7)$$

$$g_{V_o} = \frac{|\Gamma_b| (1 - |\Gamma_{OUT}|^2)}{1 - |\Gamma_b \Gamma_{OUT}|^2} \quad - (8)$$

eg: $S_{11} = 0.6 \angle 36^\circ$ $S_{12} = 0.14 \angle -85^\circ$ $S_{21} = 2.3 \angle -80^\circ$ $S_{22} = 0.15 \angle 45^\circ$

1) Determine $G_{A,max}$ and draw a constant G_A circle that is 1dB less than $G_{A,max}$

Soln

$$\textcircled{1} K = 1.17$$

$$|\Delta| = 0.368$$

$$\Delta = 0.368 \angle 27.91^\circ$$

Transistor is unconditionally stable. We can use simultaneous conjugate match with-

$$\Gamma_{MS} = \frac{B_1 - \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \quad C_1 = S_{11} - \Delta S_{22}^*$$

$$\Gamma_{ML} = \frac{B_2 - \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

$$B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \quad C_2 = S_{22} - \Delta S_{11}^*$$

$$\Gamma_{MS} = 0.714 \angle -40.45^\circ \quad \Gamma_{ML} = 0.387 \angle -129.36^\circ$$

resulting in $(\sqrt{SWR})_{IN} = (\sqrt{SWR})_{OUT} = 1$

$$G_{A,max} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1})$$

$$= 9.24 \text{ or } 9.66 \text{ dB}$$

Constant G_A \odot with 1dB less than $G_{A,max}$ is the \odot for $G_A = 8.66 \text{ dB}$. The center & radius of this \odot can be obtained as

$$C_a = \frac{g_a G_1^*}{1 + g_a (|S_{11}|^2 - |\Delta|^2)}$$

$$g_a = \frac{[1 - 2K |S_{12} S_{21}| g_a + |S_{12} S_{21}|^2 g_a^2]^{1/2}}{1 + g_a (|S_{11}|^2 - |\Delta|^2)}$$

$$g_a = \frac{G_A}{|S_{21}|^2} = \frac{7.3451}{(2.3)^2} = 1.3886$$

$$C_a = 0.602 \angle -40.45^\circ$$

$$g_a = 0.3$$

b) Select values of Γ_S on $G_A = G_{A,\max} - 1 \text{ dB}$ \odot . For each value of Γ_S determine values of Γ_L that lie on constant $(VSWR)_{\text{OUT}} = 1.5$ circle. Draw constant VSWR out \odot .

eg:

$$S_{11} = 0.55 \angle -120^\circ$$

$$S_{12} = 0.14 \angle 30^\circ$$

$$S_{21} = 3.5 \angle 60^\circ$$

$$S_{22} = 0.2 \angle -50^\circ$$

Analyze the trade-offs between operating power gain, stability & VSWRs

Soln

① Calculate
$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} = 0.947$$

$$\Delta = S_{11}S_{22} - S_{12}S_{21} = 0.521 \angle -102.01^\circ$$

$K < 1 \rightarrow$ transistor is potentially unstable.

② Draw i/p & o/p stability circles

$$C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2}$$

$$g_S = \left| \frac{S_{12}S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$

$$g_{L1} = \left| \frac{S_{12}S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2}$$

$$C_S = 16.47 \angle 130.7^\circ$$

$$C_L = 1.22 \angle -59.25^\circ$$

$$g_S = 15.52$$

$$g_L = 2.12$$

The maximum stable gain is

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|} = \frac{3.5}{0.14} = 25 \quad (13.98 \text{ dB})$$

Choose $G_p = 12 \text{ dB}$

③ Calculate C_p & r_p

$$C_p = \frac{g_p C_2^*}{1 + g_p (|S_{22}|^2 - |\Delta|^2)} = 0.519 \angle 120.75^\circ$$

$$r_p = \frac{[1 - 2K|S_{12}S_{21}|g_p + |S_{12}S_{21}|^2 g_p^2]^{1/2}}{|1 + g_p (|S_{22}|^2 - |\Delta|^2)|} = 0.639$$

④ Values of Γ_L on 12 dB gain are chosen

⑤ Mapping $G_p = 12 \text{ dB}$ constant gain Θ into $\Gamma_s = \Gamma_{in}^*$ plane.

⑥ Calculate C_i & r_i with $C_{00} = C_p = 0.519 \angle 120.75^\circ$ &

$$r_{00} = r_p = 0.639$$

$$C_i = 0.8 \angle 130.7^\circ \quad r_i = 0.338$$

⑦ Use


$$\Gamma_W = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \quad \text{for } a \& b \text{ we get } a' \& b'$$

DC Bias Circuit for Transistors

The purpose of a good dc bias design is to select the proper quiescent point and hold the quiescent point constant over variations in transistor parameters and temperature. A resistor bias N/w can be used with good results over moderate temperature changes. For large temperature changes an active bias N/w is preferred for large temperature changes.

At low frequencies a bypassed emitter resistor is an important contributor to the quiescent point stability. At microwave frequencies, the bypass capacitor, which is in parallel to the emitter resistor can produce oscillations by making the r/p part unstable at some frequencies. Resistance in an amplifier circuit can degrade the noise figure.

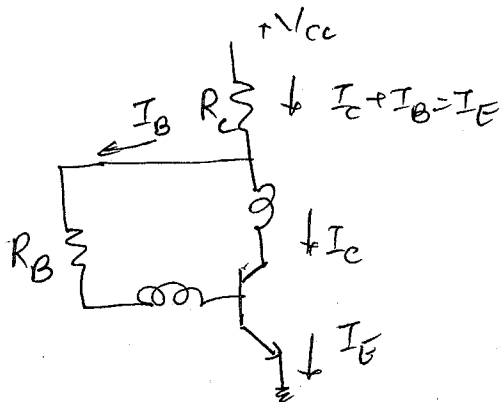A resistive feedback N/w with voltage feedback is shown in the figure below.



V_{BE} is the base emitter voltage.

$$V_{BE} + I_B R_B + I_E R_C = V_{CC}$$

$$I_B = I_E - I_C = (1 - \alpha) I_E$$

$$= \frac{I_E}{1 + \beta}$$

$$I_E = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{(1+\beta)}}$$

$$\begin{cases} I_B R_B + I_E R_C = V_{CC} - V_{BE} \\ \frac{I_E}{1+\beta} R_B + I_E R_C = V_{CC} - V_{BE} \end{cases}$$

$$I_E = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{(1+\beta)}}$$


For I_E to be less sensitive to changes in V_{BE} and β , the following condition must be satisfied

$$V_{CC} \gg V_{BE}$$

$$R_C \gg \frac{R_B}{1+\beta}$$

Advisable to use high V_{CC} and R_C . We can also use small R_B but it will limit V_{CE} and therefore the swing in output.

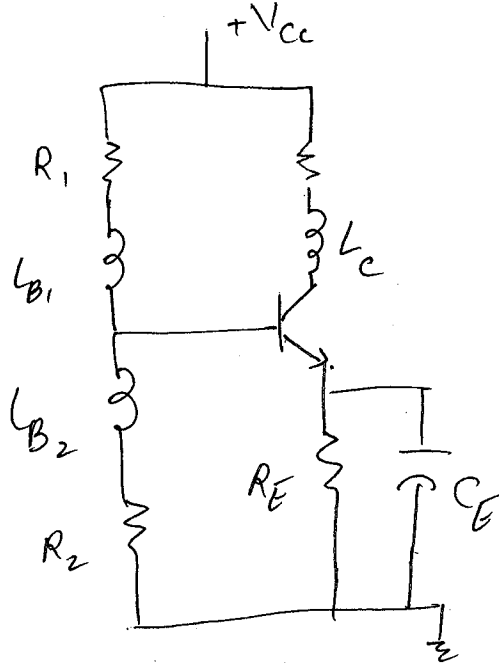An alternative biasing N/W that uses a bypassed resistor at the emitter as shown in the figure




L_C , L_B , and L_{B2} are used to block RF. C_E is used to bypass RF.

This is equivalent of this circuit for the dc condition.

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

From the equivalent ckt we have:

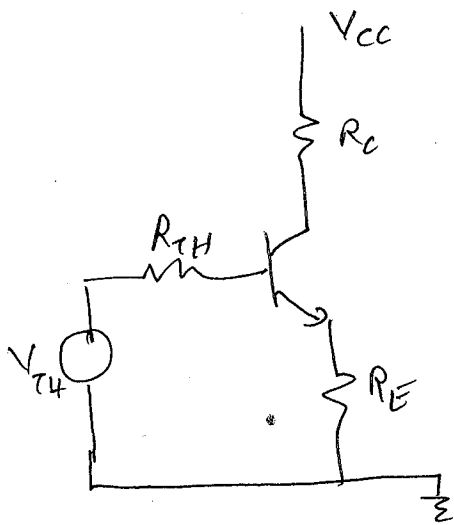

$$V_{TH} = R_{TH} I_B + V_{BE} + R_E I_E$$

$$= \left(\frac{R_{TH}}{1+\beta} + R_E \right) I_E + V_{BE}$$

$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH}/(1+\beta)}$$

Following condition must be met for stable I_E

$$V_{TH} \gg V_{BE} \quad \&$$

$$R_E \gg \frac{R_{TH}}{1+\beta}$$

V_{CC} , V_{TH} cannot be increased arbitrarily because it reduces V_{CE} and hence V_{CE} . Smaller V_{CE} means limited output swing.

→ Large R_E will reduce V_{CE} as well.

→ Smaller R_{TH} will mean low input impedance of the circuit.

V_{TH} is selected no more than 15 to 20% of V_{CC}

3.9.2

$$\begin{aligned} a) \quad V_{CC} &= 15V \quad I_C \approx I_E \\ V_{CC} &= V_{CE} + I_C (R_C + R_E) \\ R_C + R_E &= \frac{15 - 8}{2 \times 10^{-3}} = 3.5 \text{ k}\Omega \end{aligned}$$

Assuming voltage across R_E is 10% to 20% of V_{CC}

$$R_E = \frac{10\% V_{CC}}{I_C} = 750 \Omega$$

$$R_C = 2500 - 750 = 2.75 \text{ k}\Omega$$

$$V_{TH} = \frac{V_{CC} R_2}{R_1 + R_2} \quad R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_1 = R_{TH} \frac{V_{CC}}{V_{TH}} \quad R_2 = \frac{R_{TH}}{\frac{1 - V_{TH}}{V_{CC}}}$$

for good beta (β) stability

R_{TH} is selected such that

$$\beta R_E = 10 R_{TH}$$

$$R_{TH} = \frac{\beta R_E}{10} = \frac{100 (750)}{10} = 7.5 \text{ k}\Omega$$

$$V_{TH} = \frac{I}{\beta} R_{TH} + 0.7 + I_E R_E = 2.35V$$

$$R_1 = 47.9 \text{ k}\Omega$$