
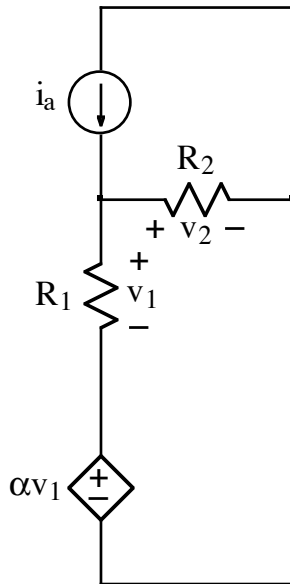


Ex:

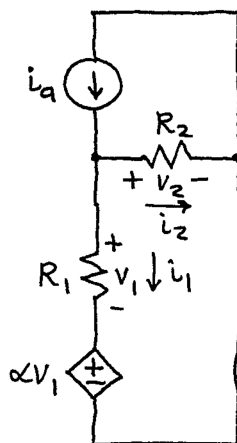

- Derive an expression for v_2 . The expression must not contain more than the circuit parameters α , i_a , R_1 , and R_2 . **Note:** $\alpha > 0$.
- Make at least one consistency check (other than a units check) on your expression. Explain the consistency check clearly.

sol'n: a) Label resistor currents.



We have a v-loop on the bottom:

$$+\alpha v_1 + v_1 - v_2 = 0V$$

All other loops would pass thru a current src.

We can write i -sum eqns for the node on the left or right but we only need one of them.

For the left node, our i -sum eq'n is

$$-i_a + i_2 + i_1 = 0A$$

We have no components in series carrying the same current, (other than a v -src and R).

Last, we write Ohm's law eq'ns for R_1 and R_2 :

$$v_1 = i_1 R_1$$

$$v_2 = i_2 R_2$$

substituting the Ohm's law expressions into the v -loop eq'n gives

$$\alpha i_1 R_1 + i_1 R_1 - i_2 R_2 = 0V$$

$$\text{or } i_1 (\alpha + 1) R_1 - i_2 R_2 = 0V$$

Now we solve our i -sum eq'n for i_1 .
(This is convenient since we will retain i_2 and be able to write an eq'n for v_2 .)

$$i_1 = i_a - i_2$$

Substituting into our last v -loop eq'n, we have

$$(i_a - i_2)(\alpha + 1) R_1 - i_2 R_2 = 0V$$

We simplify and solve for i_2 :

$$i_a (\alpha + 1) R_1 = i_2 [(\alpha + 1) R_1 + R_2]$$

$$\text{or } i_2 = i_a \frac{(\alpha + 1) R_1}{(\alpha + 1) R_1 + R_2}$$

b) Many consistency checks are possible.

ex: Set $\alpha = 0$ so dependent v-src becomes a wire. Circuit becomes i-divider.

$$i_2 = i_a \frac{R_1}{R_1 + R_2}$$

Plug $\alpha = 0$ into answer from (a):

$$i_2 = i_a \frac{(0+1) R_1}{(0+1) R_1 + R_2} = i_a \frac{R_1}{R_1 + R_2} \quad \checkmark$$

(We get the same answer.)

ex: Set $R_2 = 0 \Omega$ (a wire).

All current will flow thru the wire since it is the path of least resistance.

$$\therefore i_2 = i_a$$

Plug $R_2 = 0 \Omega$ into answer from (a):

$$i_2 = i_a \frac{(\alpha + 1) R_1}{(\alpha + 1) R_1 + 0 \Omega} = i_a \quad \checkmark \text{ (same answer)}$$