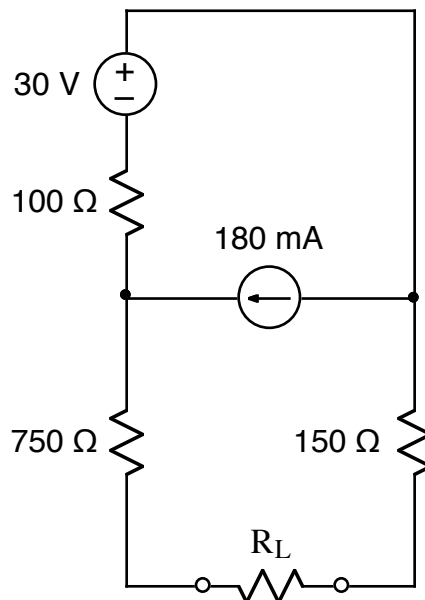



Ex:



- Calculate the value of  $R_L$  that would absorb maximum power.
- Calculate that value of maximum power  $R_L$  could absorb.

Sol'n: a)  $R_L = R_{Th}$  for max power transfer

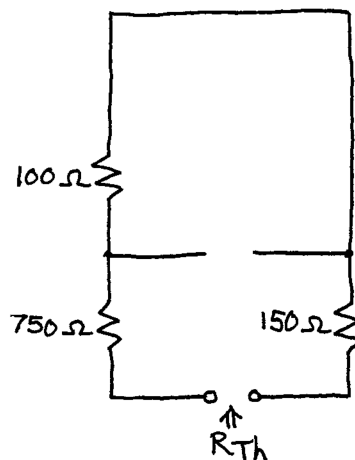We find  $R_{Th}$  by looking into the terminals where  $R_L$  is connected (but without  $R_L$ ) with the two independent sources turned off.



$$R_{Th} = 750\Omega + 100\Omega + 150\Omega$$

$$R_{Th} = 1k\Omega$$


$$\therefore R_L = 1k\Omega$$

$$b) \max pwr = \frac{\left(\frac{V_{Th}}{2}\right)^2}{R_{Th}}$$

We find  $V_{Th}$  as the open circuit voltage across the terminals where  $R_L$  is connected.

We find  $V_{Th}$  by using superposition.

case I: 30V on, 180 mA off

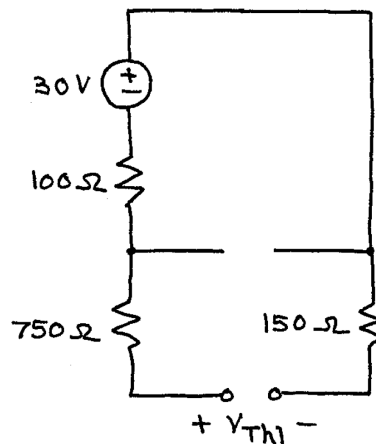


Since no current flows, there is no  $v$ -drop across the  $R$ 's.

$$\therefore V_{Th} = -30V \quad (-v \text{ src})$$

Note: Since we will square  $V_{Th}$ , the polarity we choose for measuring  $V_{Th}$  doesn't matter.

case II: 30V off, 180 mA on

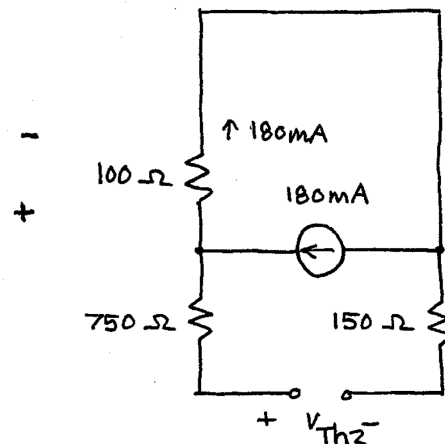

No current flows in the 750 Ω and 150 Ω. Thus, there is no v-drop across these R's.

The v-drop across the 100 Ω is equal to  $V_{Th2}$ .

$$V_{Th2} = 180 \text{ mA} \cdot 100 \Omega = 18 \text{ V}$$

We sum results to find  $V_{Th}$ .

$$V_{Th} = V_{Th1} + V_{Th2}$$

$$V_{Th} = -30 \text{ V} + 18 \text{ V} = -12 \text{ V}$$

$$\text{max pwr} = \frac{\left(\frac{V_{Th}}{2}\right)^2}{R_{Th}} = \frac{6^2}{1k} = 36 \text{ mW}$$