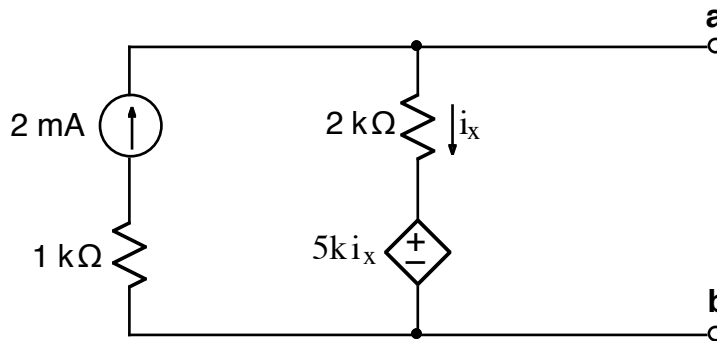


Ex:




- Find the Thevenin equivalent of the above circuit relative to terminals **a** and **b**.
- If we attach R_L to terminals **a** and **b**, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .

Sol'n: a) We first observe that the dependent source is equivalent to a resistance:

$$R_{eq} = \frac{V}{i} = 5k \frac{i_x}{i_x} = 5k\Omega$$

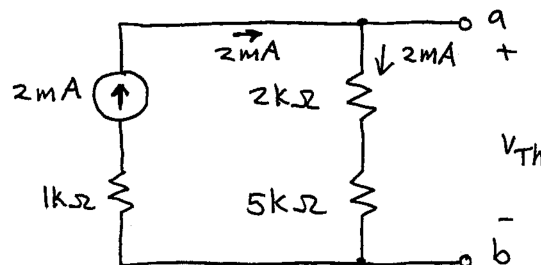
This equivalent resistance is valid regardless of what is connected between **a** and **b**.



$$V_{Th} = V_{a,b \text{ open circuit}} = 2\text{mA} \cdot (2k\Omega + 5k\Omega)$$


$$V_{Th} = 2\text{mA} \cdot 7k\Omega = 14\text{V}$$

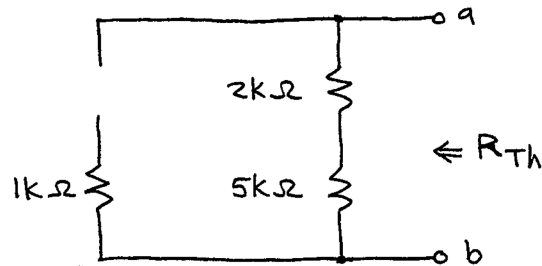We find R_{Th} by turning off i_s and looking in from a, b terminals.



$$R_{Th} = 2\text{k}\Omega + 5\text{k}\Omega = 7\text{k}\Omega$$

Thevenin equivalent:

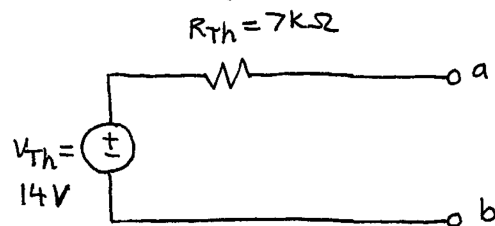

b) $R_L = R_{Th} = 7\text{k}\Omega$ for max pwr

c)
$$P_{max} = V_{R_L} \cdot i_{R_L} = \frac{V_{Th}}{2} \cdot \frac{V_{Th}}{2R_{Th}} = \frac{V_{Th}^2}{4R_{Th}}$$

$$P_{max} = \frac{(14\text{V})^2}{4(7\text{k}\Omega)} = 7\text{mW}$$