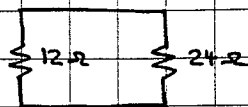


series and parallel R's


Find equivalent resistance R_{ab} looking into a b.

Sol'n:



$$12\Omega \parallel 24\Omega = 12\Omega \cdot \frac{1}{2} = 12\Omega \cdot \frac{1}{2}$$
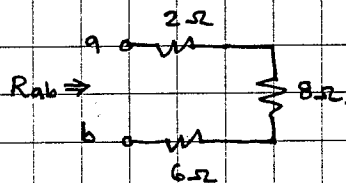
$$= 12\Omega \cdot \frac{2}{3} = 8\Omega$$



$$R_{ab} = 2\Omega + 8\Omega + 6\Omega = 16\Omega$$