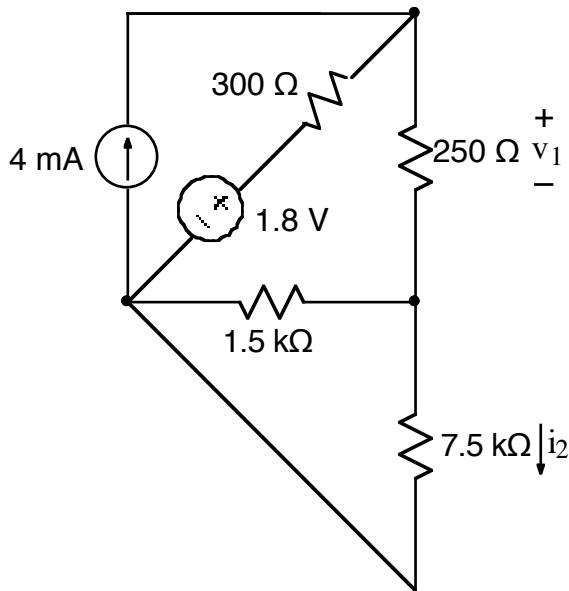


Ex:

Given $v_1 = 5/12 \text{ V}$, $v_2 = 5/2 \text{ V}$ (across 4 mA source with + at top), and $i_2 = 5/18 \text{ mA}$, calculate the power in the 300Ω resistor.

SOL'N:

The power in the 300Ω resistor is

$$\begin{aligned} P &= V \cdot i = (v_2 - 1.8V) \cdot \frac{(v_2 - 1.8V)}{300 \Omega} \\ &= \frac{(2.5V - 1.8V)^2}{300 \Omega} = \frac{(0.7)^2}{300} \text{ W} \end{aligned}$$

$$P \doteq 1.63 \text{ mW}$$