
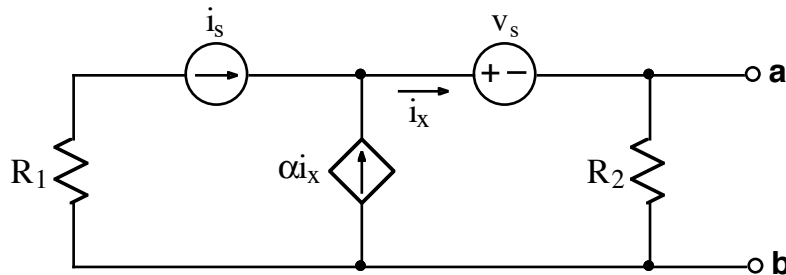


Ex:

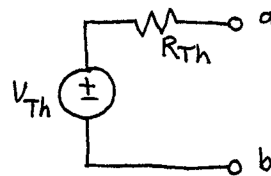


Find the Thevenin's equivalent circuit at terminals a-b. i_x must not appear in your solution. **Note:** $\alpha \neq 1$.

sol'n: We must find V_{Th} and R_{Th} for the Thevenin equivalent circuit that has the same behavior as the above circuit when viewed from a, b terminals.



$V_{Th} = V_{a,b}$ for circuit with nothing connected across a, b.

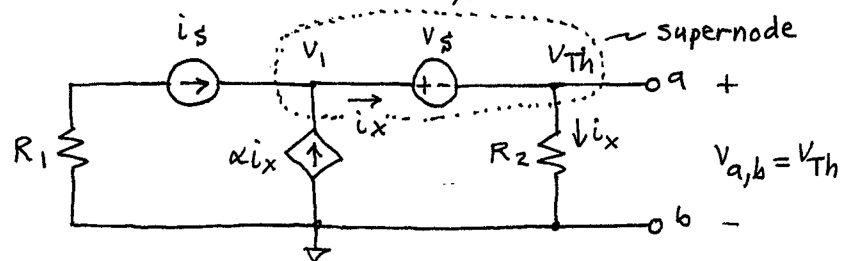We can use node-v method or another method of our choice to find $V_{a,b}$



We first define i_x in terms of node voltages. Here, i_x flows thru R_2 . Thus $i_x = \frac{V_{Th}}{R_2}$.

We have a supernode for v_1 and v_{TH} .

So we sum currents out of a bubble around v_1 , v_{TH} , and v_s .

$$v_1, v_{TH} \text{ node: } -i_s - \alpha \frac{v_{TH}}{R_2} + \frac{v_{TH}}{R_2} = 0A$$

We could continue on to write a voltage eq'n for v_1 and v_{TH} : $v_1 = v_{TH} + v_s$

But our first eq'n has only v_{TH} in it; we can solve the first eq'n for v_{TH} and stop there.

$$\text{Rearranging gives } v_{TH} \left(\frac{1}{R_2} - \frac{\alpha}{R_2} \right) = i_s$$


$$\text{or } v_{TH} = \frac{i_s R_2}{1 - \alpha}$$

To find R_{TH} , we can use the method of shorting out a and b and measuring the current in the wire. This is i_{sc} for short circuit. If we look at a Thevenin

equivalent circuit with a wire from a to b, we have current $i_{sc} = \frac{v_{TH}}{R_{TH}}$.

$$\text{Thus, } R_{TH} = \frac{v_{TH}}{i_{sc}}$$

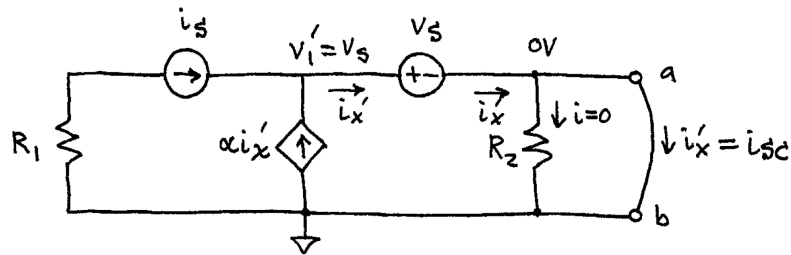We redraw our circuit with a wire from a to b.



This is a different circuit than before.
We have 0V at **a**, (instead of V_{TH}), and
no current flows in R_2 since it is
bypassed by a wire. Also, $i_{sc} = i'_x$.

We also have $v_1 = 0V + v_s = v_s$. Circuit is solved.
or is it? We still need to find $i_{sc} = i'_x$

Using a current summation at v_1 , we have

$$-i_s - \alpha i'_x + i'_x = 0A$$

$$\text{or } i'_x (1 - \alpha) = i_s$$

$$\text{or } i'_x = \frac{i_s}{1 - \alpha} = i_{sc}$$

$$\text{Using } R_{TH} = \frac{V_{TH}}{i_{sc}} \text{ gives } R_{TH} = \frac{\frac{i_s R_2}{1 - \alpha}}{\frac{i_s}{1 - \alpha}}$$

$$\text{or } R_{TH} = R_2 \text{ (Nothing else plays a role in } R_{TH}\text{)}$$

Consistency check: set $\alpha = 0 \Rightarrow$ dependent src = open.

Then R_1, v_s in series with current src i_s irrelevant.

We have Norton equiv, i_s and R_2 : $V_{TH} = i_s R_2$, $R_{TH} = R_2$ ✓