

Write time-domain expression for fifth-harmonic current in expression for i_o .

ans: $i_{o5}(t) = -6.4 \cos(50kt) \text{ A}$

soln: Fourier series for triangular wave such as $i_g(t)$ from inside back cover of Text:

$$i_g(t) = \frac{8A}{\pi^2} \sum_{\substack{k \text{ odd} \\ k > 0}}^{\infty} \left[\frac{1}{k^2} \sin\left(\frac{k\pi}{2}\right) \right] \sin k\omega_0 t \text{ A}$$

here, $A = 30\pi^2$ and $\omega_0 = \frac{2\pi}{T} = \frac{2\pi}{0.2\pi \text{ ms}} = 10\text{k rad/s}$.

We want the phasor for the 5th harmonic in $i_g(t)$:

$$k=5: i_{g5}(t) = \frac{8A}{\pi^2} \frac{1}{5^2} \sin\left(\frac{5\pi}{2}\right) \sin(5\omega_0 t) \text{ A}$$

Now $\sin\left(\frac{5\pi}{2}\right) = \sin\left(2\pi + \frac{\pi}{2}\right) = \sin\left(\frac{\pi}{2}\right) = 1$

$$\therefore i_{g5}(t) = \frac{8A}{\pi^2} \frac{1}{5^2} \cdot 1 \cdot \sin(5\omega_0 t) \text{ A}$$

$$= \frac{8 \cdot 30\pi^2}{\pi^2} \frac{1}{5^2} \sin(50kt) \text{ A}$$

$$= 9.6 \sin(50kt) \text{ A}$$

Phasor: $I_{g5} = 9.6 \angle -90^\circ \text{ A}$ ($P[\sin wt] = 1 \angle -90^\circ$)

Next, we find the transfer function, $H(j\omega)$:


$$H(j\omega) \equiv \frac{I_o}{I_g}$$

We have a current divider with 3 legs. We have a divider formula for 2 legs, but not 3. The formula for 3 legs is NOT $\frac{z_1 + z_3}{z_1 + z_2 + z_3}$ where


$$z_1 = 800\Omega \quad z_2 = 200\Omega + j\omega 20\text{mH} \quad z_3 = 1/j\omega 25\text{nF}$$

first

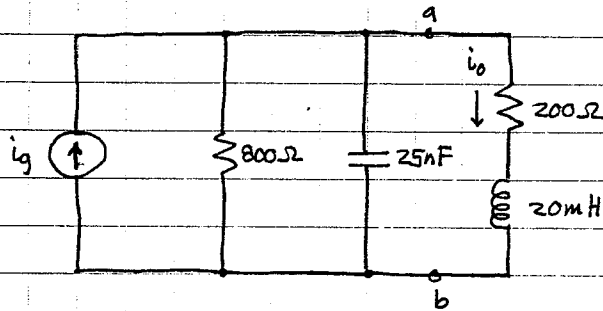To be safe, we rearrange the circuit by exchanging the 2nd leg (z_2) and the 3rd leg (z_3). This is allowed because both are across the rails:



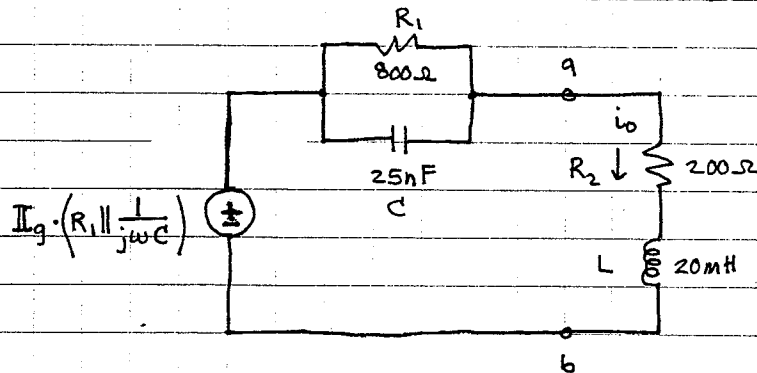The second step is to use a Thevenin equivalent for the circuit to the left of terminals a, b:



$$I_o = \frac{V}{z_{tot}} = \frac{I_g \cdot \left(R_1 \parallel \frac{1}{j\omega C} \right)}{\left(R_1 \parallel \frac{1}{j\omega C} \right) + R_2 + j\omega L}$$

$$H(j\omega) = \frac{I_o}{I_g} = \frac{R_1 \parallel 1/j\omega C}{(R_1 \parallel 1/j\omega C) + R_2 + j\omega L}$$

$$R_1 \parallel 1/j\omega C = \frac{R_1 / j\omega C}{R_1 + 1/j\omega C} = \frac{R_1}{1 + j\omega R_1 C}$$

$$\therefore H(j\omega) = \frac{\frac{R_1}{1 + j\omega R_1 C}}{\frac{R_1}{1 + j\omega R_1 C} + R_2 + j\omega L} = \frac{R_1}{R_1 + (R_2 + j\omega L)(1 + j\omega R_1 C)}$$

$$= \frac{R_1}{R_1 + R_2 + j\omega(L + R_2 R_1 C) + (j\omega)^2 L R_1 C}$$

$$= \frac{1}{R_1 + R_2 + j\omega \left(\frac{L}{R_1} + R_2 C \right) + (j\omega)^2 LC}$$

$$H(j\omega) = \frac{1/LC}{\frac{R_1 + R_2}{R_1 LC} + j\omega \left(\frac{1}{R_1 C} + \frac{R_2}{L} \right) + (j\omega)^2}$$

5th harmonic, $k=5$: $H(j5\omega_0) = H(j50k)$.

Note: ω_0 from period of triangular wave $\neq \frac{1}{\sqrt{LC}}$.
Thus, ω_0 NOT center frequency.

$$H(j50k) = \frac{1/20m25n}{\frac{800 + 200}{20m25n} + j50k \left(\frac{1}{800 \cdot 25n} + \frac{200}{20m} \right) + (j50k)^2}$$

$$= \frac{2G}{\frac{20kG}{800} + j50k \left(\frac{1}{20\mu} + 10k \right) + (j50k)^2}$$

$\frac{1}{20\mu} = 50k$

$$= \frac{2G}{2.5G + j3G - 2.5G} = \frac{2}{j3} = -j\frac{2}{3}$$

$$H(j5\omega_0) = -j\frac{2}{3} = \frac{2}{3} \angle -90^\circ$$

$$\text{We have } \mathbb{I}_{o5} = \mathbb{I}_{g5} \cdot H(j5\omega_0)$$

$$" = 9.6 \angle -90^\circ \cdot \frac{2}{3} \angle -90^\circ \text{ A}$$

$$\therefore \mathbb{I}_{o5} = 6.4 \angle -180^\circ \text{ A}$$

Take inverse phasor to get $i_{o5}(t)$:

$$i_{o5}(t) = 6.4 \cos(5\omega_0 t - 180^\circ) \text{ A}$$

$$= -6.4 \cos(5\omega_0 t) \text{ A} \quad 180^\circ \Rightarrow \text{mult by } -1$$

$$i_{o5}(t) = -6.4 \cos(50kt) \text{ A}$$