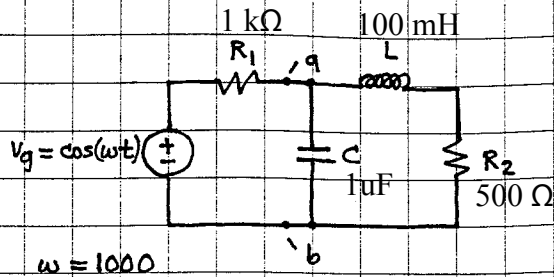


ex:



Draw a diagram of the frequency-domain representation of the circuit shown.

sol'n: We must: 1) Write sources as phasors  
2) Write R, L, C's as complex impedances


Impedances:  $Z_R = R$      $Z_L = j\omega L$      $Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$

$$j\omega L = j \cdot 1000 \cdot 0.1 = j100 \Omega$$

$$\frac{1}{j\omega C} = \frac{-j}{1000 \cdot 10^{-6}} = -j1k \Omega$$

R's are just the given R values.

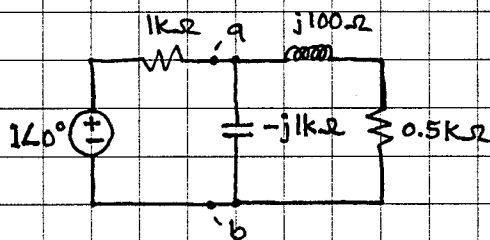$\mathcal{P}\{V_g\} \equiv$  phasor for source  $= \mathcal{P}\{\cos(\omega t)\} = 1e^{j0} = 1\angle 0^\circ$



Find an equivalent impedance at the points a-b looking to the right, and specify the resistance (i.e. real part) and reactance (i.e. imaginary part) of this impedance.

$$Z_{ab} = Z_C \parallel (Z_L + Z_R) = -j1k \Omega \parallel (j0.1k \Omega + 0.5k \Omega)$$

$$= 1k \Omega \cdot -j \parallel (j0.1 + 0.5)$$

$$\begin{aligned}Z_{ab} &= 1k\Omega \cdot \frac{-j \cdot (j0.1 + 0.5)}{-j + j0.1 + 0.5} \\&= 1k\Omega \cdot \frac{0.1 - j0.5}{0.5 - j0.9} \\&= 1k\Omega \cdot \frac{0.1 - j0.5}{0.5 - j0.9} \cdot \frac{0.5 + j0.9}{0.5 + j0.9} \\&= 1k\Omega \cdot \frac{(0.1)(0.5) - (-0.5)(0.9) + j[(0.1)(0.9) + (-0.5)(0.5)]}{0.5^2 + 0.9^2} \\&= 1k\Omega \cdot \frac{0.05 + 0.45 + j(0.09 - 0.25)}{0.25 + 0.81} \\&= 1k\Omega \cdot \frac{0.5 - j0.16}{1.06} \\&= 1k\Omega \cdot 0.47 - j0.15 \\Z_{ab} &= 0.47k\Omega - j0.15k\Omega \\&\quad \swarrow \quad \quad \quad \swarrow \\&\quad \text{resistance} \quad \quad \text{reactance}\end{aligned}$$