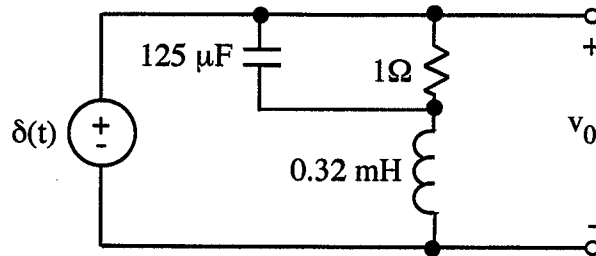



3.10.1 For the circuit illustrated below, write a numerical time-domain expression for $v_0(t)$ where $t > 0$. There is no energy stored in the circuit initially.



Answer: $v_0(t) = \left[\delta(t) - \frac{25}{3} k e^{-4kt} \sin(3kt) \right] u(t) \text{ V}$

Solution:

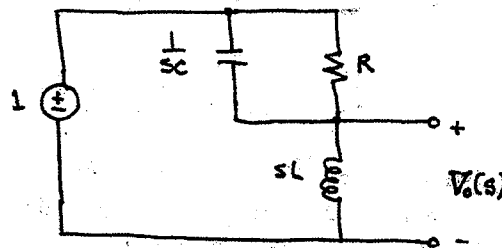s-domain model: $\mathcal{L}\{\delta(t)\} = 1$



v-divider: $V_0(s) = \frac{sL}{sL + R \parallel \frac{1}{sC}} \quad R \parallel \frac{1}{sC} = \frac{R/sC}{R + 1/sC} = \frac{R}{1 + sRC}$

$$\frac{1}{RC} = \frac{1}{1 \cdot \frac{125}{10^{-6}}} = 8k$$

$$\frac{1}{LC} = \frac{1}{0.32m \cdot \frac{125}{10^{-6}}} = \frac{1}{0.04}$$

or $\frac{1}{LC} = 25M$

$$\left(\frac{1}{2RC}\right)^2 = (4k)^2 = 16M$$

$$= \frac{sL}{sL + \frac{R}{1 + sRC}} = \frac{sL(1 + sRC)}{sL(1 + sRC) + R}$$

$$= \frac{sL + s^2 LRC}{sL + s^2 LRC + R} = \frac{s^2 + \frac{1}{RC} s}{s^2 + \frac{1}{RC} s + \frac{1}{LC}}$$

$$= 1 - \frac{1/LC}{s^2 + \frac{1}{RC} s + \frac{1}{LC}}$$

$$(s+a)^2 + \omega^2 = s^2 + 2as + a^2 + \omega^2$$

Now, $a = \frac{1}{2RC} \quad \omega^2 = \frac{1}{LC} - \left(\frac{1}{2RC}\right)^2$

$$a = 4k$$

$$\omega = 3k$$

Now we use $\mathcal{L}^{-1} \left\{ \frac{\omega}{(s+a)^2 + \omega^2} \right\} = e^{-at} \sin(\omega t)$. We write

$$V_o(s) = 1 - \frac{1/LC}{\omega} \frac{\omega}{(s+a)^2 + \omega^2} = 1 - \frac{25M}{3k} \frac{3k}{(s+4k)^2 + (3k)^2}$$

$$\therefore v_o(t) = \left[\delta(t) - \frac{25M}{3} k e^{-4kt} \sin(3kt) \right] u(t) \quad V$$

Note: $\mathcal{L}^{-1} \{ 1 \} = \delta(t)$.