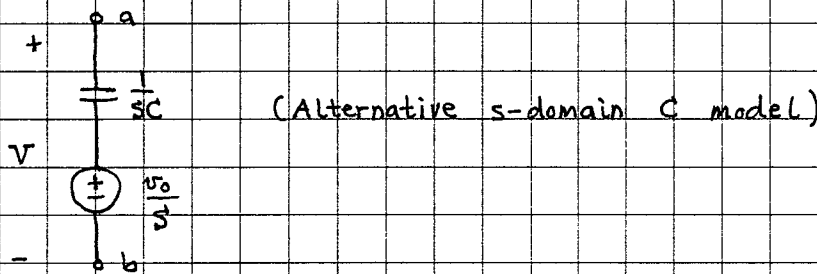


Find Thévenin equivalent of s-domain C model, above.

ans:



sol'n:  $V_{Th} =$  open circuit  $V$ , (i.e. nothing else connected from a to b)

$$V_{Th} = C v_0 \cdot \frac{1}{sC} \quad (\text{from } V = I Z)$$

$$= \frac{v_0}{s}$$

$Z_{Th} = Z_{a,b}$  with independent current source set to zero

$$Z_{Th} = \frac{1}{sC} \quad (\text{or we could use } Z_{Th} = Z_{Norton}, \text{ and given circuit is in Norton form})$$

