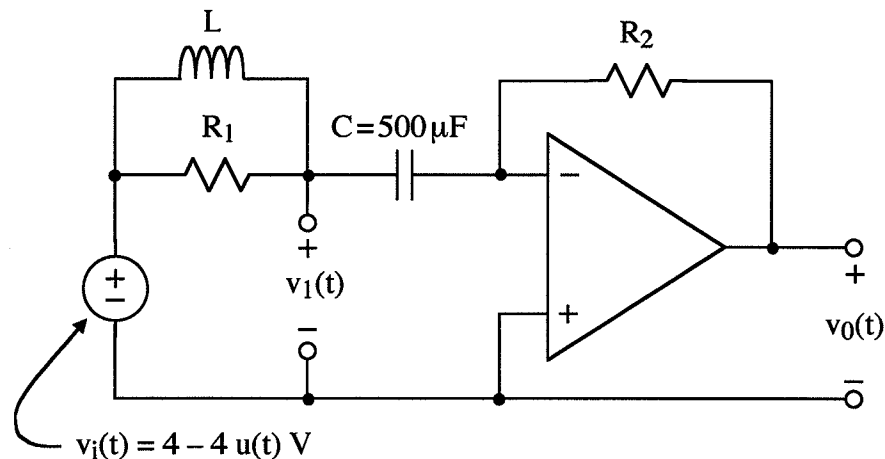


EX:



The Laplace transform of  $v_0(t)$  for the above circuit is as follows:

$$V_0(s) = 4V \cdot \frac{R_2}{R_1} \cdot \frac{s + \frac{R_1}{L}}{s^2 + \frac{1}{R_1 C}s + \frac{1}{LC}}$$

Choose numerical values for  $R_1$  and  $L$  to make

$$v_1(t) = v_m e^{-\alpha t} \cos(\beta t + \varphi)$$

where  $\alpha = \beta = 100 \text{ rad/s}$ .

sol'n: We first observe that  $\cos(\beta t + \varphi)$  is the same as a cosine of frequency  $\beta$  plus a sine of frequency  $\beta$ :

$$\cos(\beta t + \varphi) = \cos(\varphi) \cos(\beta t) - \sin(\varphi) \sin(\beta t)$$

Thus, we may rewrite  $v_1(t)$  as follows:

$$v_1(t) = v_m \cos(\varphi) e^{-\alpha t} \cos(\beta t) - v_m \sin(\varphi) e^{-\alpha t} \sin(\beta t)$$


Taking the Laplace transform, we have

$$\mathcal{L}\{v_1(t)\} = V_1(s) = v_m \cos(\varphi) \frac{s + \alpha}{(s + \alpha)^2 + \beta^2} - v_m \sin(\varphi) \frac{\beta}{(s + \alpha)^2 + \beta^2}$$

From the circuit diagram, we see that  $V_i(s)$  is the s-domain voltage across C.

The initial condition on C, found using  $v_c(0^+) = v_c(0^-)$ , is  $v_c(t=0^-) = 4V$  (from  $v_i(t < 0) = 4V$ ).

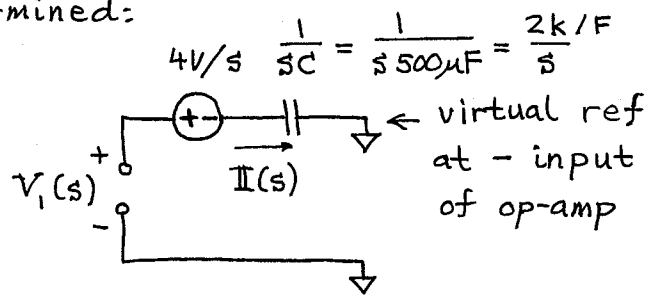This yields the following circuit for  $V_i(s)$  in which  $I(s)$  remains to be determined:



From the circuit diagram in the problem statement, we have current  $I(s)$  determining  $V_o(s)$ :

$$V_o(s) = -I(s)R_2$$

$$\text{or } I(s) = \frac{-V_o(s)}{R_2}$$

Using the expression for  $V_o(s)$  given in the problem statement, we have the following expression for  $I(s)$ :

$$I(s) = -\frac{4V}{R_1} \frac{s + R_1/L}{s^2 + \frac{1}{R_1C}s + \frac{1}{LC}}$$

Now we can write the following eq'n:

$$\begin{aligned}
 V_1(s) &= \frac{4V}{s} + \mathbf{I}(s) \cdot \frac{1}{sC} \\
 &= \frac{4V}{s} + \frac{-4V}{R_1} \frac{s + R_1/L}{s^2 + \frac{1}{R_1C}s + \frac{1}{LC}} \cdot \frac{1}{sC} \\
 &= \frac{4V \cdot R_1C(s^2 + s/R_1C + 1/LC) - 4V(s + R_1/L)}{s \cdot R_1C(s^2 + s/R_1C + 1/LC)} \\
 &= \frac{4V \cdot R_1C s^2}{s \cdot R_1C(s^2 + s/R_1C + 1/LC)} \\
 &= 4V \cdot \frac{s}{s^2 + \frac{1}{R_1C}s + \frac{1}{LC}}
 \end{aligned}$$

To match this to the symbolic form of  $V_1(s)$  given earlier, we must have the same denominator:

$$\begin{aligned}
 s^2 + \frac{1}{R_1C}s + \frac{1}{LC} &= (s + \alpha)^2 + \beta^2 \\
 \text{"} &= s + 2\alpha s + \alpha^2 + \beta^2
 \end{aligned}$$

Note: We must also match numerators,  
 $4V \cdot s = V_m \cos(\varphi)(s + \alpha) - V_m \sin(\varphi)\beta$ ,  
 but this will be possible given  
 arbitrary  $V_m$  and  $\varphi$ .

By matching the denominators, we have  
 the following eq'ns:

$$\frac{1}{R_1 C} = 2\alpha \quad \text{where } \alpha = 100 \text{ rad/s}$$

$$C = 500 \mu\text{F}$$

$$\frac{1}{LC} = \alpha^2 + \beta^2 \quad \text{where } \beta = 100 \text{ rad/s}$$

Solving for  $R_1$  and  $L$ , we have the following:

$$R_1 = \frac{1}{2\alpha \cdot C} = \frac{1}{2(100) \cdot 500 \mu} = 10 \Omega$$

$$L = \frac{1}{C(\alpha^2 + \beta^2)} = \frac{1}{500 \mu (100^2 + 100^2)} = 100 \text{ mH}$$