

Find $v_o(t)$.


ans:

sol'n: Since the source, $i_g(t)$, has a constant value for a long time before $t=0$, L will act like a wire at $t=0^-$. Thus, all of the current from $i_g(t)$ will flow thru the L at $t=0^-$, and $i_L(0^-) = 2A$.

Our *s*-domain model for L :



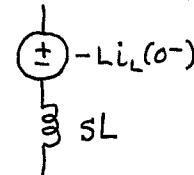Note: We choose this model for convenience, (in that we may combine this current source with $i_g(t)$). We could have chosen an alternative model consisting of a voltage source in series with sL :



Our next step is to find the Laplace transform of $i_g(t)$.

For $t > 0$, we have $i_g(t) = 4At[u(t) - u(t-1)]$

We write $i_g(t)$ in a form that allows us to use the time-delay identity for Laplace transforms:

$$\mathcal{L}\{f(t-a)u(t-a)\} \text{ where } a > 0 = e^{-as}\mathcal{L}\{f(t)u(t)\}$$

We proceed to find a way to write $-4At \cdot u(t-1)$ as a function of $(t-1)$:


$$\begin{aligned} -4At \cdot u(t-1) &= -4A(t-1+1) \cdot u(t-1) \\ &= -4A[(t-1)+1]u(t-1) \\ &\equiv f(t-1)u(t-1) \end{aligned}$$

$$\begin{aligned} \text{where } f(t-1) &= -4A[(t-1)+1] \\ \therefore f(t) &= -4A[t+1] \end{aligned}$$

$$\text{Thus, } \mathcal{L}\{i_g(t)\} \equiv I_g(s) = \mathcal{L}\{4Atu(t)\} + e^{-s}\mathcal{L}\{-4A(t+1)u(t)\}$$

$$\text{or } I_g(s) = 4A\left(\frac{1}{s^2} - e^{-s}\left[\frac{1}{s^2} + \frac{1}{s}\right]\right)$$

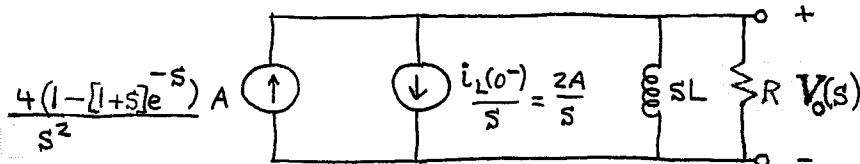Combining results gives us the s-domain model:



$$\text{We have } V_o(s) = I_{\text{Tot}}(s) \cdot sL \parallel R = I_{\text{Tot}}(s) \cdot \frac{s \cdot R}{s + R/L}$$

$$\text{where } I_{\text{Tot}}(s) = \frac{4A(1 - [1+s]e^{-s})}{s^2} - \frac{2A}{s}$$

Multiplying thru, we have the following for $V_o(s)$:

$$V_o(s) = \frac{4A(1-[1+s]e^{-s})R}{s(s+R/L)} - \frac{2A R}{s+R/L}$$

Using $R = 5\Omega$ and $R/L = 5\Omega/250mH = 20 s^{-1}$:

$$V_o(s) = \frac{20V(1-e^{-s})}{s(s+20)} - \frac{20Ve^{-s}}{s+20} - \frac{10V}{s+20}$$

For the first term, we use partial fractions:

$$\frac{1}{s(s+20)} = \frac{K_1}{s} + \frac{K_2}{s+20}$$

$$\text{where } K_1 = s \cdot \left. \frac{1}{s(s+20)} \right|_{s=0} = \frac{1}{20}$$

$$K_2 = (s+20) \left. \frac{1}{s(s+20)} \right|_{s=-20} = -\frac{1}{20}$$

$$\therefore V_o(s) = \frac{1V(1-e^{-s})}{s} - \frac{1V(1-e^{-s})}{s+20} - \frac{20Ve^{-s}}{s+20} - \frac{10V}{s+20}$$

From the delay identity, $\mathcal{L}^{-1}\left\{\frac{e^{-s}}{s+a}\right\} = e^{-a(t-1)} u(t-1)$.

$$\therefore v_o(t) = 1V u(t) - 1V u(t-1)$$

$$-1Ve^{-20t} u(t) + 1Ve^{-20(t-1)} u(t-1)$$

$$-20Ve^{-20(t-1)} u(t-1) - 10Ve^{-20t} u(t)$$

