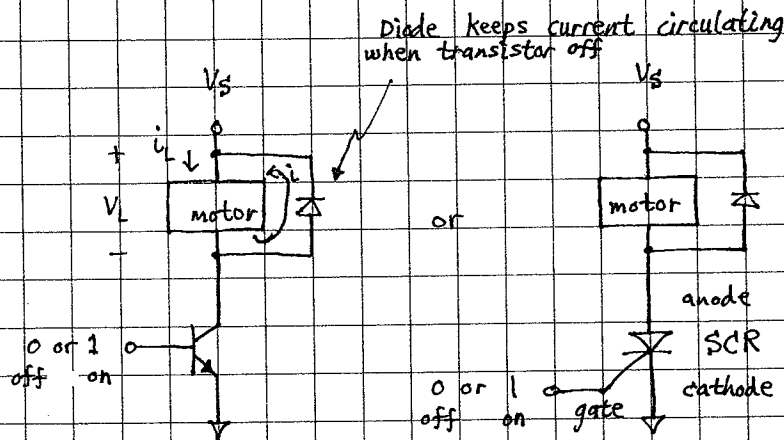


Switching Electronics

- Use switching device (e.g., transistor or SCR) that acts as short when turned on.
- To minimize power loss in switch, use in situation where applying V step = V_s to load is possible, (without having $i_L \rightarrow \infty$).

In particular, if load = L we can apply step V . If load = C we cannot apply step V , (as that would imply $i = \infty$).

Conclusion: switching circuits are effective for motors.



- When transistor SCR is on, it acts like a closed switch (with $R \approx 0.2$).
- SCR acts like a self latching relay. Turn on SCR with current pulse on gate terminal, and it stays on as long as voltage drop from anode to cathode is positive.

