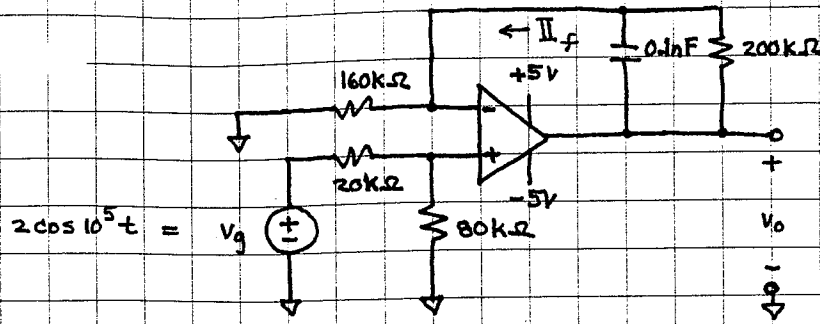


ex:



The op-amp is ideal

- a) Find the steady-state expression for $v_o(t)$.
(In other words, solve in frequency domain to find sinusoidal expression for $v_o(t)$.)

sol'n: Same approach as with R's and DC sources, but use phasors for sources and complex impedances for L's and C's.

We still have rules: $V_n = V_p$ for phasor voltages and - and + inputs, and $I_n = I_p = 0$ for phasor currents into - and + inputs.

First, we find V_p , (as always with op-amp probs):

$$V_g = 2 \angle 0^\circ \quad V_p = V_g \cdot \frac{80k\Omega}{80k\Omega + 20k\Omega} = 2 \angle 0^\circ \cdot \frac{4}{5} = 1.6 \angle 0^\circ$$

$$V_n = V_p = 1.6 \angle 0^\circ$$

Now equate feedback current, I_f , with current in $160k\Omega$, since $I_n = 0$.

$$I_f = \frac{V_o - V_n}{200k\Omega \parallel Z_c} \quad \text{where } Z_c = \frac{-j}{\omega C} = \frac{-j}{10^5 \cdot 0.1n} = -j100k\Omega$$

$$\text{and } I_f = \frac{V_n}{160k\Omega} \quad \therefore \frac{V_o - V_n}{200k\Omega \parallel Z_c} = \frac{V_n}{160k\Omega}$$

$$\therefore V_o = V_n \left(1 + \frac{200\text{k}\Omega \parallel Z_c}{160\text{k}\Omega} \right)$$

$$200\text{k}\Omega \parallel Z_c = 200\text{k}\Omega \parallel -j100\text{k}\Omega = 100\text{k}\Omega \cdot 2 \parallel -j$$

$$= 100\text{k}\Omega \cdot \frac{-2j}{2-j} \cdot \frac{2+j}{2+j} = 100\text{k}\Omega \cdot \frac{2-j4}{2^2+1^2}$$

$$= 20\text{k}\Omega \cdot (2-j4)$$

$$= 40\text{k}\Omega - j80\text{k}\Omega$$

$$V_o = 16 \angle 0^\circ \left(1 + \frac{40\text{k}\Omega - j80\text{k}\Omega}{160\text{k}\Omega} \right) \text{ V}$$

$$= 16 \angle 0^\circ \frac{160\text{k}\Omega + 40\text{k}\Omega - j80\text{k}\Omega}{160\text{k}\Omega} \text{ V}$$

$$= \frac{200\text{k}\Omega - j80\text{k}\Omega}{160\text{k}\Omega} = 2 - j0.8 \text{ V}$$

$$= \sqrt{2^2 + 0.8^2} e^{j \tan^{-1} \frac{-0.8}{2}} = 2.15 e^{-j21.8^\circ} \text{ V or } 2.5 \angle -21.8^\circ \text{ V}$$

$$v_o(t) = 2.15 \cos(\omega t - 21.8^\circ) \text{ V} \quad \omega = 10^5 \text{ since } v_g = 2 \cos 10^5 t$$

- b) How large can amplitude of v_g be before the amplifier saturates? (i.e. before $v_o(t)$ exceeds $\pm 5\text{V}$ at some point during one cycle of sinusoid)

sol'n: The principle of (linear) superposition tells us that the magnitude of $v_o(t)$ is directly proportional to the magnitude of $v_g(t)$. Furthermore, scaling $v_g(t)$'s magnitude leaves phase relationships unaffected.

$$\text{For } v_g = 2 \cos 10^5 t \text{ we have } v_o(t) = 2.15 \cos(\omega t - 21.8^\circ) \text{ V}$$

\therefore for $v_o(t) = 5 \cos(\omega t - 21.8^\circ) \text{ V}$ we have

$$v_g = \frac{5 \cdot 2 \cos 10^5 t}{2.15} = 4.65 \cos 10^5 t \text{ V} \therefore \underline{4.65 \text{ V max}}$$