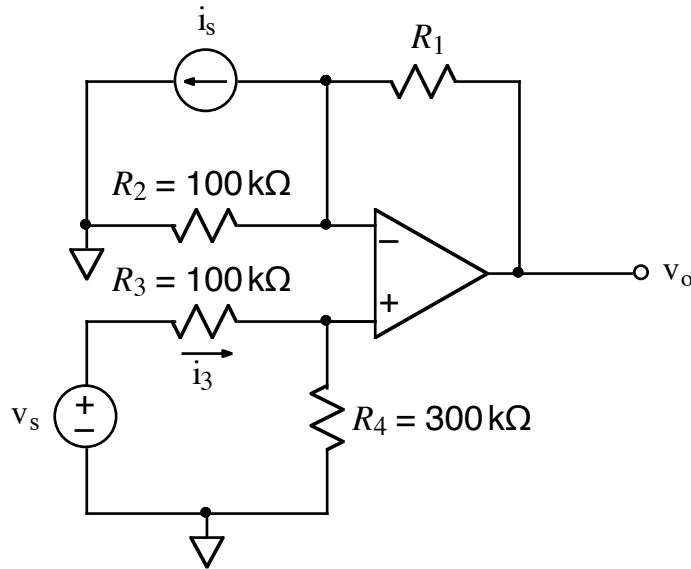


Ex:



- The above circuit operates in linear mode. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_s , v_s , R_1 , R_2 , R_3 , and R_4 .
- If $i_s = 0$ A, find the value of R_1 that will yield an output voltage of $v_o = 1$ V when $v_s = 1$ V.
- Using the value of R_1 from part (b), find the value of i_s that will yield $v_o = 1$ V when $v_s = 0$ V.
- Using the value of R_1 from part (b), calculate the input resistance, $R_{in} = v_s/i_3$, seen by the v_s source.

Sol'n: a) We use superposition and turn on one independent source at a time.

Case I: v_s on, i_s off

i) Find v_+ : Use v-divider
(+ input of
op-amp)
$$v_+ = v_s \frac{R_4}{R_3 + R_4}$$


ii) Set $v_- = v_+ = v_s \frac{R_4}{R_3 + R_4}$

$$\text{or } -v_{o1} = -v_- \left(\frac{R_1}{R_2} + 1 \right)$$

$$\text{or } v_{o1} = v_- \left(1 + \frac{R_1}{R_2} \right)$$

$$\text{or } v_{o1} = v_s \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_1}{R_2} \right)$$

Case II: v_s off, i_s on

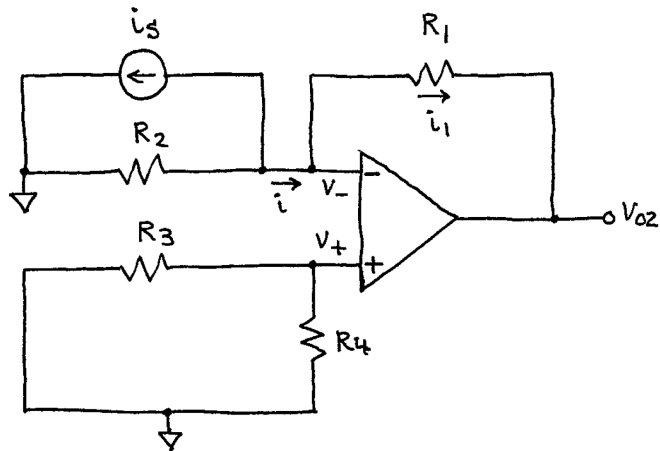


i) Find v_+ : $v_+ = 0V$ since no current in R_3 or R_4

ii) Set $v_- = v_+ = 0V$

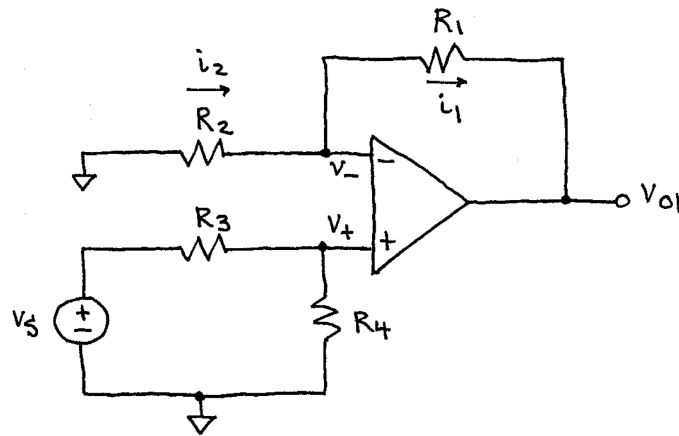iii) Calculate i flowing toward $-$ input from left. (Note how circuit is drawn to show i as total current on left side.)

$$i = -i_s + \frac{0V - 0V}{R_2} = -i_s$$



iii) Calculate current i_2 flowing toward - input from the left. Use node voltage v_- .

$$i_2 = \frac{0V - v_-}{R_2} = -\frac{v_-}{R_2} = -\frac{v_s \frac{R_4}{R_3 + R_4}}{R_2}$$

iv) Calculate current i_1 flowing in feedback. Use node voltage v_- .

$$i_1 = \frac{v_- - v_{01}}{R_1} = \frac{v_s \frac{R_4}{R_3 + R_4} - v_{01}}{R_1}$$

v) Since no current flows into the op-amp, set $i_1 = i_2$ and solve for v_{01} .

$$\frac{v_- - v_{01}}{R_1} = -\frac{v_-}{R_2}$$

$$\text{or } v_- - v_{01} = -v_- \frac{R_1}{R_2}$$

iv) Calculate i_1 flowing in feedback.

$$i_1 = \frac{V_- - V_{o2}}{R_1} = -\frac{V_{o2}}{R_1}$$

v) Since no current flows into op-amp, set $i = i_1$. Then solve for V_{o2} .

$$i = -i_5 = -\frac{V_{o2}}{R_1} = i_1$$

$$\text{or } V_{o2} = i_5 R_1$$

Sum V_{o1} and V_{o2} to find V_o :

$$V_o = V_{o1} + V_{o2} = V_s \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_1}{R_2} \right) + i_5 R_1$$

b) $i_5 = 0A$ and $V_o = 1V$ for $V_s = 1V$:

$$V_o = 1V = V_s \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_1}{R_2} \right)$$

$$1V = 1V \frac{300k\Omega}{100k\Omega + 300k\Omega} \left(1 + \frac{R_1}{100k\Omega} \right)$$

$$\text{or } 1 = \frac{3}{4} \left(1 + \frac{R_1}{100k\Omega} \right)$$

$$\text{or } 1 + \frac{R_1}{100k\Omega} = \frac{4}{3} \quad \text{or } \frac{R_1}{100k\Omega} = \frac{1}{3}$$

$$\text{or } R_1 = \frac{100 \text{ k}\Omega}{3} \approx 33 \text{ k}\Omega$$

$$\text{c) } v_o = 1 \text{ V and } v_s = 0 \text{ V with } R_1 = \frac{100 \text{ k}\Omega}{3} :$$

$$v_o = 1 \text{ V} = i_s R_1 = i_s \frac{100 \text{ k}\Omega}{3}$$

$$\text{or } i_s = \frac{1 \text{ V} \cdot 3}{100 \text{ k}\Omega} = 30 \mu\text{A}$$

$$\text{d) } R_{in} = \frac{v_s}{i_s} = \frac{v_s}{\frac{v_s}{R_3 + R_4}} = R_3 + R_4$$

$$R_{in} = 100 \text{ k}\Omega + 300 \text{ k}\Omega = 400 \text{ k}\Omega$$