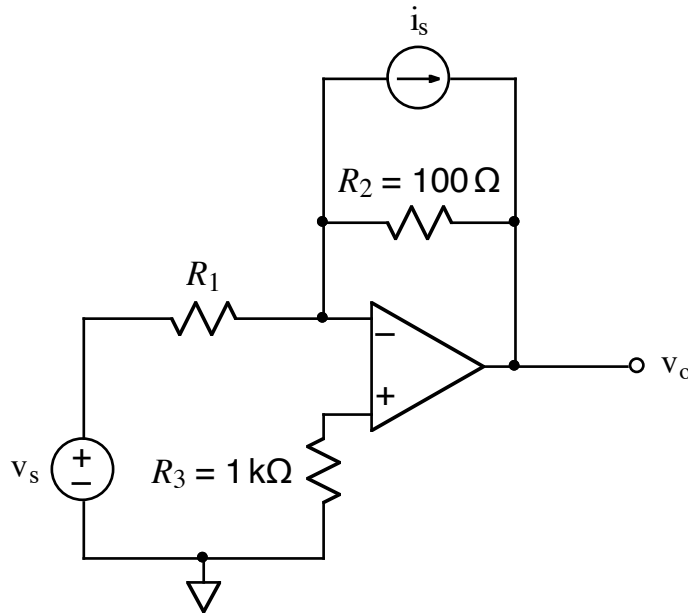


Ex:




Rail voltage =  $\pm 10 \text{ V}$

- The above circuit operates in linear mode. Derive a symbolic expression for  $v_o$ . The expression must contain not more than the parameters  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ , and  $R_3$ .
- If  $i_s = 0 \text{ A}$ , find the value of  $R_1$  that will yield an output voltage of  $v_o = -2 \text{ V}$  when  $v_s = 1 \text{ V}$ .
- Using the value of  $R_1$  from part (a), find the value of  $i_s$  that will yield  $v_o = 0 \text{ V}$  when  $v_s = 1 \text{ V}$ .
- Using the value of  $R_1$  from part (a), calculate the input resistance,  $R_{in} = v_s/i_1$ .

Sol'n: We use superposition to find  $v_o$ .  
We turn on one independent source at a time

Case I:  $v_s$  on,  $i_s$  off

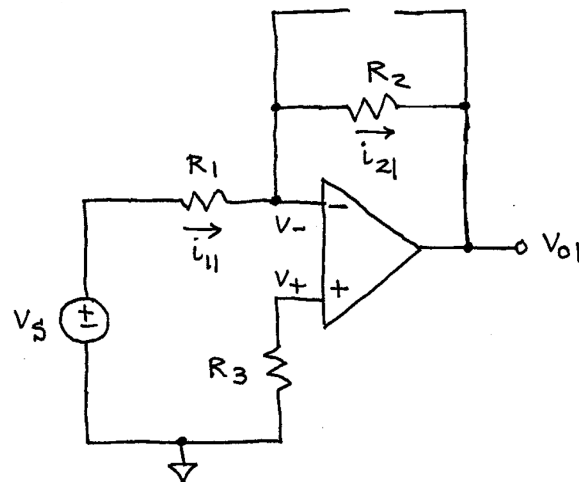

First, we find  $V_+$ :  $V_+ = 0V$  since no current flows into op-amp (or, therefore, thru  $R_3$ )

Second, we set  $V_- = V_+$ :  $V_- = 0V$

Third, we find an expression for  $i_{11}$  flowing toward - input from the left. We use  $V_-$  in this expression:

$$i_{11} = \frac{V_s - V_-}{R_1} = \frac{V_s}{R_1}$$

Fourth, we find an expression for  $i_{21}$ , the total feedback current, flowing thru  $R_2$ . We use  $V_-$  in this expression:


$$i_{21} = \frac{V_- - V_{o1}}{R_2} = -\frac{V_{o1}}{R_2}$$

Fifth, we set  $i_{11} = i_{21}$  (since no current flows into op-amp) and solve for  $V_{o1}$ :

$$\frac{V_s}{R_1} = -\frac{V_{o1}}{R_2}$$

$$\therefore V_{o1} = -V_s \frac{R_2}{R_1}$$

Case II:  $V_s$  off,  $i_s$  on

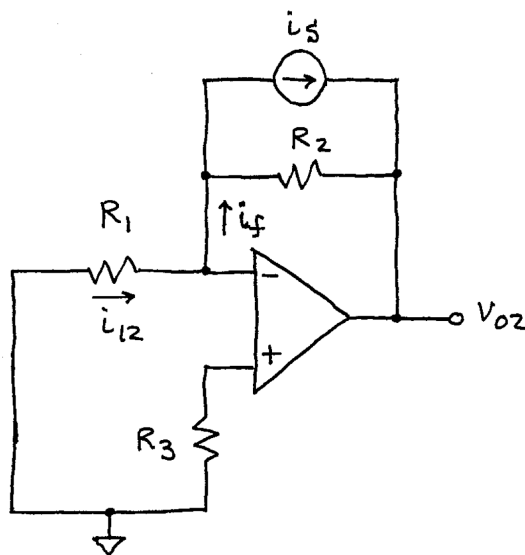

First, we find  $V_+$ :  $V_+ = 0V$  since no current flows in  $R_3$

Second, we set  $V_- = V_+$ :  $V_- = 0V$

Third, we find an expression for  $i_{12}$  flowing toward - input from left:

$$i_{12} = \frac{0V - 0V}{R_1} = 0A$$

Fourth, we find an expression for  $i_f$ , the total current flowing in the feedback:

$$i_f = \frac{0V - v_{o2}}{R_2} + i_s$$

Fifth, we set  $i_{R2} = i_f$  (since no current flows into op-amp) and solve for  $v_o$ :

$$0A = -\frac{v_{o2}}{R_2} + i_s$$

$$\therefore v_{o2} = i_s R_2$$

Now sum the results:  $v_o = v_{o1} + v_{o2}$

$$v_o = -v_s \frac{R_2}{R_1} + i_s R_2$$

b) If  $i_s = 0A$ , we have the first case analyzed in part (a):  $v_o = -v_s \frac{R_2}{R_1} = -2V$  (desired  $V$ )

For  $v_s = 1V$  and  $R_2 = 100\Omega$ , we have

$$R_1 = \frac{-1V}{-2V} 100\Omega = 50\Omega$$

c) Now we turn on  $i_s$  and keep  $v_s = 1V$ :

$$0V = v_o = -v_s \frac{R_2}{R_1} + i_s R_2 = -1V \frac{100\Omega}{50\Omega} + i_s 100\Omega$$

$$\text{or } i_s = -2V/100\Omega = -20\text{ mA}$$

$$d) \quad i_1 = \frac{V_s - V_-}{R_1} = \frac{V_s}{R_1}$$

$$\text{Thus } R_{in} \equiv \frac{V_s}{i_1} = R_1.$$