



a) Give power factor and reactive factor of each load.

Sol'n: $\omega = 2\pi f = 2\pi \cdot 60 = 377 \text{ rad/s}$

$$V = IZ \quad \therefore \angle V - \angle I = \theta_v - \theta_i = \angle Z$$

Load 1: $\angle 240\Omega + j70\Omega = \tan^{-1} 70/240 = 16.3^\circ$

power factor = $\cos 16.3^\circ = 0.96$ lagging

reactive factor = $\sin 16.3^\circ = 0.28$

Load 2: $\angle 160\Omega - j120\Omega = \tan^{-1} -120/160 = -36.9^\circ$

power factor = $\cos -36.9^\circ = 0.8$ leading

reactive factor = $\sin -36.9^\circ = 0.6$

Load 3: $\angle 30\Omega - j40\Omega = \tan^{-1} -40/30 = -53.1^\circ$

power factor = $\cos -53.1^\circ = 0.6$ leading

reactive factor = $\sin -53.1^\circ = 0.8$ lagging

b) Give power factor and reactive factor of total load.

Sol'n: $Z_{tot} = \frac{1}{\frac{1}{240 + j70} + \frac{1}{160 - j120} + \frac{1}{30 - j40}} \Omega$

$$= \frac{10^3 \cdot 7}{\frac{1}{24 + j7} + \frac{1}{16 - j12} + \frac{1}{3 - j4}}$$

$$= \frac{10^3}{\frac{24 - j7}{25^2} + \frac{16 + j12}{20^2} + \frac{3 + j4}{5^2}}$$

$$\begin{aligned}
 Z_{tot} &= \frac{10^{-2} \cdot 5^2 \cdot 5^2 \cdot 4^2}{(24-j7) \cdot 4^2 + (16+j12) \cdot 5^2 + (3+j4) \cdot 5^2 \cdot 4^2} \\
 &= \frac{10 \cdot 5^2 \cdot 5^2 \cdot 4^2}{384 + 400 + 1200 + j(-112 + 300 + 1600)} \\
 &= \frac{10 \cdot 5^2 \cdot 5^2 \cdot 4^2}{1984 + j1788} \\
 &= \frac{10 \cdot 5^2 \cdot 5^2 \cdot 4^2}{7133.200} \frac{1984 - j1788}{7133.200} \\
 &= 1.4 \cdot 10^{-2} \cdot (1984 - j1788) \\
 &= 1.4 \cdot 10^{-2} \cdot 2670.8 e^{-j42^\circ}
 \end{aligned}$$

$$Z_{tot} = 37.4 \angle -42^\circ$$

$$\therefore \theta_v - \theta_i = -42^\circ$$

$$\begin{aligned}
 \text{power factor} &= \cos -42^\circ = 0.74 \text{ leading} \\
 \text{reactive factor} &= \sin -42^\circ = -0.67
 \end{aligned}$$