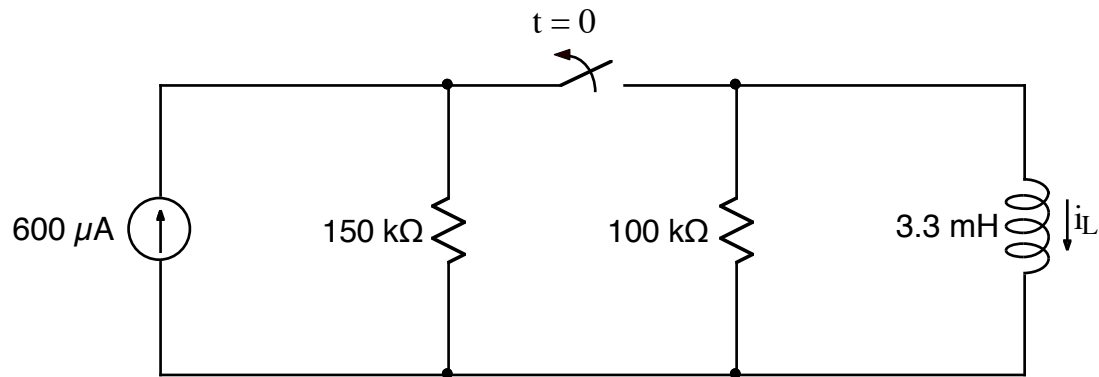


Ex:



After being closed for a long time, the switch opens at $t = 0$. Find $i_L(t)$ for $t > 0$.

sol'n: Use the general form of solution for RL problems:

$$i_L(t > 0) = i_L(t \rightarrow \infty) + [i_L(t = 0^+) - i_L(t \rightarrow \infty)]e^{-t/\tau_{Th}}$$

To find $i_L(0^+)$, we consider $t = 0^-$.


At $t = 0^-$, the circuit has reached stable values, and all time derivatives of i and v are zero. Thus,

$$v_L = L \frac{di_L}{dt} = L \cdot 0 = 0 \text{ and } L \text{ acts like a wire.}$$

Since the switch is closed at $t = 0^-$, we have a current source shorted by a wire.

We are only interested in the energy variable, $i_L(0^-)$. All other currents and voltages may change instantly when the switch opens.

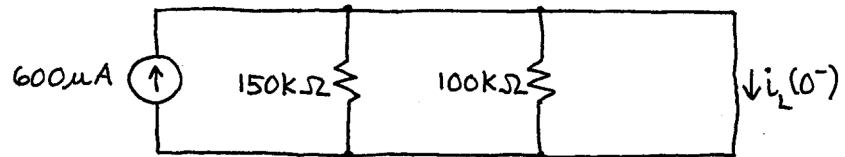
$t=0^-$: $L = \text{wire}$, switch closed, find $i_L(0^-)$



$i_L(0^-) = 600 \mu\text{A}$ since all the current will flow thru the $L = \text{wire}$

$i_L(0^+) = i_L(0^-)$ since energy variables (like i_L and v_L cannot change instantly

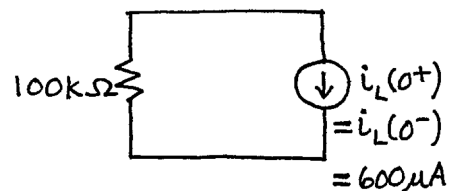
$t=0^+$: $L = \text{current source}$, $i_L(0^+) = i_L(0^-)$, switch open (left side of circuit disconnected)



$$i_L(0^+) = i_L(0^-) = 600 \mu\text{A}$$

Now we find $i_L(t \rightarrow \infty)$. As $t \rightarrow \infty$, the circuit again reaches stable values, and the L again acts like a wire.


$t \rightarrow \infty$:

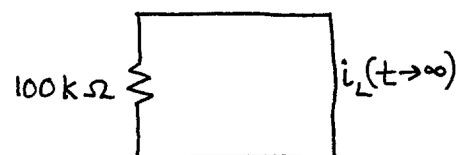

$i_L(t \rightarrow \infty) = 0$ since there is no power source.

The last quantity we need is R_{Th} , the Thevenin equivalent resistance of the circuit as seen from the terminals where the L is connected. In other words, we remove the L and find the Thevenin equivalent of the remaining circuit.

Since $t > 0$, the switch is open.

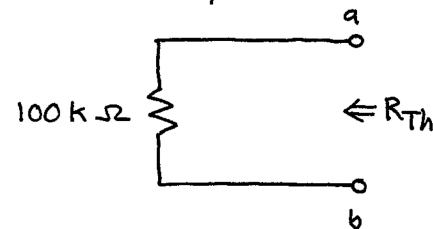

The circuit is already in Thevenin equivalent form with $V_{Th} = 0V$ and $R_{Th} = 100k\Omega$.

Thus, the time constant of the circuit is

$$\frac{L}{R_{Th}} = \frac{3.3 \text{ mH}}{100 \text{ k}\Omega} = \frac{33 \text{ mH}}{1 \text{ M}\Omega} = 33 \text{ ns}$$

Substituting values into the general form of solution, we have our desired answer:

$$i_L(t > 0) = 0 \text{ A} + (600 \mu\text{A} - 0 \text{ A}) e^{-t/33 \text{ ns}}$$

or

$$i_L(t > 0) = 600 \mu\text{A} \cdot e^{-t/33 \text{ ns}}$$