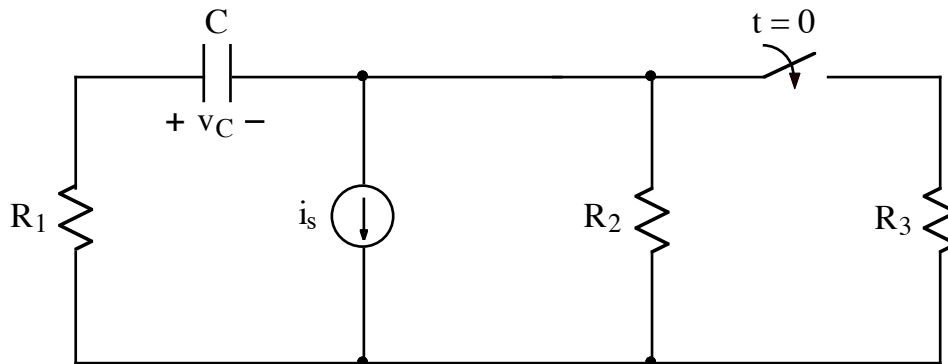



Ex:



After being open for a long time, the switch closes at $t = 0$. Write an expression for $v_C(t \geq 0)$ in terms of R_1 , R_2 , R_3 , i_s , and C .

Sol'n: At $t = 0^-$ the switch is open and $C = \text{open}$.

$t = 0^-$:

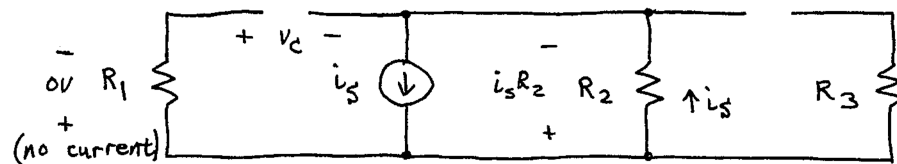


i_s flows thru R_2 producing v -drop $i_s R_2$.

Since there is no current in R_1 , this voltage appears across C .

$$v_C(0^-) = i_s R_2$$


Note that + sign of $i_s R_2$ v -drop connects to + sign of v_C thru R_1 ($0V$ drop \approx wire) and - sign of $i_s R_2$ v -drop connects to - sign of v_C thru wire.

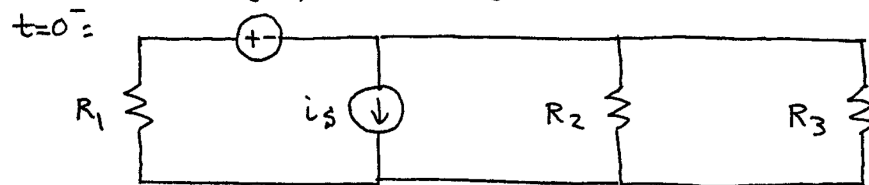At $t=0^+$, we treat C as v -source with value $v_C(0^+) = v_C(0^-)$. Switch is closed.
 $v_C(0^+) = v_C(0^-) = i_S R_2$



Since the value we need is $v_C(0^+)$, there is nothing further to solve.

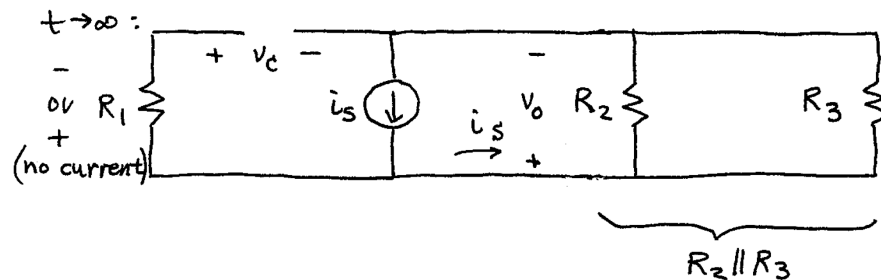For $t \rightarrow \infty$, we treat C as open, switch closed.




Now we have $v_C = i_S \cdot R_2 \parallel R_3$. This is the same as $t=0^-$ except that we have $R_2 \parallel R_3$ instead of R_2 .

$$v_C(t \rightarrow \infty) = i_S R_2 \parallel R_3$$

The time constant is $R_{TH}C$.

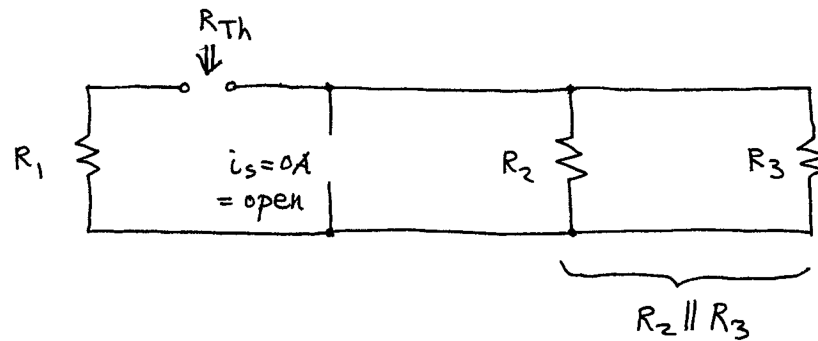We remove C and look into the circuit from terminals where C attaches. We also turn off i_S . What we see is R_{TH} .



We have $R_{Th} = R_1 + R_2 \parallel R_3$

Now plug terms into general sol'n:

$$v_c(t > 0) = v_c(t \rightarrow \infty) + [v_c(0^+) - v_c(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

Here, we have:

$$v_c(t > 0) = i_s \cdot R_2 \parallel R_3 + (i_s R_2 - i_s R_2 \parallel R_3) e^{-\frac{t}{(R_1 + R_2 \parallel R_3)C}}$$