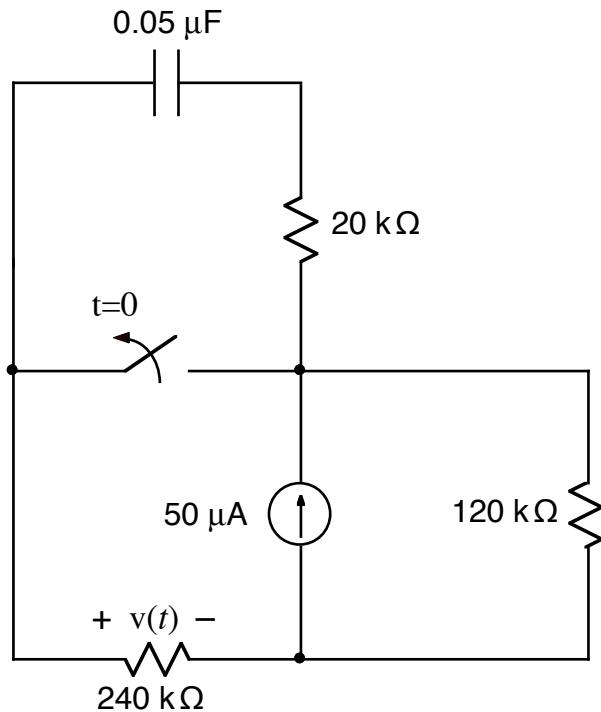


Ex:



Write a numerical expression for $v(t)$ for $t > 0$.

Sol'n: We use general form of solution for RC circuits.

$$v(t>0) = v(t \rightarrow \infty) + [v(0^+) - v(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

We find $v(0^+)$, $v(t \rightarrow \infty)$, and R_{Th} .


We start at $t=0^-$ to find voltage on C at $t=0^+$.

$t=0^-$: C acts like open circuit.
Switch is closed.

Switch creates a short circuit,
and $v_C(0^-) = 0V$.

$t = 0^+$: $v_C(0^+) = v_C(0^-) = 0V$ since v_C can't change instantly.

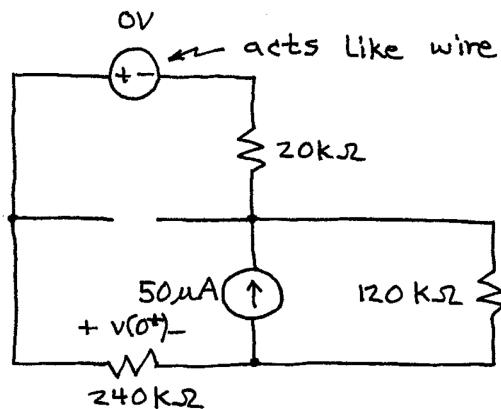We model C as voltage source of 0V. Thus, it acts like a wire.



This is a current-divider circuit with $20\text{k}\Omega + 240\text{k}\Omega = 260\text{k}\Omega$ on one side and $120\text{k}\Omega$ on the other side.

The current thru the $240\text{k}\Omega$ is

$$i(0^+) = 50\mu\text{A} \cdot \frac{120\text{k}\Omega}{20\text{k}\Omega + 240\text{k}\Omega + 120\text{k}\Omega}$$


$$i(0^+) = 50\mu\text{A} \cdot \frac{120\text{k}\Omega}{380\text{k}\Omega}$$

$v(0^+)$ from Ohm's Law is

$$v(0^+) = 50\mu\text{A} \cdot \frac{120\text{k}\Omega}{380\text{k}\Omega} \cdot 240\text{k}\Omega$$

$$v(0^+) = 6V \cdot \frac{12}{19}$$

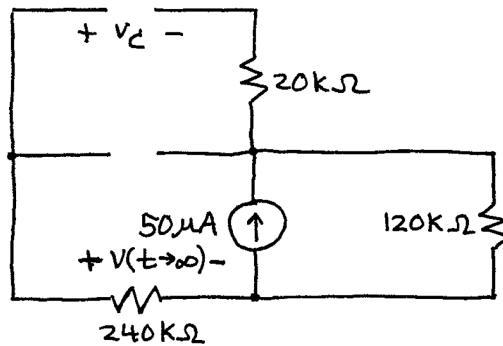
$t \rightarrow \infty$: Switch is open, $C = \text{open circuit}$.



No current can flow thru the $240\text{ k}\Omega$ resistor.

$$\therefore v(t \rightarrow \infty) = 0V$$

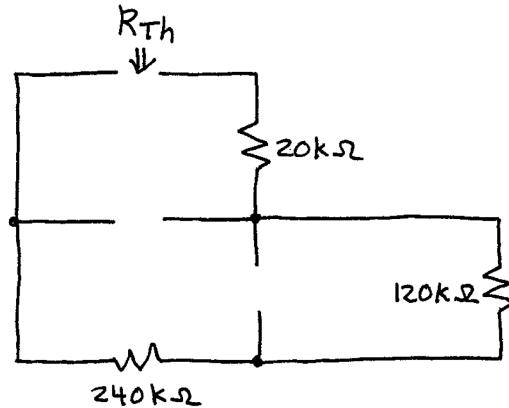R_{Th} : We look in from the terminals where C is connected, and we turn off the current source.



$$R_{Th} = 20\text{k}\Omega + 120\text{k}\Omega + 240\text{k}\Omega = 380\text{k}\Omega$$

The time constant is $R_{TH}C$:

$$\tau = 380 \text{ k}\Omega \cdot 0.05 \mu\text{F} = 19 \text{ ms}$$

Putting results together:

$$v(t > 0) = 0V + \left(6V \cdot \frac{12}{19} - 0V \right) e^{-t/19\text{ms}}$$

or

$$v(t > 0) = 6V \cdot \frac{12}{19} e^{-t/19\text{ms}} \doteq 3.8V e^{-t/19\text{ms}}$$