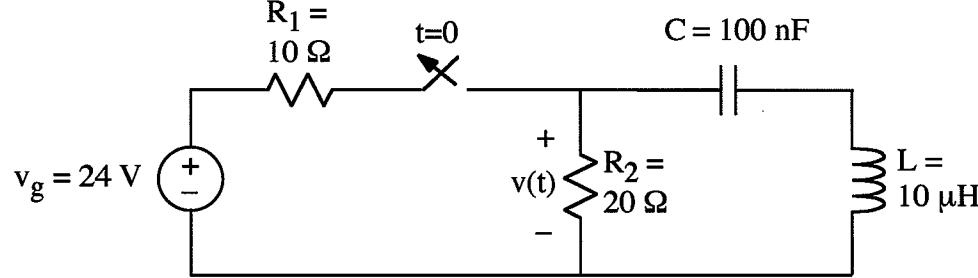


**Ex:**

After being closed for a long time, the switch opens at  $t = 0$ .

- State whether  $v(t)$  is underdamped, overdamped, or critically damped.
- Write a numerical time-domain expression for  $v(t)$ ,  $t > 0$ , the voltage across  $R_2$ . This expression must not contain any complex numbers.

sol'n: a) characteristic roots from series  $R_2 LC$  circuit after  $t = 0^+$ .

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}, \quad \alpha = \frac{R_2}{2L}, \quad \omega_0^2 = \frac{1}{LC}$$

$$\alpha = \frac{20 \Omega}{2 \cdot 10 \mu\text{H}} = 1 \text{ M r/s}$$

$$\omega_0^2 = \frac{1}{10 \mu\text{H} \cdot 100 \text{ nF}} = \frac{1}{1 \mu^2} \text{ r}^2/\text{s}^2 = (1 \text{ M r/s})^2$$

$$\sqrt{\alpha^2 - \omega_0^2} = \sqrt{(1 \text{ M r/s})^2 - (1 \text{ M r/s})^2} = 0$$

$\therefore$  The circuit is critically damped.


$$s = -\alpha = -1 \text{ M r/s}$$

b) Our sol'n is of form

$$v(t) = A_1 e^{st} + A_2 t e^{st} + (A_3 = 0) \text{ (no src as } t \rightarrow \infty)$$

Now find  $v(0^+)$  and  $\frac{dv(t)}{dt} \Big|_{t=0^+}$  from circuit.

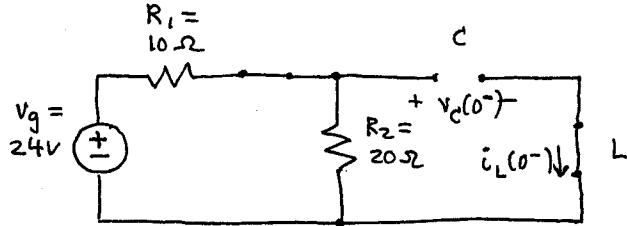Start at  $t=0^-$  when  $L=\text{wire}$ ,  $C=\text{open}$ .



Find  $i_L(0^-)$  and  $v_C(0^-)$ , (energy vars).


$i_L(0^-) = 0$  since  $C = \text{open}$

$$v_C(0^-) = v_{R_2} = \frac{v_g R_2}{R_1 + R_2} \quad v\text{-divider}$$

$$v_C(0^-) = 24V \cdot \frac{20}{10+20} = 16V$$

Now solve circuit at  $t=0^+$  with

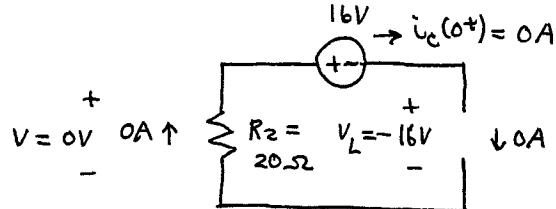$i_L(0^+) = i_L(0^-)$  and  $v_C(0^+) = v_C(0^-)$ :



We see that  $v(0^+) = 0V$ .

$$v(0^+) = A_1 \text{ from symbolic form.}$$

$\therefore A_1 = 0V$  matching circuit value to symbolic form

Now find  $\left. \frac{dv(t)}{dt} \right|_{t=0^+}$  from circuit.

We write  $v(t)$  in terms of  $i_L$  and  $v_C$ .  
 (Write an eq'n that is true for all  $t > 0$ .  
 Plug in specific values only after taking derivative.)

$$v(t) = -i_L R_2 \text{ since } i_L \text{ flows thru } R_2$$

$$\frac{dv(t)}{dt} = -R \frac{di_L}{dt} = -R \frac{v_L}{L} \text{ from } v_L = L \frac{di_L}{dt}$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0^+} = -R \frac{v_L(0^+)}{L} = \frac{20\Omega \cdot 16V}{10mH} \text{ for } t=0^+$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0^+} = 32 \text{ MV/s}$$

from symbolic form

$$\left. \frac{dv(t)}{dt} \right|_{t=0^+} = A_1 s e^{0^+} + A_2 e^{0^+} + A_3 \cancel{\cdot 0^+} \cancel{s_2 e^{0^+}}$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0^+} = A_1 s + A_2$$

Equate symbolic and circuit values.

$$A_1 s + A_2 = 32 \text{ MV/s}$$

From before,  $A_1 = 0$ .

Thus,  $A_2 = 32 \text{ MV/s}$

$$v(t) = 32 \frac{\text{MV}}{\text{s}} \cdot t \cdot e^{-1\text{Mt}}$$