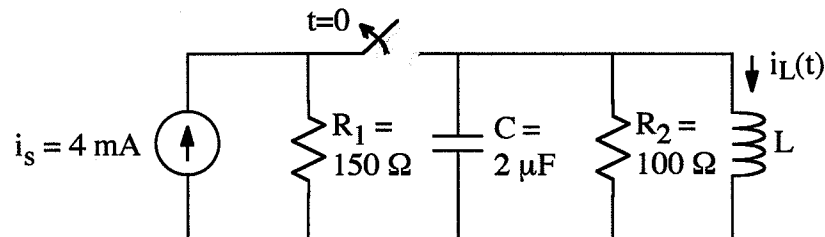


EX:



After being closed for a long time, the switch opens at $t = 0$.

- If $L = 125$ mH, find the characteristic roots, s_1 and s_2 , for the above circuit.
- If $L = 11.834$ mH, find the damping frequency, ω_d .
- Find the value of L that makes the circuit critically damped.

SOL'N: a) After $t=0$ we have parallel RLC.

From the differential eq'n for the parallel RLC with Ae^{st} substituted for the sol'n, we get the characteristic eq'n for the circuit:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

We get the characteristic roots by solving this quadratic eq'n.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{where } \alpha \equiv \frac{1}{2RC} \quad \omega_0^2 \equiv \frac{1}{LC}$$

Now we plug in values for components.

$$R = R_2 = 100 \Omega \quad L = 125 \text{ mH (for part a)} \quad C = 2 \mu\text{F}$$

$$\alpha = \frac{1}{2 \cdot 100 \Omega \cdot 2 \mu\text{F}} = \frac{1}{400} \text{ M rad/s} = \frac{2.5}{1\text{k}} \text{ M rad/s}$$

$$\alpha = 2.5 \text{ k rad/s}$$

$$\omega_0^2 = \frac{1}{125 \text{ mH} \cdot 2 \mu\text{F}} = \frac{1}{250 \text{ n}} (\text{rad/s})^2 = \frac{4}{1\text{k}} \text{ G} (\text{rad/s})^2$$

$$\omega_0^2 = 4 \text{ M} (\text{rad/s})^2 \quad \text{or} \quad \omega_0 = 2 \text{ k rad/s}$$

$$\therefore s_{1,2} = -2.5 \text{ k} \pm \sqrt{(2.5 \text{ k})^2 - (2 \text{ k})^2} \text{ rad/s}$$

$$" = -2.5 \text{ k} \pm 1.5 \text{ k rad/s}$$

$$s_{1,2} = -4 \text{ k and } -1 \text{ k rad/s}$$

Note: Real part of s is always ≤ 0 for an RLC circuit.

b) For $L = 11.834 \text{ mH}$ we have different ω_0^2 :

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{11.834 \text{ mH} \cdot 2 \mu\text{F}} = \frac{42.25 \text{ m}}{\text{ns}}$$

$$\omega_0^2 = 42.25 \text{ M rad/s}^2 \quad \text{or} \quad \omega_0 = 6.5 \text{ k rad/s}$$

Note: Changing L does not change α for a parallel RLC, but it would change α for a series RLC where $\alpha = R/2L$.

$$\text{Here, } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \text{with } \omega_0 > \alpha.$$

Since $\omega_0 > \alpha$, we get complex roots:

$$s_{1,2} = -2.5 \text{ k} \pm \sqrt{(2.5 \text{ k})^2 - (6.5 \text{ k})^2} \text{ rad/s}$$

$$s_{1,2} = -2.5 \text{ k} \pm j 6.0 \text{ k} \text{ rad/s}$$

We define the damping frequency to be the magnitude of the $\sqrt{\quad}$ term, or

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad (\text{order of } \omega_0^2, \alpha^2 \text{ is reversed})$$

$$\omega_d = \sqrt{(6.5 \text{ k})^2 - (2.5 \text{ k})^2} \text{ rad/s}$$

$$\omega_d = 6 \text{ k} \text{ rad/s}$$

c) The circuit is critically damped when $s_1 = s_2$, i.e. when $\sqrt{\quad} = 0$ or $\alpha = \omega_0$.

Since $\alpha = 2.5 \text{ k} \text{ rad/s}$ doesn't change with L ,

we must have $\omega_0 = 2.5 \text{ k} \text{ rad/s}$.

$$\therefore \frac{1}{\sqrt{LC}} = 2.5 \text{ k} \text{ rad/s} \Rightarrow \frac{1}{LC} = (2.5 \text{ k})^2 (\text{r/s})^2$$

$$\text{or } L = \frac{1 (\text{s/r})^2}{(2.5 \text{ k})^2 \text{ C}} = \frac{1 \text{ H}}{6.25 \text{ k}^2 \cdot 2 \mu} = \frac{1 \text{ H}}{6.25 \cdot 2}$$

$$L = 80 \text{ mH}$$