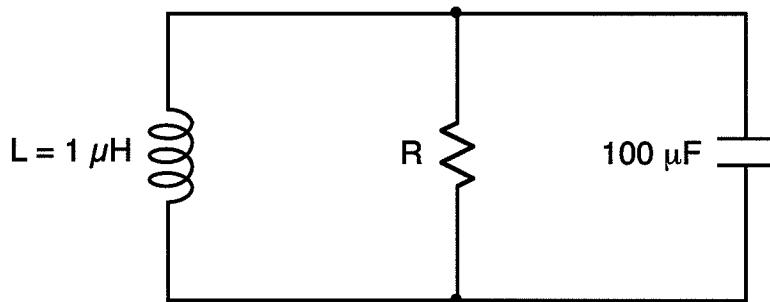


Ex:

- If $R = 40 \text{ m}\Omega$, find the characteristic roots, s_1 and s_2 , for the above circuit.
- If $R = 40 \text{ m}\Omega$, find the value of L that makes the circuit critically damped.
- If $L = 1 \mu\text{H}$, find the damping frequency, ω_d , for the value of R that gives a damping frequency of $\alpha = 10 \text{ krad/s}$.

sol'n: a) For parallel RLC, characteristic roots are

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \alpha = \frac{1}{2RC}, \quad \omega_0^2 = \frac{1}{LC}$$

$$\alpha = \frac{1}{2 \cdot 40 \text{ m}\Omega \cdot 100 \mu\text{F}} = \frac{1}{8 \text{ k}\Omega \mu\text{F}} \text{ r/s} = \frac{1 \text{ M}}{8} \text{ r/s}$$

$$\alpha = 125 \text{ kr/s}$$

$$\omega_0^2 = \frac{1}{1 \mu\text{H} \cdot 100 \mu\text{F}} = \frac{(1 \text{ M})^2}{10^2} (\text{r/s})^2 = (100 \text{ k r/s})^2$$

$$\sqrt{\alpha^2 - \omega_0^2} = \sqrt{(125 \text{ k})^2 - (100 \text{ k})^2} = 75 \text{ k r/s}$$

$$s_{1,2} = -125 \text{ k} \pm 75 \text{ k r/s} = -50 \text{ k r/s} \text{ and } -200 \text{ k r/s}$$

b) Critically damped $\Rightarrow \sqrt{\alpha^2 - \omega_0^2} = 0 \Rightarrow \alpha^2 = \omega_0^2 \quad (125 \text{ k})^2 = \frac{1}{LC}$

$$L = \frac{1}{(125 \text{ k})^2 C} = \left(\frac{8}{1 \text{ M}}\right)^2 \frac{1}{100 \mu\text{F}} \text{ H} = \frac{64 \text{ H}}{100 \text{ M}} = 640 \text{ nF}$$

c) $L = 1 \mu\text{H}$, $\alpha = 10 \text{ k r/s}$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad \omega_0^2 = \frac{1}{LC} = \frac{1}{1\mu\text{H} \cdot 100\mu\text{F}}$$

$$\omega_0^2 = \left(\frac{1\text{M}}{10}\right)^2 = (100\text{k})^2 \text{ r}^2/\text{s}^2$$

$$\omega_d = \sqrt{(100\text{k})^2 - (10\text{k})^2} \text{ r/s}$$

$$= 10\text{k} \sqrt{10^2 - 1^2} \text{ r/s}$$

$$= 10\text{k} \sqrt{99} \text{ r/s}$$

$$\omega_d \approx 10\text{k} \cdot 9.5 \text{ r/s}$$

$$\omega_d \approx 99.5 \text{ k r/s}$$