
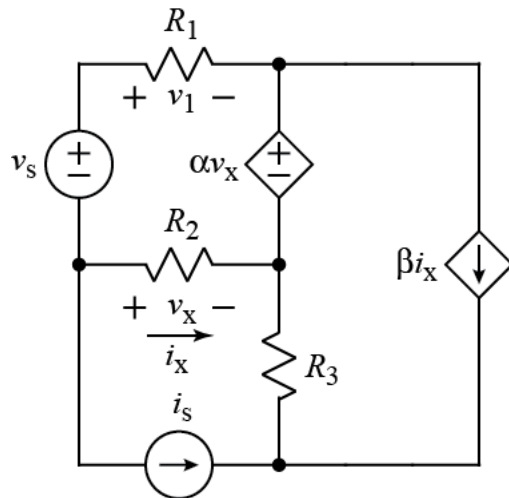


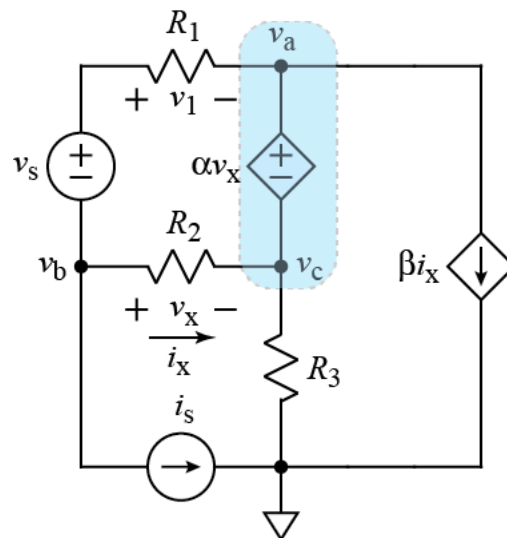**Ex:** Using superposition, find an expression for  $v_1$  in the circuit shown below.



**SOL'N I:** We first illustrate brute force attempts at solution using the node-voltage method and superposition. When the suffering is complete, we consider judicious use of the reference placement, superposition, and Kirchhoff's laws to simplify matters.

For the node-voltage method, we label a reference and any nodes where three or more components are joined.



Before going any further, we define variables for dependent sources in terms of node voltages.

$$v_x = v_b - v_c$$

$$i_x = \frac{v_x}{R_2} = \frac{v_b - v_c}{R_2}$$

We use the above definitions whenever we write  $v_x$  or  $i_x$ .

The blue indicates a supernode. We proceed to sum currents out of nodes, starting with the supernode, (two nodes connected by just a voltage source), for which we sum currents out of the blue bubble. The key is to define currents in terms of node voltages.

$$\frac{v_a - (v_b + v_s)}{R_1} + \beta \frac{v_b - v_c}{R_2} + \frac{v_c - v_b}{R_2} + \frac{v_c}{R_3} = 0 \text{ A}$$

or

$$\frac{v_a - (v_b + v_s)}{R_1} + (\beta - 1) \frac{v_b - v_c}{R_2} + \frac{v_c}{R_3} = 0 \text{ A}$$

or, if we write things in a form suitable for matrix solution,

$$\frac{1}{R_1} v_a + \left( -\frac{1}{R_1} + \frac{\beta - 1}{R_2} \right) v_b + \left( \frac{1 - \beta}{R_2} + \frac{1}{R_3} \right) v_c = \frac{v_s}{R_1} \quad (1)$$

The voltage equation is simpler:

$$v_a - v_c = \alpha (v_b - v_c).$$

or, in matrix compatible form,

$$(1)v_a + (-\alpha)v_b + (\alpha - 1)v_c = 0 \text{ V}. \quad (2)$$

Finally, we have the  $v_b$  node:

$$\frac{v_b + v_s - v_a}{R_1} + \frac{v_b - v_c}{R_2} + i_s = 0 \text{ A}$$

or, in matrix compatible form,

$$\left( -\frac{1}{R_1} \right) v_a + \left( \frac{1}{R_1} + \frac{1}{R_2} \right) v_b + \left( -\frac{1}{R_2} \right) v_c = -\frac{v_s}{R_1} - i_s. \quad (3)$$

Now what? We solve the equations by hand, introducing terms to save writing:

$$X \equiv \frac{R_1(1-\beta)}{R_2} \quad \text{and} \quad Y \equiv \frac{R_1}{R_2}$$

Multiplying (1) by  $R_1$  and (3) by  $-R_1$  gives us the following three equations:

$$(1)v_a + (-1-X)v_b + (X + R_1/R_3)v_c = v_s \quad (1')$$

$$(1)v_a + (-\alpha)v_b + (\alpha-1)v_c = 0 \text{ V} \quad (2')$$

$$(1)v_a + (-1-Y)v_b + (Y)v_c = v_s + i_s R_1 \quad (3')$$

Solving (2') for  $v_a$ , we may substitute the result into (1') and (3').

$$(1)v_a = (\alpha)v_b + (1-\alpha)v_c \quad (2'')$$

which gives

$$\alpha v_b + (1-\alpha)v_c + (-1-X)v_b + (X + R_1/R_3)v_c = v_s \quad (1'')$$

and

$$\alpha v_b + (1-\alpha)v_c + (-1-Y)v_b + (Y)v_c = v_s + i_s R_1 \quad (3'')$$

Cleaning things up, we have

$$(\alpha-1-X)v_b + (1-\alpha+X+R_1/R_3)v_c = v_s \quad (1''')$$

and

$$(\alpha-1-Y)v_b + (1-\alpha+Y)v_c = v_s + i_s R_1 \quad (3''')$$

We can do a bit more with (1''') and (3'''):

$$(\alpha-1-X)v_b + (-\alpha+1+X+R_1/R_3)v_c = v_s$$

or

$$v_b + \left( -1 + \frac{R_1/R_3}{\alpha-1-X} \right) v_c = \frac{v_s}{\alpha-1-X} \quad (1'''')$$

and

$$(\alpha - 1 - Y)v_b + (-\alpha + 1 + Y)v_c = v_s + i_s R_1$$

or

$$v_b + (-1)v_c = \frac{v_s + i_s R_1}{\alpha - 1 - Y} \quad (3''''')$$

Solving (3''''') for  $v_c$ , we may substitute into (1'''''), leaving only  $v_b$ . Keeping  $v_b$  instead of  $v_c$  is convenient since we want to find  $v_1$ .

$$v_c = v_b - \frac{v_s + i_s R_1}{\alpha - 1 - Y}$$

Substituting into (1'''''), we have

$$v_b + \left(-1 + \frac{R_1 / R_3}{\alpha - 1 - X}\right) \left(v_b - \frac{v_s + i_s R_1}{\alpha - 1 - Y}\right) = \frac{v_s}{\alpha - 1 - X}$$

or

$$\left(\frac{R_1 / R_3}{\alpha - 1 - X}\right) v_b = \frac{v_s}{\alpha - 1 - X} + \left(-1 + \frac{R_1 / R_3}{\alpha - 1 - X}\right) \left(\frac{v_s + i_s R_1}{\alpha - 1 - Y}\right)$$

Ugh! We struggle on... Multiply both sides by  $\alpha - 1 - X$ .

$$(R_1 / R_3)v_b = v_s + (-\alpha + 1 + X) + R_1 / R_3 \left(\frac{v_s + i_s R_1}{\alpha - 1 - Y}\right)$$

or

$$(R_1 / R_3)v_b = \left(\frac{\alpha - 1 - Y - (\alpha - 1 - X) + R_1 / R_3}{\alpha - 1 - Y}\right) v_s + (-\alpha + 1 + X) + R_1 / R_3 \left(\frac{i_s R_1}{\alpha - 1 - Y}\right)$$

or

$$(R_1 / R_3)v_b = \left(\frac{X - Y + R_1 / R_3}{\alpha - 1 - Y}\right) v_s + (X + 1 - \alpha + R_1 / R_3) \left(\frac{i_s R_1}{\alpha - 1 - Y}\right)$$

Since  $X - Y = \beta R_1 / R_2$ , if we multiply by  $R_3 / R_1$ , we have

$$v_b = \left( \frac{\beta R_3 / R_2 + 1}{\alpha - 1 - Y} \right) v_s + ((X + 1 - \alpha) R_3 + R_1) \left( \frac{i_s}{\alpha - 1 - Y} \right). \quad (1''''')$$

Very well, but we want  $v_1$ . Curiously, things are much better when we try to find  $v_1$ .

$$v_1 = v_b + v_s - v_a$$

where

$$(1)v_a = (\alpha)v_b + (1 - \alpha)v_c \quad (2'')$$

so

$$v_1 = v_b + v_s - \alpha v_b - (1 - \alpha)v_c = v_s + (1 - \alpha)(v_b - v_c)$$

where

$$v_b + (-1)v_c = \frac{v_s + i_s R_1}{\alpha - 1 - Y} \quad (3''''')$$

so

$$v_1 = v_s + (1 - \alpha) \frac{v_s + i_s R_1}{\alpha - 1 - Y} = v_s + (1 - \alpha) \frac{v_s + i_s R_1}{\alpha - 1 - R_1 / R_2}$$

or

$$v_1 = \frac{\alpha - 1 - R_1 / R_2}{\alpha - 1 - R_1 / R_2} v_s + (1 - \alpha) \frac{v_s + i_s R_1}{\alpha - 1 - R_1 / R_2}$$

or

$$v_1 = \frac{\alpha - 1 - R_1 / R_2 + 1 - \alpha}{\alpha - 1 - R_1 / R_2} v_s + (1 - \alpha) \frac{i_s R_1}{\alpha - 1 - R_1 / R_2}$$

or

$$v_1 = \frac{-R_1 / R_2}{\alpha - 1 - R_1 / R_2} v_s + (1 - \alpha) \frac{i_s R_1}{\alpha - 1 - R_1 / R_2}$$

or

$$v_1 = \frac{-R_1}{R_2(\alpha - 1) - R_1} v_s + (1 - \alpha) \frac{i_s R_1 R_2}{R_2(\alpha - 1) - R_1}$$

or


$$v_1 = \frac{v_s R_1 - i_s R_1 R_2 (1 - \alpha)}{R_2 (1 - \alpha) + R_1}$$

Wait. What happened to the mess we had before in (1''''')? The above solution didn't even use  $\beta$ ! Maybe there is a simpler way to have this problem.

SOL'N II: We use superposition and some basic ideas, like Kirchhoff's laws.


We turn on one independent source at a time. Dependent sources stay on.

case I:  $v_s$  on,  $i_s$  off = open

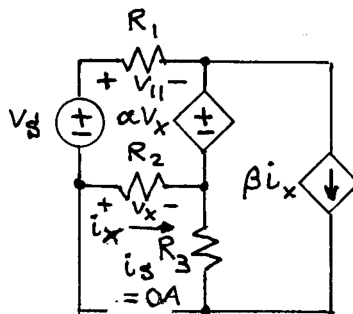

If we examine where  $i_x$  goes, we discover that  $i_x$  flows thru  $R_1$ . Thus, a  $v$ -loop around the upper left yields a value for  $i_x$ .

Note that  $v_{x1} = i_{x1} R_2$ .

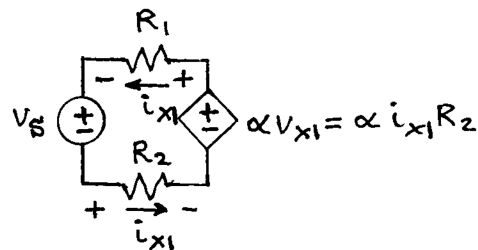

$$v\text{-loop: } V_S + i_{x1} R_1 - i_{x1} \alpha R_2 + i_{x1} R_2 = 0V$$


$$\text{or } i_{x1} (R_1 + R_2 - \alpha R_2) = -V_S$$

$$\text{or } i_{x1} = \frac{-V_S}{R_1 + R_2 - \alpha R_2}$$


Using Ohm's law to find  $V_{11}$  we have

$$V_{11} = -i_{x1} R_1 = V_S \frac{R_1}{R_1 + R_2 - \alpha R_2}$$

case II:  $V_S$  off = wire,  $i_S$  on

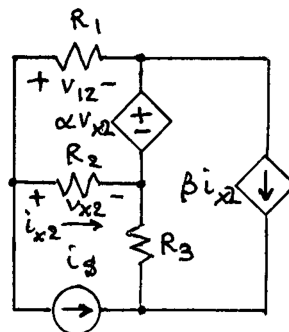

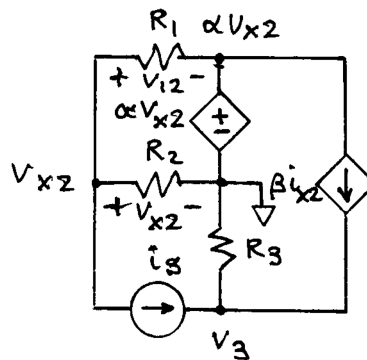We can always use node-voltage.  
Putting a reference in the center  
is convenient.



Consider the  $v_{x2}$  node:

$$\frac{v_{x2} - \alpha v_{x2}}{R_1} + \frac{v_{x2}}{R_2} + i_s = 0A$$

$$\text{or } v_{x2} \left( \frac{1}{R_1} - \frac{\alpha}{R_1} + \frac{1}{R_2} \right) = -i_s$$

$$\text{or } v_{x2} (R_2 - \alpha R_2 + R_1) = -i_s R_1 R_2$$

$$\text{or } v_{x2} = \frac{-i_s R_1 R_2}{R_1 + R_2 (1 - \alpha)}$$

$$v_{12} = v_{x2} - \alpha v_{x2} = (1 - \alpha) v_{x2}$$

$$\text{or } v_{12} = \frac{-i_s R_1 R_2 (1 - \alpha)}{R_1 + R_2 (1 - \alpha)}$$

Now we sum the results from the two cases.


$$v_1 = v_{11} + v_{12} = \frac{v_s R_1 - i_s R_1 R_2 (1 - \alpha)}{R_1 + R_2 (1 - \alpha)}$$

Consistency checks follow.



We perform some consistency checks. We set some component values to zero to create a circuit with an obvious solution. Then we see if our above expression for  $v_1$  gives the correct answer.

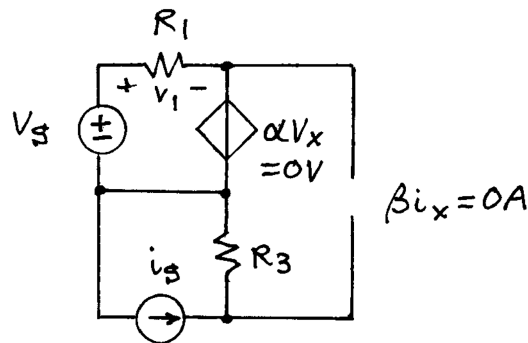Check 1: Set  $R_2 = 0$  so  $v_x = 0V$ .  
Set  $\beta = 0$  so  $\beta i_x = 0A$ .



From the  $v$ -loop in the upper left we have  $v_1 = v_s$ .

Our answer above gives

$$v_1 = \frac{v_s R_1 - i_s R_1 (0)(1-\alpha)}{R_1 + 0(1-\alpha)} = v_s \checkmark$$


Check 2: Set  $R_1 = 0$ , then  $v_1 = 0V$ .

Our answer for  $v_1$  gives

$$v_1 = \frac{v_s(0) - i_s(0) R_2(1-\alpha)}{0 + R_2(1-\alpha)} = 0V \checkmark$$

One more check follows.

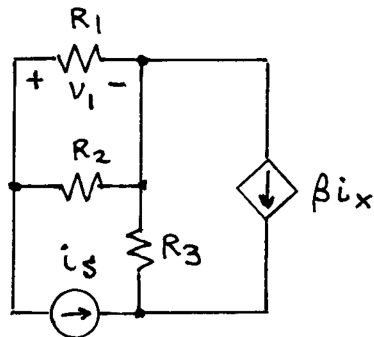Check 3: Set  $v_g = 0V$  and  $\alpha = 0$ .



Careful inspection reveals that  $R_1$  and  $R_2$  are in parallel and  $i_s$  flows thru  $R_1$  and  $R_2$ .

So we have a current divider, and voltage  $v_1$  is given by

$$v_1 = -i_s \frac{R_2}{R_1 + R_2} \cdot R_1$$

Our answer above gives

$$v_1 = \frac{0 \cdot R_1 - i_s R_1 R_2 (1-0)}{R_1 + R_2 (1-0)}$$

$$\text{or } v_1 = -\frac{i_s R_1 R_2}{R_1 + R_2} \quad \checkmark$$

All checks thus far are satisfied.