

Given load:  $150\ \Omega$  and  $20\ \mu\text{F}$  in series

Linear transformer:  $R_1 = 12\ \Omega$   $L_1 = 80\ \mu\text{H}$

$R_2 = 50\ \Omega$   $L_2 = 500\ \mu\text{H}$

$M = 100\ \mu\text{H}$

sinusoidal  $V$ -source:  $\omega = 500\ \text{krad/s}$

$Z_{\text{internal}} @ \omega = 500\ \text{krad/s} = 5 + j16\ \Omega$


$V_{\text{no load}} = 125\ \text{V}$

Find a) value of impedance reflected into primary  
b) value " " seen from terminals of  $V$  source

ans: a)  $8 - j6\ \Omega$   
b)  $20 + j34\ \Omega$

sol'n: a) We use the linear transformer model, and we observe that  $V_{\text{no load}} = \text{Voltage of source in model.}$

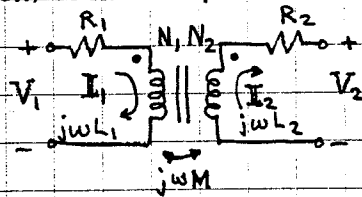Note: We use standard position of dots and directions of currents for our transformer:




The equations for the above transformer are

$$V_1 = (R_1 + j\omega L_1)I_1 - j\omega M I_2$$

$$V_2 = j\omega M I_1 - (R_2 + j\omega L_2)I_2$$

We'll use these eqns for our model.

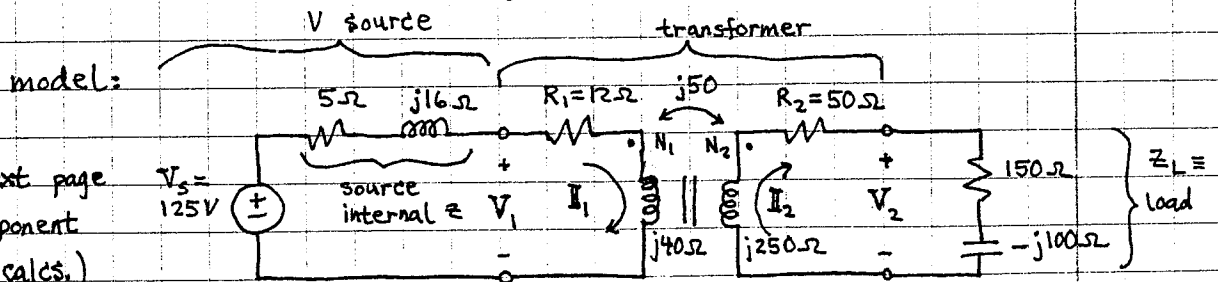


$$\frac{1}{j\omega C} = -j \frac{1}{500k \cdot 20n} = -j100$$

$$j\omega L_1 = j 500k \cdot 80\mu = j 40k k\mu = j40$$

$$j\omega L_2 = j 500k \cdot 500\mu = j 250k k\mu = j250$$

$$j\omega M = j 500k \cdot 100\mu = j 50k k\mu = j50$$

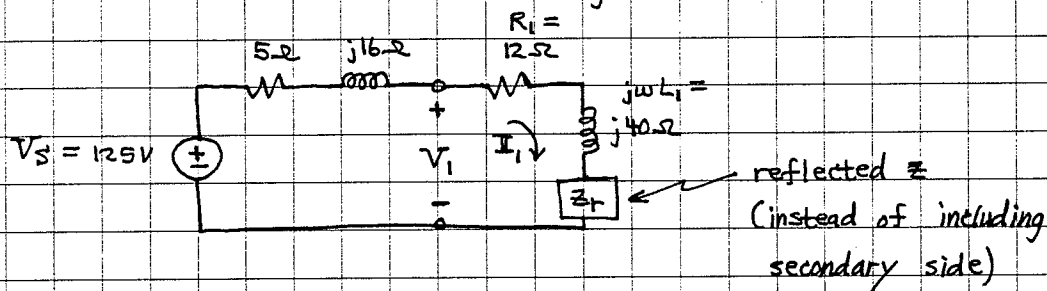Reflected impedance  $z_r$  is the impedance we would place in series with the primary side of the transformer to get the same  $V_1$  versus  $I_1$  characteristics as the original circuit:



The Text calculates 
$$z_r = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + z_L}$$

We'll derive this result, too:

For the secondary we have sum of  $V$  drops around loop:

$$V_2 = z_L I_2 = \underbrace{j\omega M I_1 - (R_2 + j\omega L_2) I_2}_{\text{from transformer eq's}}$$

$$\text{or } (R_2 + j\omega L_2 + z_L) I_2 = j\omega M I_1$$

$$\text{or } I_2 = \frac{j\omega M}{R_2 + j\omega L_2 + z_L} I_1$$

From the first transformer eq'n, with this result substituted for  $I_2$ , we have:

$$V_1 = (R_1 + j\omega L_1) I_1 - j\omega M \frac{j\omega M}{R_2 + j\omega L_2 + z_L} I_1$$

$$\text{or } V_1 = (R_1 + j\omega L_1) I_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} I_1$$

For the reflected impedance model we have

$$V_1 = (R_1 + j\omega L_1) I_1 + Z_r I_1$$

Equating expressions for  $V_1$  gives:

$$Z_r = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} \quad \checkmark$$

Now we plug in values to obtain the answer to (a):

$$Z_r = \frac{(500\text{K})^2 (100\mu)^2}{50 + j250 + 150 - j100} = \frac{250\text{K}^2 \cdot 10\text{K}\mu^2}{200 + j150}$$

$$= \frac{2.5\text{K}}{50(4+j3)} = \frac{50}{4+j3} = \frac{50(4-j3)}{4^2+3^2}$$

$$= \frac{50}{25} (4-j3) = 2(4-j3)$$

$$Z_r = 8 - j6 \Omega$$

- b) The impedance seen from the terminals of the  $V$  source is the impedance seen to the right of the terminals where we measure  $V_1$ .

In other words, we are finding the impedance seen looking into the transformer.

From the reflected impedance model we see that this is

$$Z = R_1 + j\omega L_1 + Z_r = 12 + j40 + 8 - j6 = 20 + j34 \Omega$$