

POWER TRANSISTORS

- Heat is a major concern
- T_J = Collector-base junction temperature
 - Most power is dissipated here
 - V_{CB} usually larger than V_{BE}
- Every transistor has a T_{JMAX}
- Consider transistor operating in open air at an ambient temperature T_A :

$$T_J - T_A = \theta_{JA} P_D$$


$\theta_{JA} \Rightarrow$ thermal resistance between junction and air $\{\text{°C/W}\}$

$P_D \Rightarrow$ power dissipation of transistor

Temperature difference \Leftrightarrow voltage difference

Thermal resistance \Leftrightarrow electrical resistance

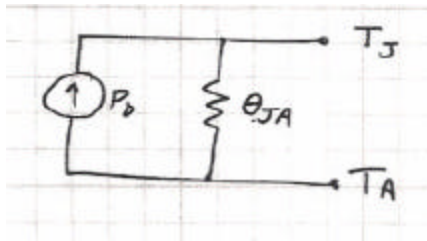
Power dissipation \Leftrightarrow current



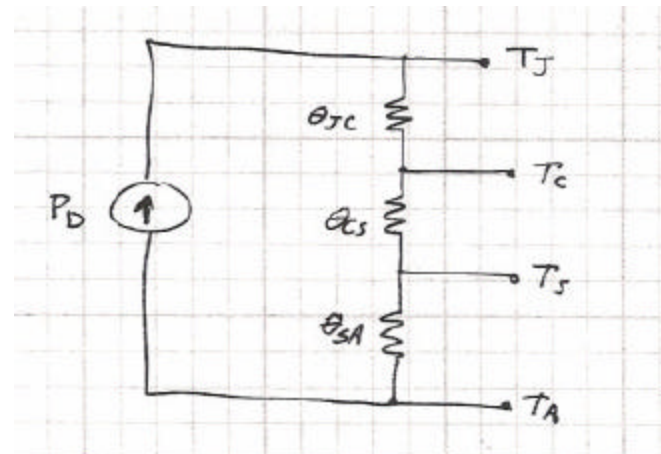Example: From a data sheet, a particular transistor can safely dissipate a maximum of 40W at an ambient temperature of 25°C. $T_{JMAX} = 150^\circ\text{C}$, how much power can we dissipate in a case where $T_A = 50^\circ\text{C}$?

Heat Sinks:

$$\theta_{JA} = \theta_{JC} + \theta_{CS} + \theta_{SA}$$




POWER TRANSISTORS

Example: A particular transistor can dissipate a maximum of 40W at a case temperature (T_C) = 25°C. $T_{JMAX} = 150^\circ\text{C}$. What is P_{DMAX} at $T_A = 50^\circ\text{C}$, given the following heat sink?

$$\theta_{CS} = 1^\circ\text{C/W}$$

$$\theta_{SA} = 4^\circ\text{C/W}$$

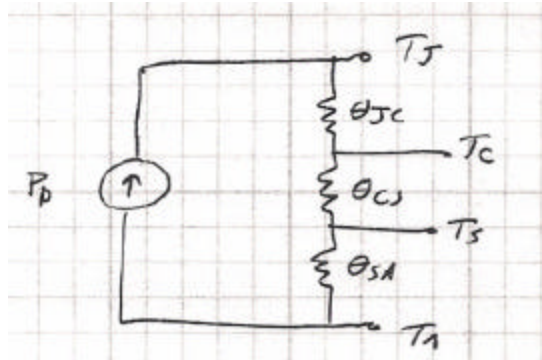

$$P_D = \frac{T_J - T_A}{\theta_{JC} + \theta_{CS} + \theta_{SA}}$$
$$T_S = T_A + P_D \theta_{SA} =$$
$$T_C = T_S + P_D \theta_{CS} =$$



IC issues:

- Area = \$\$
 - BJTs are small
 - MOSFETs are VERY small
 - Resistors are LARGE (typically < 10kohm)
 - Caps are LARGE (typically < 20pF)
- Driving on-chip loads: usually MOSFET gates => small capacitive loads



POWER TRANSISTORS

Common CMOS Op-Amp:

Two-stage topology:

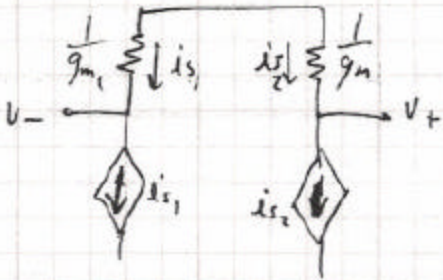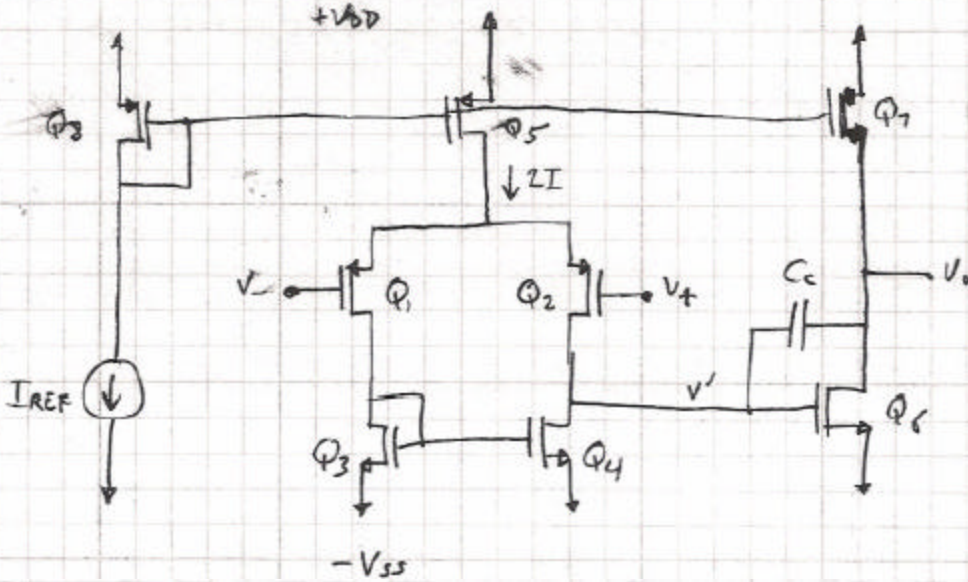
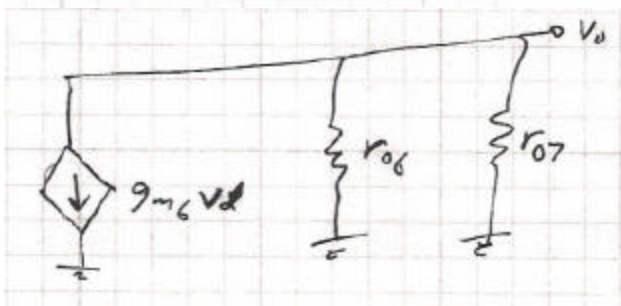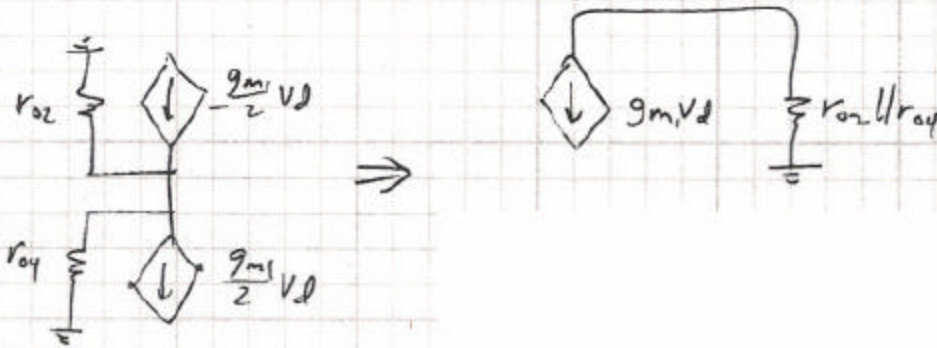
$$i_{d1} = \frac{V_+ - V_p}{\frac{1}{g_m} + \frac{1}{g_m}} = \frac{g_m}{2} v_d$$



POWER TRANSISTORS

What is A? Let $I_{Q5} = I_{Q7} = 25\mu\text{A}$, $|V_A| = 25\text{V}$, $k_n' = 20\mu\text{A/V}^2$, $k_p' = 10\mu\text{A/V}^2$, $|V_t| = 1\text{V}$, $W/L = 10$ for all devices.

What is the purpose of C_C ? _____