

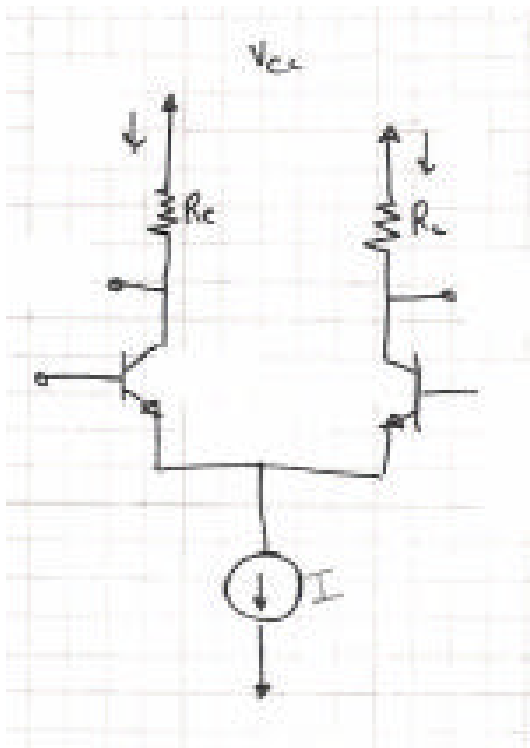
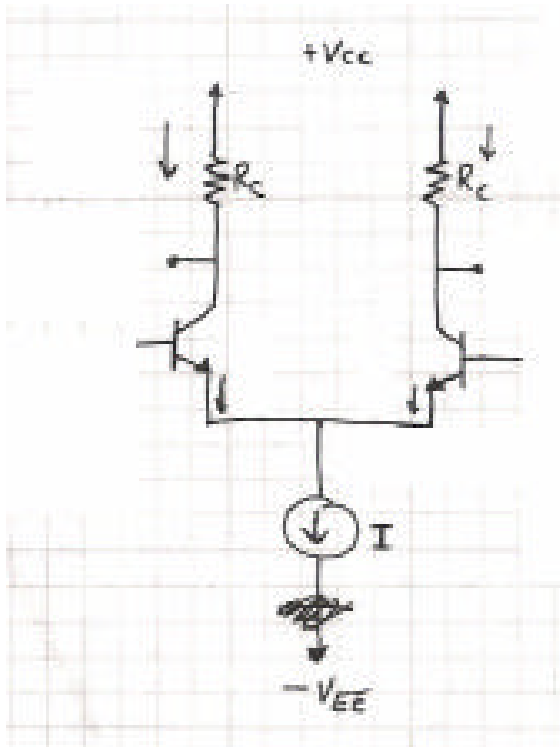


BJT DIFFERENTIAL

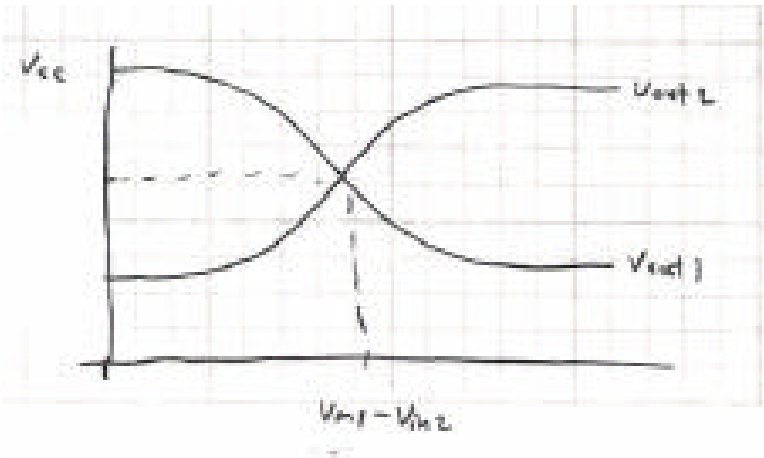


BJT DIFFERENTIAL

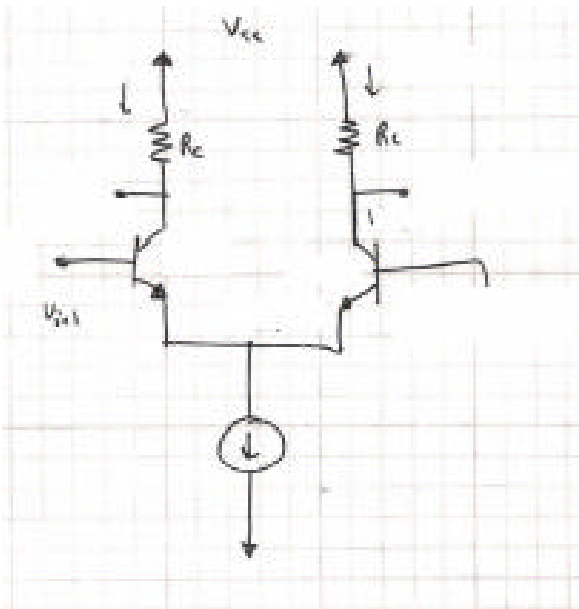


BJT DIFFERENTIAL

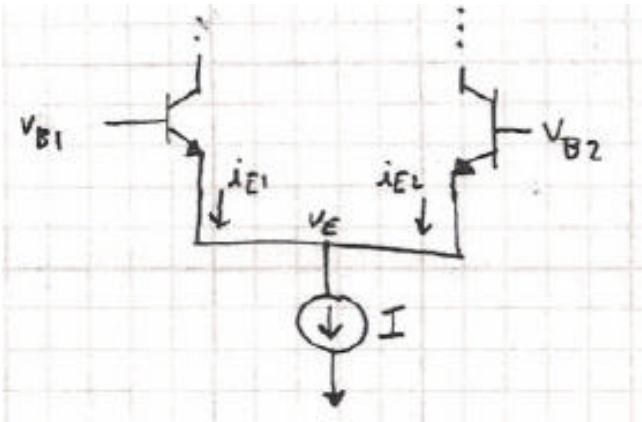Large Signal Operation of BJT Differential Pair




- This is a _____ controlled by the _____
in voltage between V_{B1} and V_{B2}

BJT DIFFERENTIAL

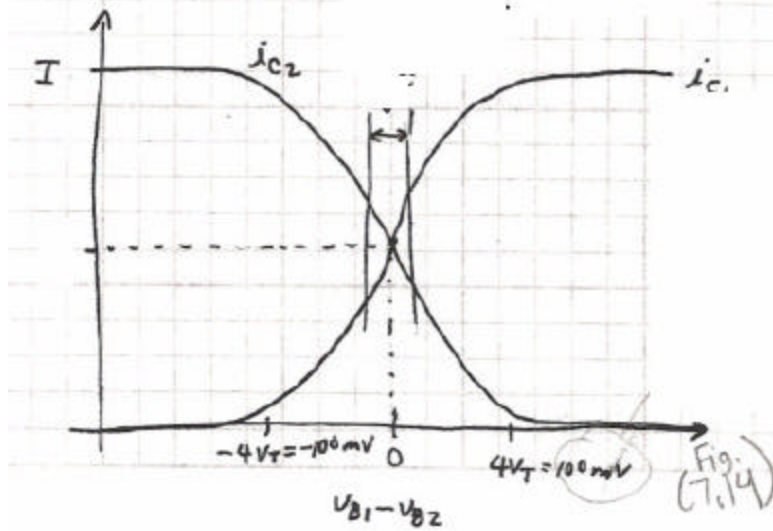

Small-signal model:

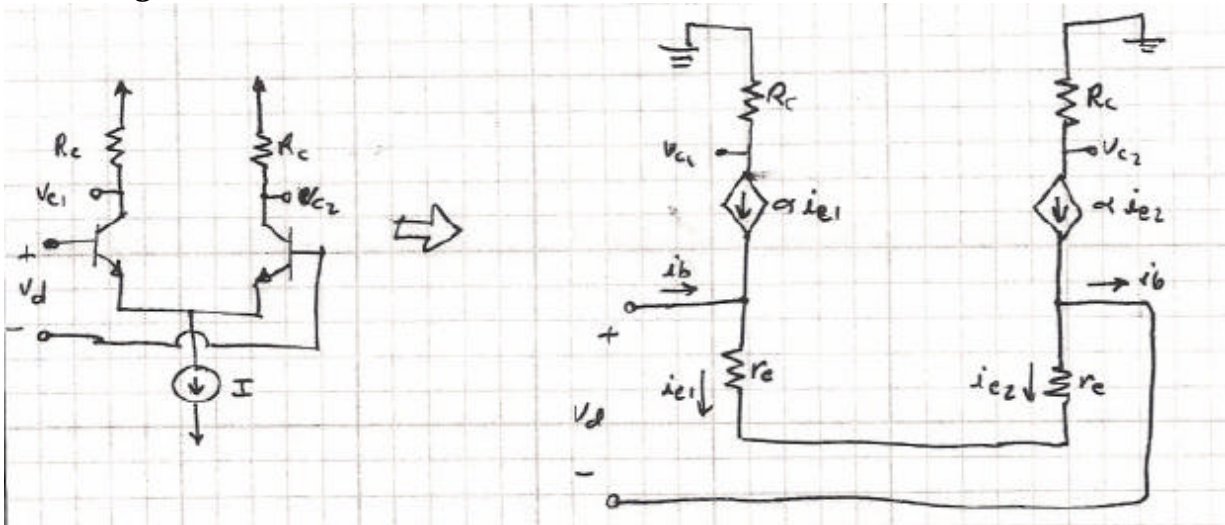


- Note that output can be taken differentially ($V_{C1} - V_{C2}$) or single-ended (V_{C1} or V_{C2} alone, referenced to ground)

BJT DIFFERENTIAL

What is the differential input resistance?


Problem: No perfect current sources!

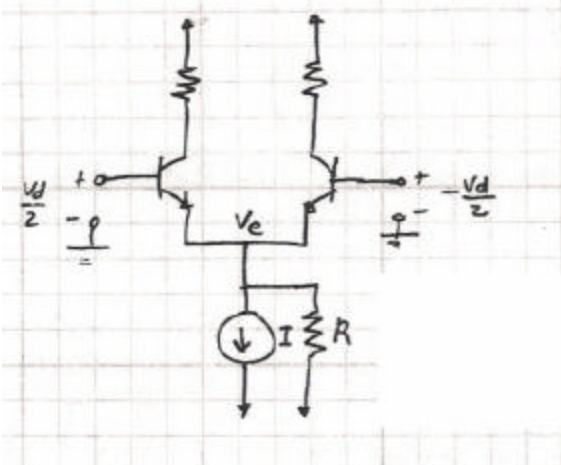

- Tough to analyze
 - **TRICK:** Split circuit into _____
 - Rewrite inputs as _____

- This shows that R has _____


New circuit:

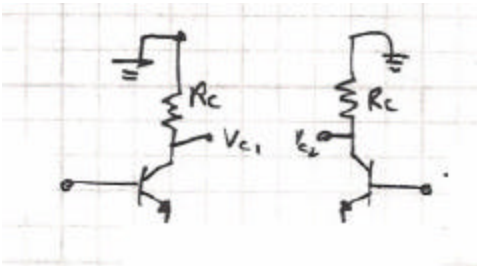


Analyze as separate circuits.

BJT DIFFERENTIAL

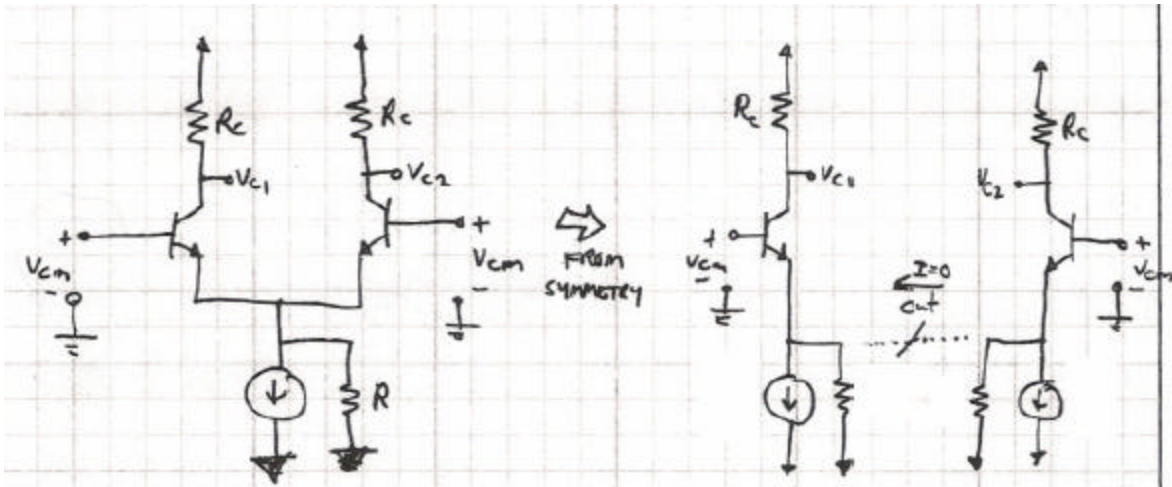What is so bad about a non-ideal current source then? _____




Small-signal:

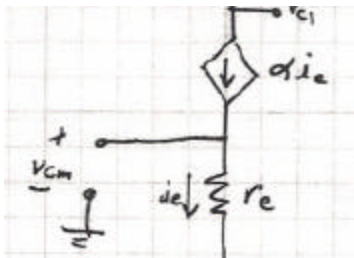


BJT DIFFERENTIAL

Nonideal characteristics of Diff. Amps:

- Input offset voltage:

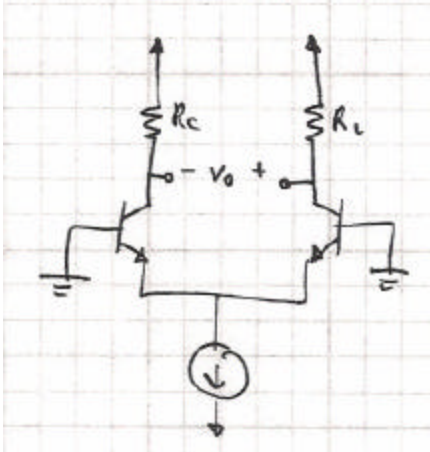

- This can be modeled as:

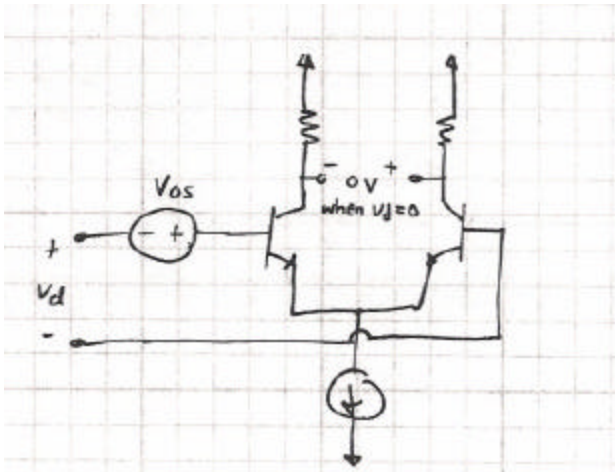

- Input bias currents can be mismatched due to _____