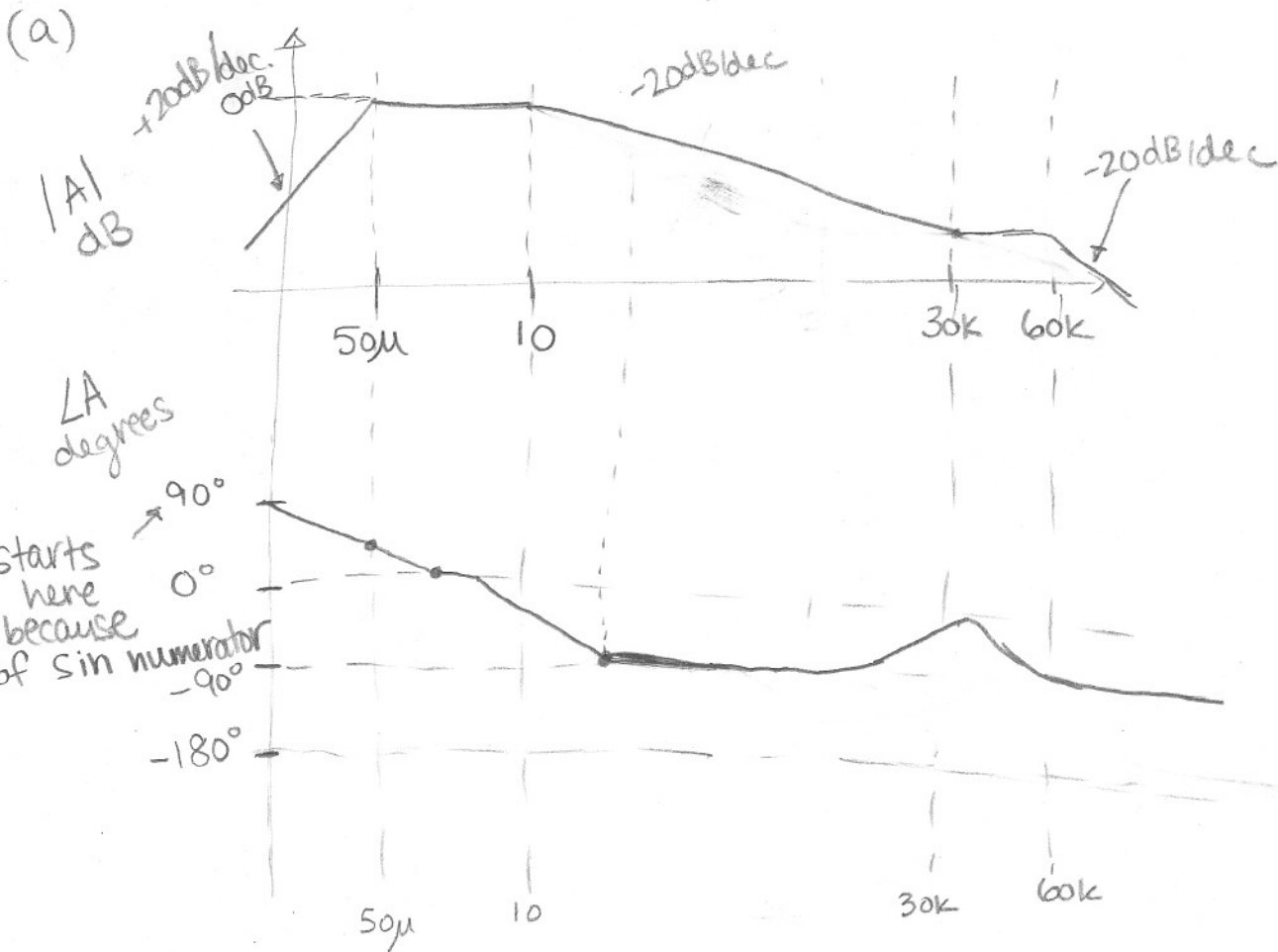


HW #11 Sol'n

1.
$$A(s) = \frac{10s \left(\frac{s}{30k} + 1\right)}{(s+10) \left(\frac{1}{20k} + s\right) \left(\frac{s}{60k} + 1\right)}$$

↑
lowest frequency

$$= \frac{10 \cdot s \cdot \left(\frac{s}{30k} + 1\right)}{\left(\frac{s}{10} + 1\right) \left(\frac{1}{20ks} + 1\right) \left(\frac{s}{60k} + 1\right)} = \frac{\left(\frac{s}{30k} + 1\right)}{\left(\frac{s}{10} + 1\right) \left(\frac{1}{20ks} + 1\right) \left(\frac{s}{60k} + 1\right)}$$



(b) $\omega_L = 50\mu$, $\omega_H = 10$ rad/sec.

(c) 0dB

(d) poles $\Rightarrow 50\mu, 10, 60k$

(e) zeros $\Rightarrow 1$ at zero, $30k$

1. (cont.)

(f) Need to find freq. when phase = $-90^\circ \Rightarrow \approx 1$ decade after 10
 \therefore start at 100



$$\left(\tan^{-1}\left(\frac{100}{30k}\right) - \tan^{-1}\left(\frac{100}{10}\right) - \tan^{-1}\left(\frac{100}{60k}\right) \right) \approx -84^\circ$$

@ 600 rad/sec $\approx -89^\circ \therefore |A\beta| = 1 = \frac{\beta}{\sqrt{\left(\frac{600}{30k}\right)^2 + 1} \sqrt{\left(\frac{600}{10}\right)^2 + 1} \sqrt{\left(\frac{600}{60k}\right)^2 + 1}}$

$\beta \approx 60$

(g) $A_f = \frac{A}{1+A\beta} = \frac{1 \left[\text{need } V/V \right]}{1+(1)(2)} = 0.33 \text{ V/V} = -9.5 \text{ dB}$

5.

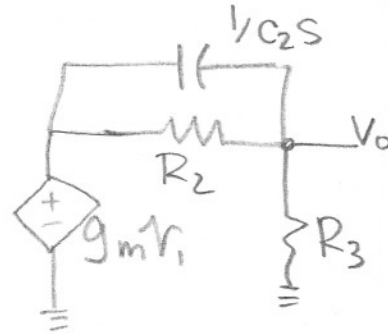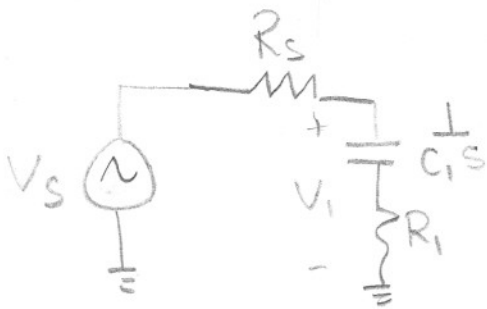

$$V_o = \frac{g_m V_1 \cdot R_3}{R_3 + (R_2 \parallel \frac{1}{C_2s})}$$

$$R_2 \parallel \frac{1}{C_2s} = \frac{R_2 \cdot \frac{1}{C_2s}}{R_2 + \frac{1}{C_2s}} = \frac{R_2}{R_2 C_2s + 1}$$

$$= \frac{g_m R_3 V_1}{R_3 + \frac{R_2}{(R_2 C_2s + 1)}} = \frac{g_m R_3 (R_2 C_2s + 1) V_1}{R_3 (R_2 C_2s + 1) + R_2} = \frac{g_m R_3 (R_2 C_2s + 1)}{(R_3 + R_2) \left[\frac{R_3 R_2 C_2s}{(R_3 + R_2)} + 1 \right]}$$

$$V_1 = \frac{\left(\frac{1}{C_1s} + R_1 \right) V_s}{\frac{1}{C_1s} + R_1 + R_s} = \frac{(1 + R_1 C_1s) V_s}{1 + (R_1 + R_s) C_1s}$$


$$\frac{V_o}{V_s} = \frac{g_m R_3 (R_2 C_2s + 1) (1 + R_1 C_1s)}{(R_3 + R_2) \left[\frac{R_3 R_2 C_2s}{(R_3 + R_2)} + 1 \right] [1 + (R_1 + R_s) C_1s]}$$

∴ Midband gain, $A_m \Rightarrow$

$$A_m = \frac{g_m R_3}{R_3 + R_2}$$

Low-freq. poles: None
 Low-freq. zeros: None
 high-freq. poles: $\frac{(R_2 + R_3)}{R_2 R_3 C_2}$, $\frac{1}{(R_1 + R_s) C_1}$
 high-freq. zeros: $\frac{1}{R_2 C_2}$, $\frac{1}{R_1 C_1}$

6.

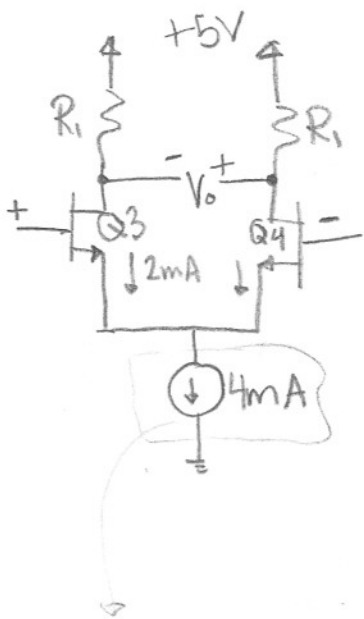

$$A_d = 100 \text{ V/V} = g_m \cdot R_D$$


$$g_m = \sqrt{2(k' \frac{W}{L}) I_D} = \sqrt{2(4\text{m})(2\text{m})}$$

$$g_m = 4\text{m A/V}$$

$$\therefore R_D = \frac{100}{4\text{m}} = \boxed{25\text{K}}$$

$$g_m = 4\text{m} = \frac{2I_D}{V_{ov}}$$
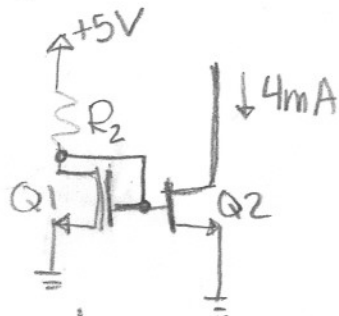
$$\therefore V_{GS} = \frac{2(2\text{m})}{4\text{m}} + 1 = \boxed{2\text{V}}$$



• Need $2\text{V} = V_{GS}$

$$\therefore V_{Q1D} = 2\text{V}$$

$$R_2 = \frac{5 - 2}{4\text{m}} = \boxed{750\Omega}$$

OR $4\text{m} = \frac{1}{2}(4\text{m})(V_{GS} - V_t)^2$

$$\Rightarrow V_{GS} = 2\text{V}$$

$$\therefore R_2 = \frac{5 - 2}{4\text{m}} \text{ (same)}$$

• minimum gate $v \Rightarrow$
 • saturation condition (min.)

$$\text{for } Q_2 \Rightarrow V_{DS} = V_{GS} - V_t = 2 - 1 = 1\text{V}$$


$$\therefore V_{S_{Q4, Q3}} = 1\text{V}$$

$$V_{G_{Q4, Q3}} = \boxed{3\text{V}}$$

3

② differential (not single-ended) gain for mosfet = $50 \text{ V/V} = g_m \cdot (10\text{k})$

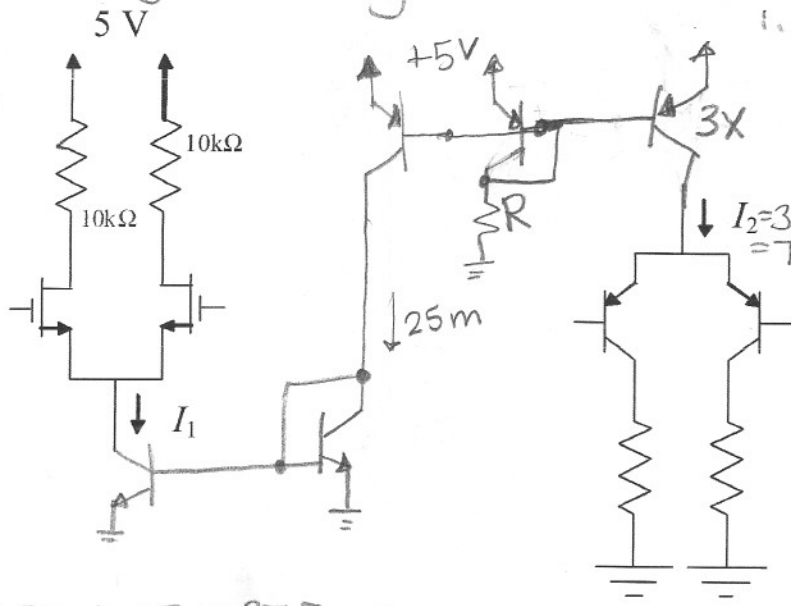$I_1 = 2 I_D = 25\text{m}$
 $I_2 = 2 I_C = 75\text{m}$
 $\therefore I_2 = 3 \cdot I_1$




$g_m = 5\text{m}$
 $g_m = \sqrt{2K'(\frac{W}{L})I_D}$
 $\Rightarrow \frac{(5\text{m})^2}{2(1\text{m})} = I_D$
 $I_D = 12.5\text{mA}$

$R = \frac{(5-7)}{25\text{m}} = 172\Omega$

$\text{BJT: } g_m = \frac{I_C}{V_T} = 1.5\text{A} \Rightarrow I_C = 37.5\text{mA}$

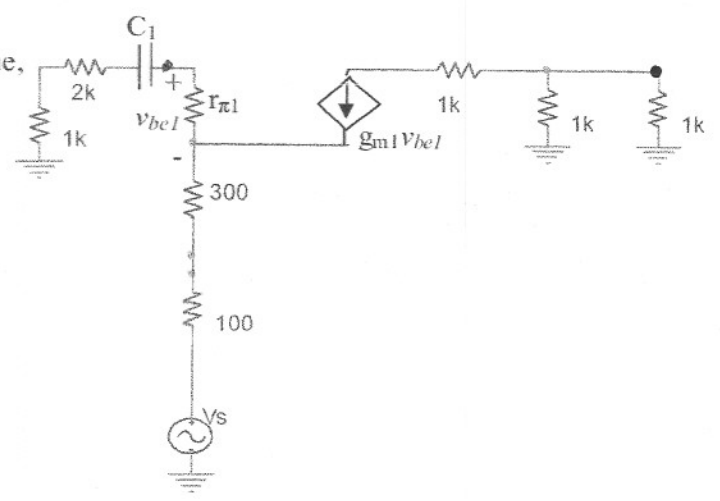3. (a) Using the short-circuit time constant technique, what is the resistance seen by C_1 ?

$R = r_{\pi 1} + 400(\beta + 1) + 3\text{k}$



(b) Describe in your own words the Miller Effect.

(c) As a general rule of thumb (discussed in lecture), if your low frequency poles are 4 and 9 rad/sec and your low frequency zeros are 16 rad/sec, find ω_L . $\omega_L = \sqrt{4^2 + 9^2 - 2(16)^2} \approx$ Does not exist \therefore Not an amplifier


4. Assume the transistors below have a finite β and an infinite Early voltage.

Write an expression for the input resistance R_{in} in the circuit shown below. Your expression should include only real resistances (R_1, R_2, R_3, R_4 , or a subset of these) and possibly β, r_{e1} or $r_{\pi 1}$, and r_{e2} or $r_{\pi 2}$. (Assume both transistors have the same β .) Circle your answer.

- ② Short and open γ
- Miller Effect
- Resistance Reflection Rule
- Circuit Analysis for gain
- Current Mirror design


2

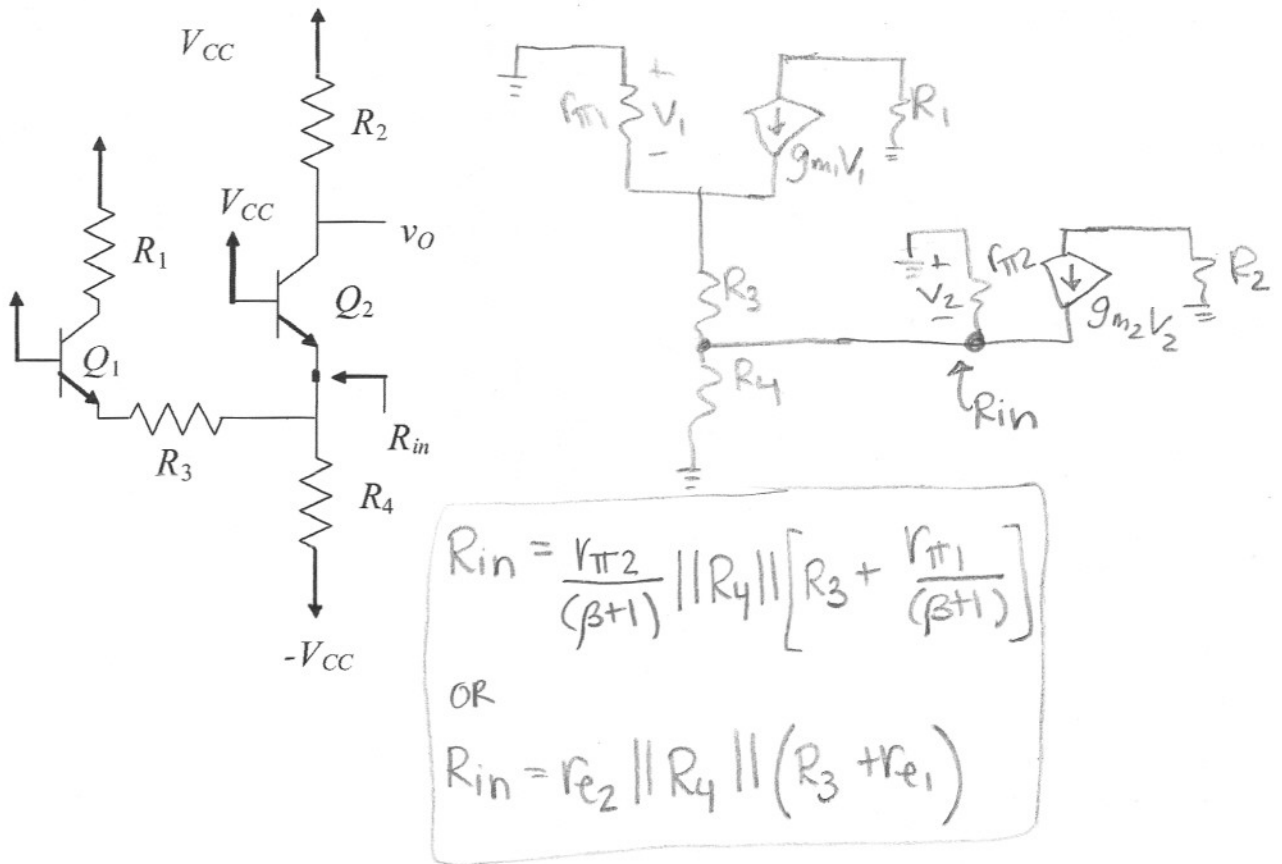- Class A, B, AB output stages
- feedback topologies
- B, A-circuit, Af
- Data converters
- Multivibrators
- Digital logic \rightarrow power implementation



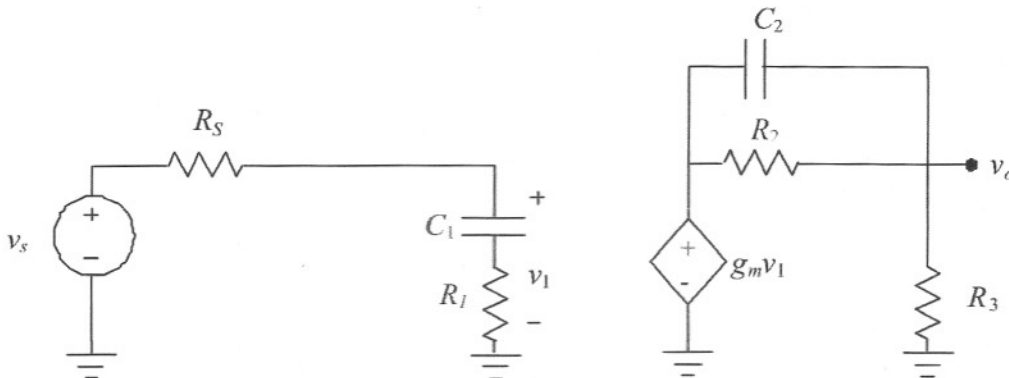5. For the circuit shown below, derive expressions for:

- the midband gain A_M , the low-frequency poles and/or zeros (if any; state if none), and the high-frequency poles and/or zeros (if any; state if none)




6. Design a MosFet differential amplifier to operate with a dc current bias of 2mA through each transistor and to provide a differential gain equal to 100V/V. The transistors have $k'_n W/L = 4 \text{ mA/V}^2$, $V_t = 1 \text{ V}$.

- State the required dc bias voltage (V_{GS}) needed for the amplifier to work correctly.
- Design a current mirror to supply the needed current bias. Draw the schematic and all values. Any value of R can be used.
- After choosing your current mirror configuration, state the minimum value for the gate voltage in order for the amplifier to operate correctly.

7

class A:

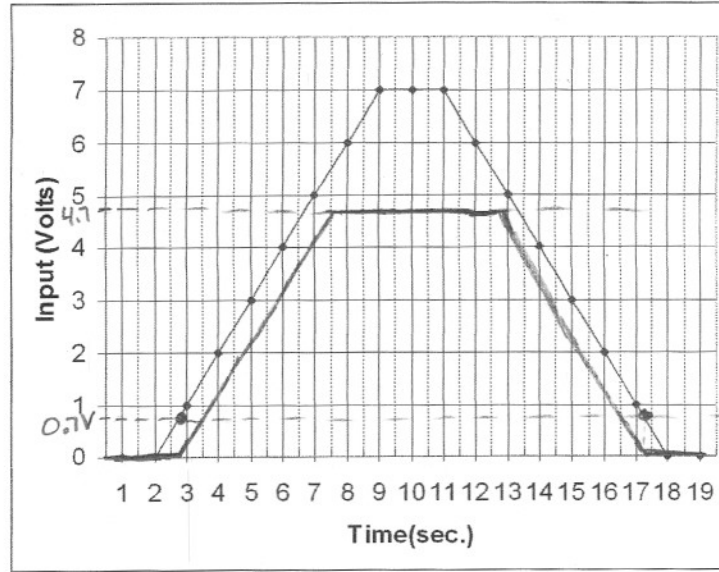


max:

$$V_{CC} - V_{CESAT} = 5 - 0.3 = 4.7V$$


min:

$$-V_{CC} + V_{CESAT} = -5 + 0.3 = -4.7V$$

class B:

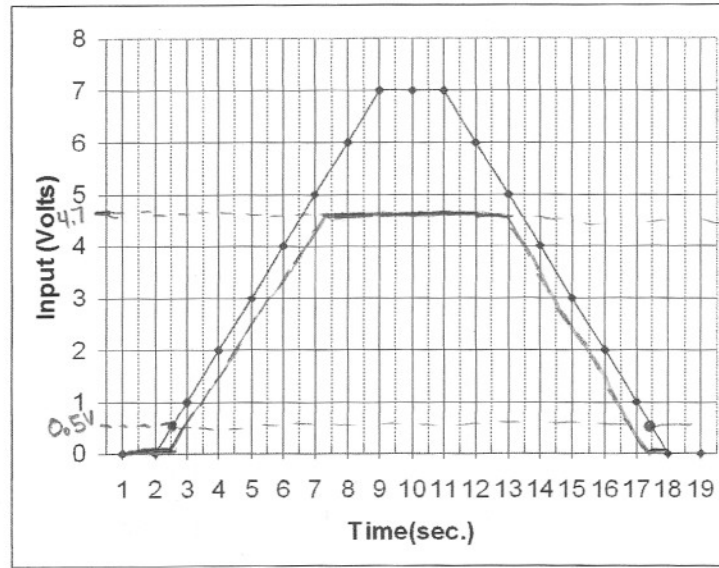


class AB:

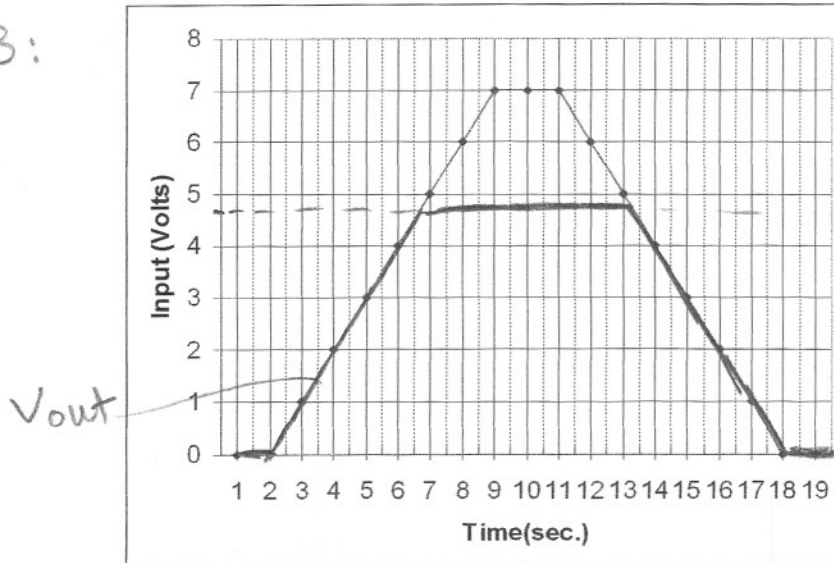

8. (i) series-shunt (ii) shunt-shunt

9.

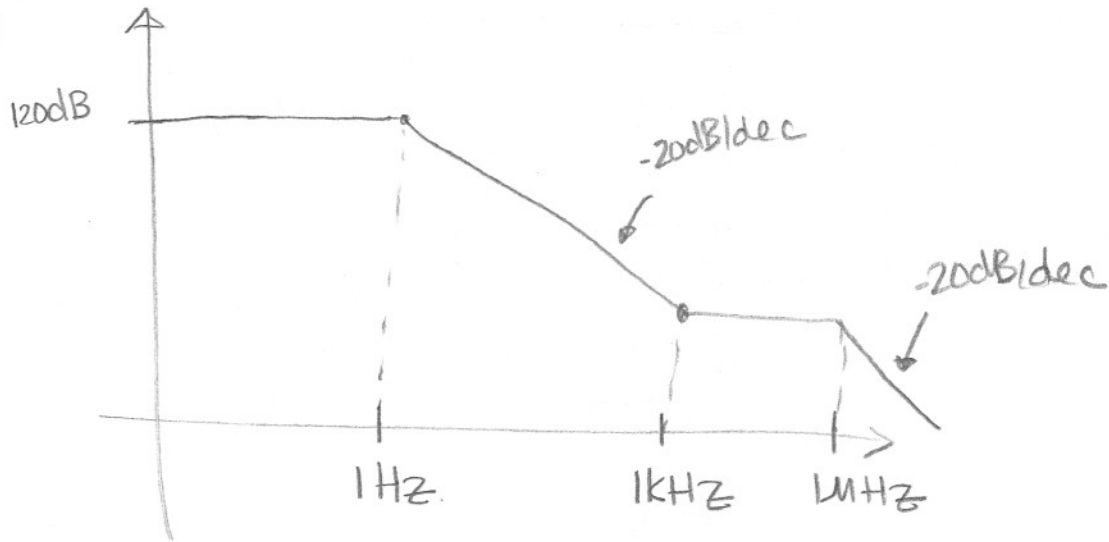

starting at 0° means no pole/zero at origin.


each -45° slope / 2dec. means pole

" $+45^\circ$ " " " zero

\therefore Since the gain is 120 dB at a very low freq. we have all poles/zeros at high-freq. \Rightarrow

$$A(s) = \frac{1 \text{ Meg} \left(\frac{s}{1\text{K}} + 1 \right)}{(s+1) \left(\frac{s}{1 \text{ Meg}} + 1 \right)}$$

10. (a) series-shunt

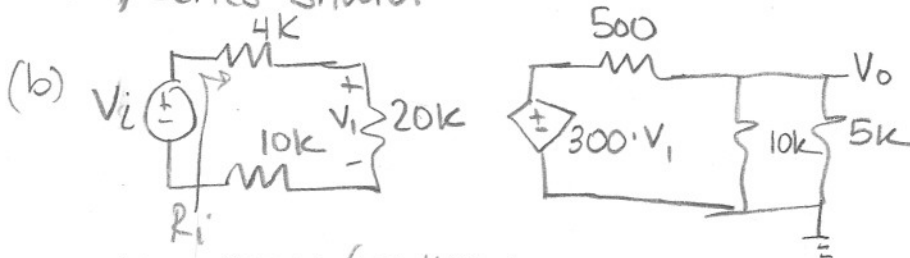

$$V_o = \frac{300 \cdot V_i (10\text{k} \parallel 5\text{k})}{(10\text{k} \parallel 5\text{k}) + 500} \approx 261 V_i$$

$$V_i = \frac{V_i \cdot 20\text{k}}{34\text{k}}$$

$$\frac{V_o}{V_i} = 261 \cdot \frac{20\text{k}}{34\text{k}} \approx 154 \text{ V/V} = A$$

$$10. (c) A_f = \frac{154}{1 + (154)(0.2)} = \boxed{4.8 \text{ V/V}}$$

$$(d) R_i = 4\text{k} + 20\text{k} + 10\text{k} = 34\text{k}$$

$$R_{if} = R_i(1 + A\beta) \approx 1 \text{ Meg}\Omega$$

$$R_{in} = R_{if} - R_s \approx \boxed{1 \text{ Meg}\Omega}$$

11. (a)

$$I_{B1} = I_{B2} = \frac{I_E}{\beta + 1}$$

$$I_{E3} = \frac{2I_E}{\beta + 1}$$

$$I_{B3} = \frac{2I_E}{(\beta + 1)^2}$$

$$I_o = I_{c1} = \left(\frac{\beta}{\beta + 1}\right) I_E$$

$$(b) I_{REF} = I_{c1} + I_{B3} = \frac{\beta}{\beta + 1} I_E + \frac{2I_E}{(\beta + 1)^2} = \frac{[\beta(\beta + 1) + 2] I_E}{(\beta + 1)^2}$$

$$\therefore I_E = \frac{I_{REF} (\beta + 1)^2}{\beta(\beta + 1) + 2} = \frac{I_{REF} (\beta + 1)^2}{\left[1 + \frac{2}{\beta(\beta + 1)}\right] \beta(\beta + 1)}$$

$$= \frac{I_{REF} (\beta + 1)}{\beta \left(1 + \frac{2}{\beta(\beta + 1)}\right)}$$


$$\therefore I_o = \left(\frac{\beta}{\beta + 1}\right) \left(\frac{\beta + 1}{\beta}\right) \left[\frac{I_{REF}}{1 + \frac{2}{\beta(\beta + 1)}} \right]$$

$$(c) \frac{I_o}{I_{REF}} = \boxed{0.99980}$$

$$(d) V_{B3} = V_{c1} = \boxed{1.4 \text{ V}}$$

12. (a) $V_+ = 2V$

(b) $V_+ = 0V$

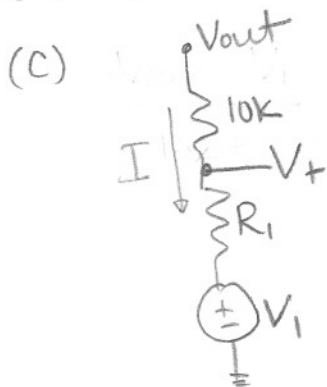

$V_{out} = +2, V_+ = 2V$

$V_+ = \frac{2 - V_1}{R_1} = \frac{2 - 2}{10k} = 0$

$\therefore V_1 = 2V$

$V_{out} = -2, V_+ = 0V$

$\frac{0 - 2}{R_1} = \frac{0 - 2}{10k}$

$\frac{2 \cdot 10k}{+2} = R_1 = 10k$

Check:

$I = \frac{V_{out} - V_1}{20k} \Rightarrow$ If $V_{out} = 2V \Rightarrow I = 0, V_+ = 2V$

When $V_{IN} = 2$ or larger, the output goes to negative rail. $\Rightarrow -2V.$ ✓

If $V_{out} = -2 \Rightarrow I = \frac{-4}{20k} = -200\mu A$


$V_+ \Rightarrow -V_{out} + 10k(I) + V_+$

$V_+ = V_{out} - 10k(I) = -2 - 10k(-200\mu) = 0V.$

13. (a)


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(b)

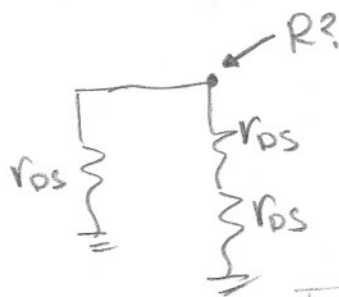

$r_{DS} \parallel 2r_{DS} = \frac{2}{3}r_{DS}$

13. (c) $A=B=C=1$

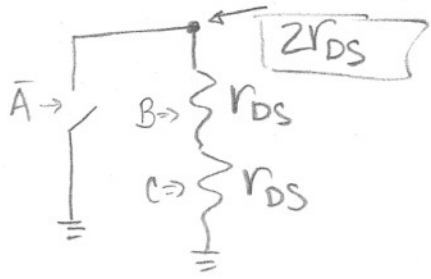

(d)
$$r_{DS} = \frac{1}{k' \left(\frac{W}{L}\right) (V_{GS} - V_t)} = \frac{1}{80 \mu \left(\frac{5 \mu}{0.5 \mu}\right) (5 - 0.5)}$$

$$\cong \boxed{278 \Omega}$$

14. $P_{tot.} = P_D + P_S$

$$100 \text{ mW} = P_S + (100 \mu) C (5)^2$$

$$- 40 \text{ mW} = P_S + (100 \mu) C (2.5)^2$$

$$60 \text{ mW} = (100 \mu C) (18.75)$$

$$\therefore C = 32 \text{ pF}$$

$$(100 \mu) = P_S + 100 \mu (32 \text{ p}) (25) \Rightarrow P_S = 20 \text{ mW}$$

(a) $P_{tot.} = 20 \text{ m} + (100 \mu) (32 \text{ p}) (4)^2 = \boxed{71.2 \text{ mW}}$

(b) $P_{tot.} = 20 \text{ m} + (50 \mu) (32 \text{ p}) (5)^2 = \boxed{60 \text{ mW}}$

(c) $P_{tot.} = \boxed{20 \text{ m}}$