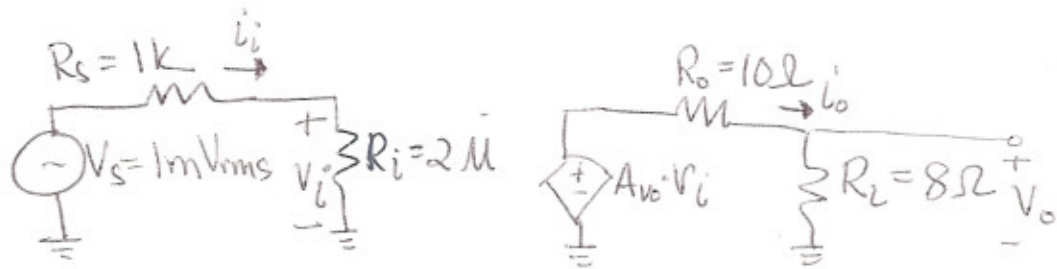


# Homework #1 Sol'n

1.



a. Voltage gain,  $v_o/v_i$ :

voltage divider  $\Rightarrow v_o = A_{vo} \cdot v_i \cdot \frac{R_L}{R_L + R_o}$

$$\frac{v_o}{v_i} = 100 \cdot \frac{8}{8+10} = \boxed{44.4 \text{ V/V}}$$

overall voltage gain,  $v_o/v_s$ :

voltage divider  $\Rightarrow v_i = v_s \cdot \frac{R_i}{R_i + R_s}$

$$v_o = \frac{A_{vo} R_L}{R_L + R_o} \cdot \frac{R_i}{R_i + R_s} \cdot v_s \Rightarrow \frac{v_o}{v_s} = \frac{100(8)}{18} \cdot \frac{2M}{2M+1K} = \boxed{44.4 \text{ V/V}}$$

$$\frac{v_o}{v_s} = 20 \log(44.4) \approx \boxed{33 \text{ dB}}$$

b. Current gain,  $i_o/i_i$ :

$$i_o = \frac{A_{vo} v_i}{R_o + R_L} \quad \text{and} \quad i_i = \frac{v_s}{R_s + R_i}$$

$$\therefore \frac{i_o}{i_i} = \frac{A_{vo}}{R_o + R_L} \cdot \frac{v_i}{v_s} \cdot \frac{R_s + R_i}{1} = \frac{100}{18} \cdot \frac{v_s \cdot R_i}{v_s (R_s + R_i)} \cdot (R_s + R_i)$$

$$\frac{i_o}{i_i} = \frac{100}{18} \cdot 2M = 11.1 \text{ MA/A}$$

OR  $i_o = \frac{v_o}{R_L}$  and  $i_i = \frac{v_i}{R_i}$

$$\therefore \frac{i_o}{i_i} = \frac{v_o}{v_i} \cdot \frac{R_i}{R_L} = 44.4 \left( \frac{2M}{8} \right) = \boxed{11.1 \text{ MA/A}} = \boxed{141 \text{ dB}}$$

1. c. (cont.)


HW 1 sol'n

$$\text{power gain} = A_{vs} \cdot A_i = (44.4 \cdot 11.1 \mu) \approx \boxed{493 \mu \frac{W}{W} \approx 87 \text{ dB}}$$

d. If  $R_i = 1 \text{ k}\Omega$ :

$$A_{vs} = \frac{A_{vo} \cdot R_L}{R_L + R_o} \cdot \frac{R_i}{R_i + R_s} = \frac{100(8)}{18} \cdot \frac{1 \text{ k}}{2 \text{ k}} = \boxed{22.2 \text{ V/V} \approx 27 \text{ dB}}$$

2.

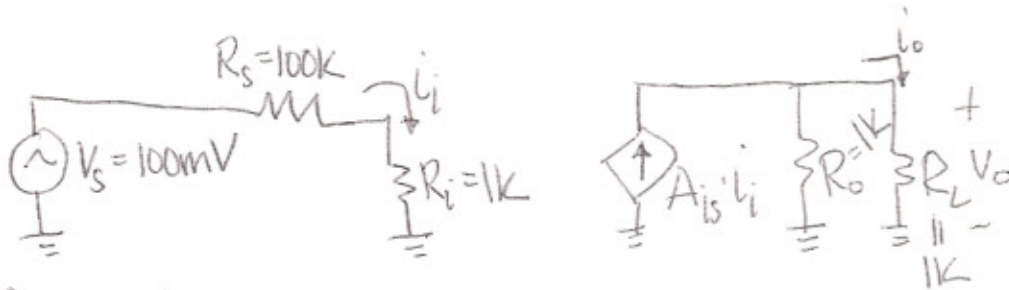

a. Current gain:  $\frac{i_o}{i_i}$

$$i_o \Rightarrow \text{current divider} \Rightarrow i_o = \frac{A_{is} i_i \cdot R_o}{R_o + R_L}$$


$$\frac{i_o}{i_i} = \frac{100(1 \text{ k})}{2 \text{ k}} = \boxed{50 \text{ A/A} \approx 34 \text{ dB}}$$

b. Voltage gain:  $v_o = A_{is} \cdot i_i \cdot (R_o \parallel R_L)$

$$i_i = \frac{v_s}{R_s + R_i} \Rightarrow \frac{v_o}{v_s} = 100 \left( \frac{1}{101 \text{ k}} \right) (500) \approx \boxed{0.5 \text{ V/V} = -6.1 \text{ dB}}$$

$$\text{c. power gain} = \frac{v_o}{v_s} \cdot \frac{i_o}{i_i} = 0.5 \text{ V/V} \cdot 50 \text{ A/A} = \boxed{25 \text{ W/W} \approx 14 \text{ dB}}$$

# HW 1 sol'n

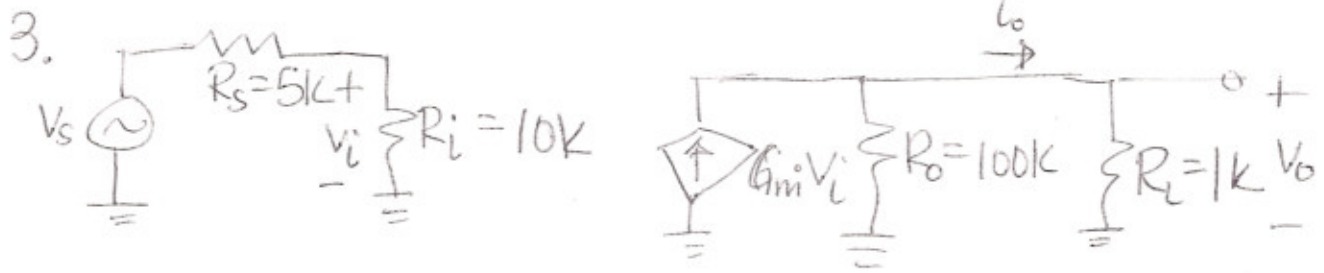

$$V_o = G_m \cdot V_i \cdot (R_o \parallel R_L) = 80m \cdot V_i \cdot (100k \parallel 1k)$$

$$V_i = \frac{V_s \cdot R_i}{R_i + R_s} = \frac{V_s \cdot 10k}{15k} = 0.67 V_s$$

$$\frac{V_o}{V_s} = 80m (0.67) (990) = \boxed{53 \frac{V}{V}}$$

4.  $i_o = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$

$$I_m = \frac{1}{2} (0.5m) (V_{GS} - 1)^2$$

$$\sqrt{4} = (V_{GS} - 1)^2$$

$$2 = V_{GS} - 1$$

$$\therefore V_{GS} = \boxed{3V}$$

$$V_{DSmin} = V_{GS} - V_t = 3 - 1 = \boxed{2V}$$


$$i_o = 0.3m \Rightarrow 0.3m = \frac{1}{2} (0.5m) (V_{GS} - 1)^2$$

$$V_{GS} \approx \boxed{2.1V}$$


$$V_{DSmin} = V_{GS} - V_t = 2.1 - 1 = \boxed{0.1V}$$

5.

HW 1 sol'n

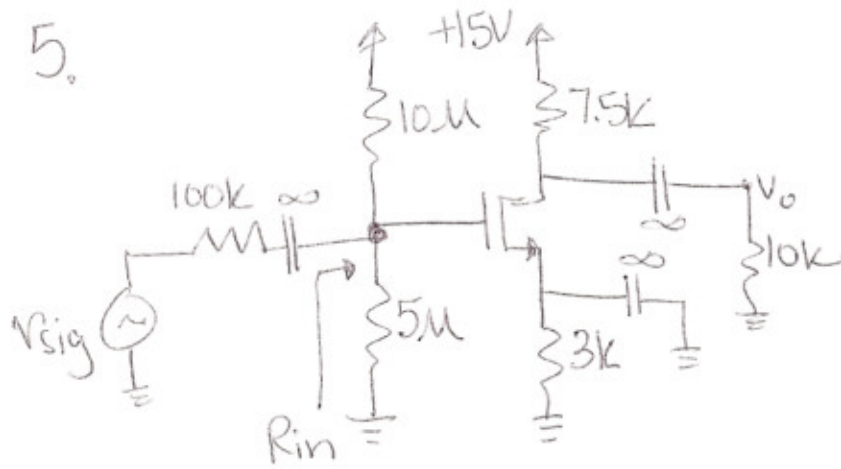

• DC analysis:

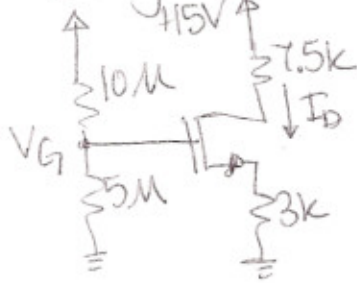

$$V_G = \frac{15(5M)}{5M + 10M} = 5V$$

$$I_D = \frac{1}{2} k_n' \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} (1m) (5 - I_D(3k) - 1)^2$$

$$2kI_D = 16 - 24kI_D + I_D^2(3k)^2$$

$$0 = 16 - 26kI_D + I_D^2(3k)^2 \Rightarrow I_D = \frac{+26k \pm \sqrt{(26k)^2 - 4(3k)^2(16)}}{2(3k)^2}$$

$$I_D = 0.002, 890\mu$$

$$I_D = 0.002(3k) = 6V \Rightarrow V_{GS} = -1 \text{ (cutoff)}$$

$$\therefore I_D \approx 890\mu, V_{GS} = 5 - 890\mu(3k) = 2.33V$$


$$V_D = 15 - 890\mu(7.5k) = 8.325V$$

$\therefore \text{SAT} \Rightarrow (V_{DS} \geq V_{GS} - V_t) \rightarrow \text{correct choice}$

parameters:  $g_m = \frac{2I_D}{V_{ov}} = \frac{2(890\mu)}{2.33 - 1} = 1.34m$

# HW1 sol'n

5. (cont.)

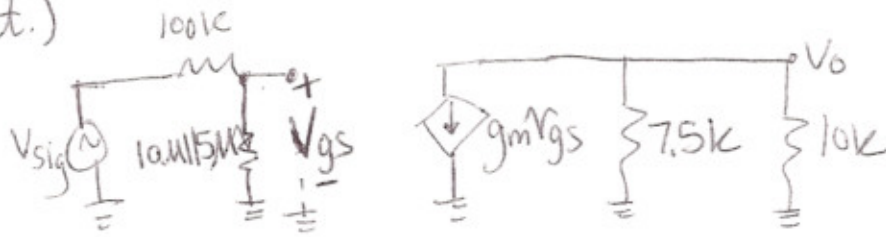

$$R_{in} = 10M \parallel 5M = \boxed{3.33M}$$

voltage divider:


$$\frac{V_{gs}}{V_{sig}} \Rightarrow V_{gs} = \frac{V_{sig}(3.33M)}{3.33M + 100K} \Rightarrow \frac{V_{gs}}{V_{sig}} = \underline{\underline{0.97 V/V}}$$

$$V_o = -g_m V_{gs} (7.5k) \parallel (10k) = (+1.34m)(4.3k) V_{gs}$$

$$\frac{V_o}{V_{gs}} = \underline{\underline{5.74}}$$

$$\frac{V_o}{V_{sig}} = \frac{V_o}{V_{gs}} \cdot \frac{V_{gs}}{V_{sig}} = 5.74(0.97) = \boxed{5.6 V/V}$$

6. a.

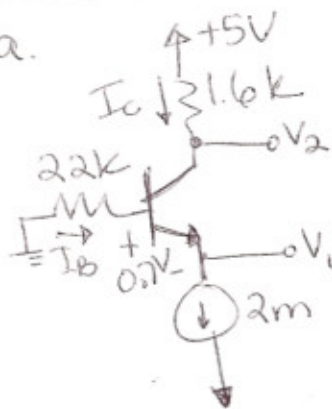

$$\beta = 50$$

$$I_E = 2m$$

$$I_B = I_E / \beta + 1 = 39.2\mu$$

$$V_B = -I_B(22k) = -0.86$$


$$V_1 = -0.7 - 0.86 = \boxed{-1.56V}$$

$$I_C \approx I_E = \frac{50}{51}(2m) = 1.96m$$

$$V_2 = 5 - 1.96m(1.6k) = \boxed{1.86V}$$

# HW1 Sol'n

6. b.

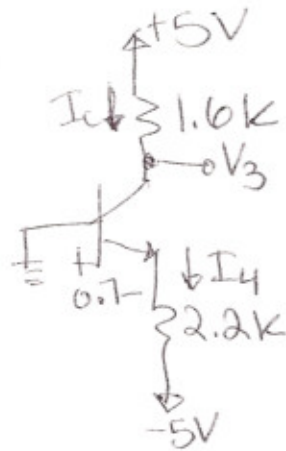


$$+0.7 + I_E (2.2k) - 5 = 0$$

$$I_E = \boxed{1.96m}$$

$$I_C = \alpha I_E = 1.92mA$$

$$v_3 = 5 - 1.6k(1.92m) = \boxed{1.93V}$$

c.

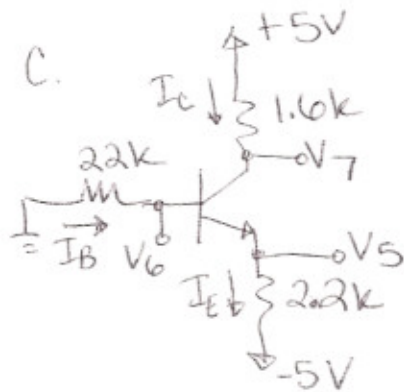

$$0 - I_B (22k) + 0.7 - I_E (2.2k) + 5 = 0$$


$$I_B = I_E / \beta + 1$$

$$\therefore I_E = 1.78mA$$

$$v_6 = I_E (2.2k) - 5 = \boxed{-1.1V}$$

$$I_C = \alpha I_E = 1.75mA$$

$$v_7 = 5 - 1.6k(1.75m) = \boxed{2.2V}$$

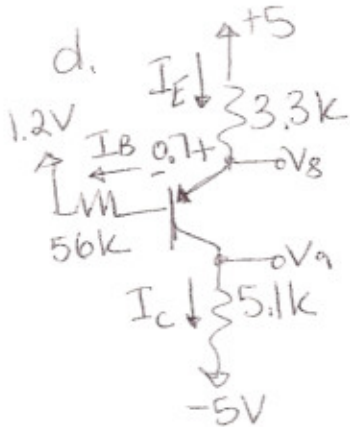

$$+5 - 3.3k I_E - 0.7 - I_B (56k) - 1.2V = 0$$

$$(I_B = I_E / \beta + 1)$$

$$\therefore I_E = 0.70mA$$



$$v_8 = 5 - 0.70m(3.3k) = \boxed{2.7V}$$

$$I_C = \alpha I_E = \frac{50}{51} (0.70m) = .69mA$$

$$v_8 = 5 - 0.8m(3.3k) = 2.3V$$

$$v_9 = 5.1k(.69m) - 5 = \boxed{-1.48V}$$

# HW 1 sol'n

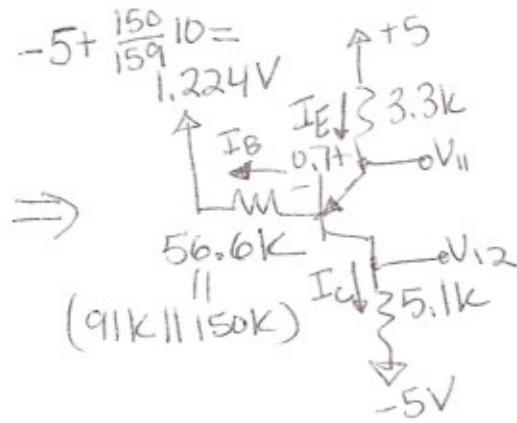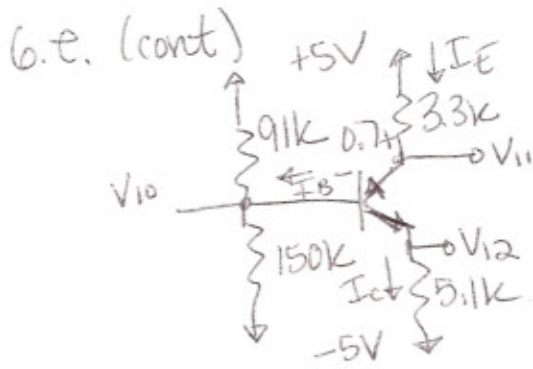

$$5 - I_E(3.3k) - 0.7 - I_B(56.6k) - 1.224 = 0$$

$(I_B = I_E/\beta + 1)$


$$I_E = 0.7m$$

$$V_{11} = 5 - 0.7m(3.3k) = \boxed{2.7V}$$

$$I_C \approx I_E = \frac{50}{51}(0.7m) = 0.69m$$

$$V_{12} = 5.1k(0.69m) - 5 = \boxed{-1.48V}$$
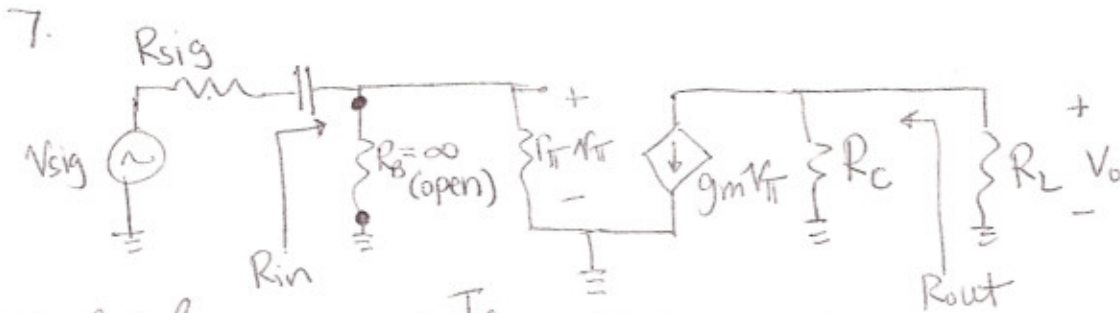
$$V_{10} = -0.7 + V_{11} = 2.7 - 0.7 = \boxed{2V}$$



$$5k\Omega = r_{\pi} = \frac{\beta}{g_m}, \quad g_m = \frac{I_C}{V_T} = \frac{0.5m}{25m} = 20mA/V$$

$$R_{in} = r_{\pi} = \boxed{5k\Omega}$$

$$A_{vo} \Rightarrow -g_m v_{\pi} (R_c \parallel R_L) = -g_m \left( \frac{V_{sig} \cdot r_{\pi}}{r_{\pi} + R_{sig}} \right) (R_c \parallel R_L) = V_o$$

$$\frac{V_o}{V_{sig}} = -20m \left( \frac{5k}{5k + 1k} \right) (20k \parallel 1k) = \boxed{-15.9V/V}$$

$$R_{out} = R_c = \boxed{20k\Omega}$$