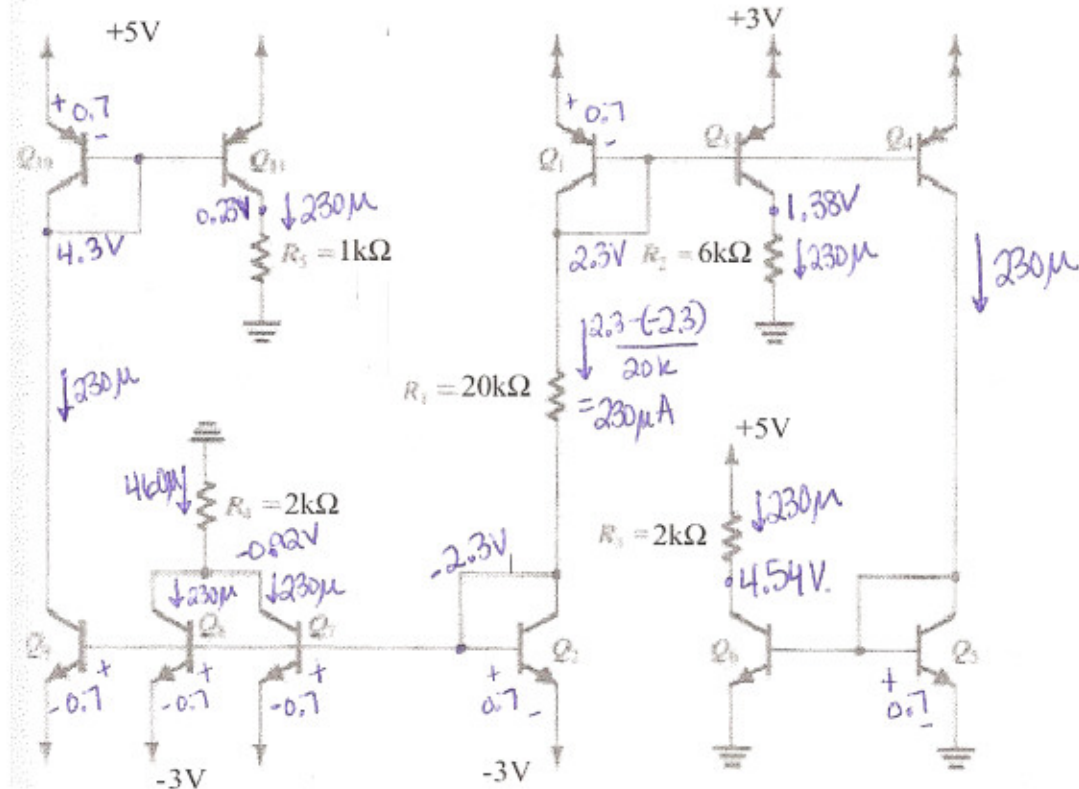


(Due Sept. 7 by 6pm in homework locker)

1. Design the circuit of Fig. 6.4 to obtain an output current whose nominal value is $25\mu\text{A}$. Find R when Q_1 and Q_2 are matched with channel lengths of $1\mu\text{m}$, channel widths of $10\mu\text{m}$, $V_t=1\text{V}$, $k'_n=100\mu\text{A}/\text{V}^2$, $V_A=20\text{V}$, $V_{DD}=3\text{V}$ and $I_{REF}=25\mu\text{A}$. What is the minimum allowable value of V_o for proper operation? What is the output resistance? What is the change in the output current when V_o is changed by $+1\text{V}$?


2. Design the circuit of Fig. 6.10 to obtain an output current whose nominal value is $100\mu\text{A}$ when V_o is 2V . Find R , I_{REF} , $V_{o\text{min}}$ when $I_s=10^{-15}\text{A}$, $\beta=100$, $V_{CC}=6\text{V}$, and $V_A=60\text{V}$. If V_o is changed to 5V , what is I_o ?

3. Find voltages at all nodes and currents through all branches in the circuit below. Assume $|V_{BE}| = 0.7\text{V}$ and $\beta=\infty$.



4. Design a current source that generates a constant current $I_o=50\mu\text{A}$ that operates from a 3V supply. State all values if resistors are used. Assume that V_{BE} is 0.7V at a current of 1mA and neglect the effect of a finite β . You can only use resistors that are less than $50\text{k}\Omega$.

HW #2 solution

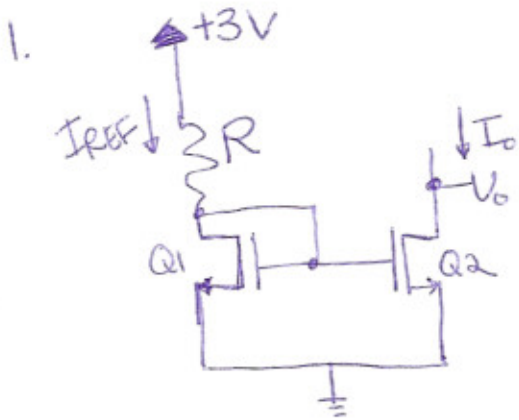

Want $I_o = 25\mu A$,
 $\left(\frac{W}{L}\right)_{Q1} = \left(\frac{W}{L}\right)_{Q2} = \frac{10\mu m}{1\mu m} = 10$

Let $I_{REF} = I_o = 25\mu$

$$I_o = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$$

$$\sqrt{\frac{25\mu(2)}{(100\mu \cdot 10)}} = (V_{GS} - V_t)^2$$

$$.22 + V_t = V_{GS}$$

$$\therefore V_{GS} = 1.22V$$

$$R = \frac{3 - V_{GS}}{I_{REF}} = \frac{(3 - 1.22)}{100\mu} = \boxed{17.8K\Omega}$$

$V_{o\min}$ will occur when $V_{DS} = V_{GS} - V_t$

$$\therefore \boxed{V_{o\min} = 0.22V}$$


$$R_{out} = r_{o2} = \frac{V_A}{I_o} = \frac{20}{25\mu} = \boxed{800K\Omega}$$

The output current will be $25\mu A$ at $V_o = 0.22V$. If V_o changes by $+1V$, then I_o will change

$$\Delta I_o = \frac{\Delta V_o}{r_{o2}} = \frac{1V}{800k} = \boxed{1.25\mu A}$$

$$\therefore I_o = 26.25\mu \text{ at } V_o = 1.22V$$

2.

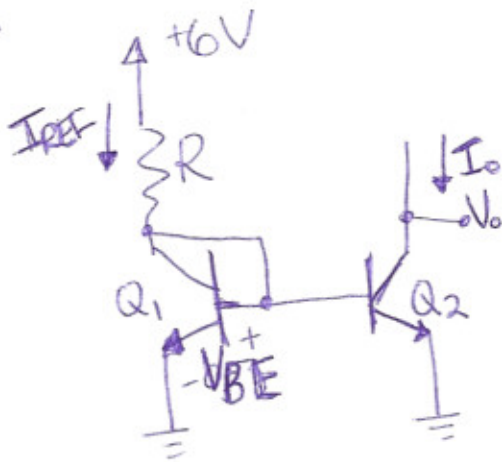

$$I_o = 100 \mu\text{A}$$

$$V_o = 2\text{V}$$

Assume $V_{BE} = 0.7$

$$I_o = \frac{I_{REF}}{1 + \frac{2}{\beta}} \left[1 + \frac{(V_o - V_{BE})}{V_A} \right]$$

$$I_o = 100 \mu\text{A} = \frac{I_{REF}}{1 + \frac{2}{100}} \left[1 + \frac{(2 - 0.7)}{60} \right]$$

$$\therefore I_{REF} = 100 \mu\text{A} \cdot 1.02 \cdot (.9788)$$

$$I_{REF} = \boxed{99.8 \mu\text{A}}$$

$$R = \frac{V_{CC} - V_{BE}}{I_{REF}} = \boxed{53.1 \text{K}\Omega}$$

$V_o = 5\text{V}$:

$$I_o = \frac{99.8 \mu}{1 + \frac{2}{100}} \left[1 + \frac{(5 - 0.7)}{60} \right] = 97.8 \mu \cdot 1.072 = \boxed{104.8 \mu\text{A}}$$

$V_{o\text{min}}$ occurs when Q_2 goes from active to another state. This happens when


$$V_{CE} = 0.3\text{V} \quad (\text{see Table 6.3})$$

Since $V_E = 0\text{V}$ (gnd).


$$\therefore V_{o\text{min}} = \boxed{0.3\text{V}}$$

4.

TRADITIONAL

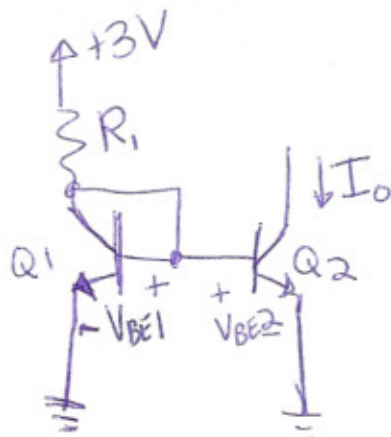

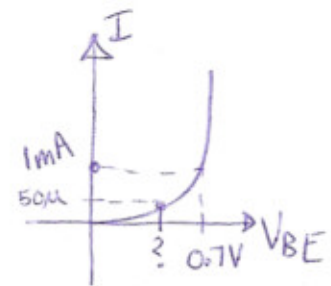→ We know that it is given that $V_{BE} = 0.7$ at 1mA .



To find V_{BE} at a lesser current,


$$V_{BE1} = 0.7 + V_T \ln\left(\frac{I_{REF} = 50\mu}{1\text{m}}\right) = 0.625\text{V}$$

$$R_1 = \frac{3 - 0.625}{50\mu} = \boxed{47.5\text{k}\Omega} < 50\text{k}$$

Widlar ⇒

Choose
 $I_{REF} = 1\text{mA}$
 So that $V_{BE1} = 0.7$
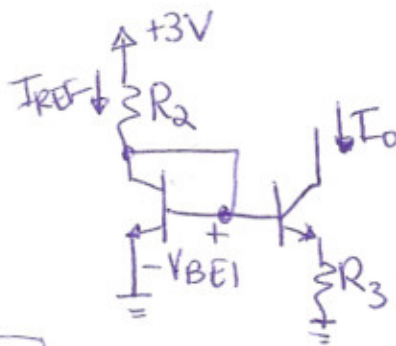
$$R_2 = \frac{3 - 0.7}{1\text{m}} = \boxed{2.3\text{k}}$$



$$I_o R_3 = V_T \ln\left(\frac{I_{REF}}{I_o}\right)$$

$$R_3 = \frac{25\text{m}}{50\mu} \ln\left(\frac{1\text{m}}{50\mu}\right)$$

$$R_3 = \boxed{1.5\text{k}\Omega}$$

∴ R's < 5kΩ