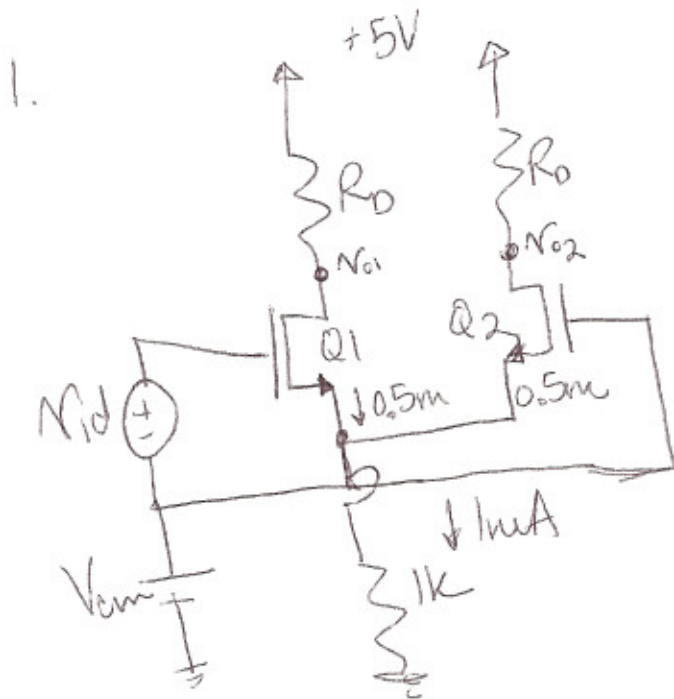


# HW #3 sol'n



$$k_n' \frac{W}{L} = 3 \text{ mA/V}^2$$

$$V_t = 0.9 \text{ V}$$

ignoring  $\lambda$

a. To get 0.5mA through the transistor requires  $\Rightarrow$   
 $0.5 \text{ m} = \frac{1}{2} (3 \text{ m}) (V_{ov})^2$

$$V_{ov} \approx 0.6 \text{ V}$$

$$V_s = 1 \text{ m} (1 \text{ k}) = 1 \text{ V}$$

$$\therefore V_G - V_s - V_t = 0.6 \text{ V}$$


$$\Rightarrow V_G = 1 + 0.9 + 0.6 = 2.5 \text{ V} = V_{cm}$$

b.  $A_d = 10 \text{ V/V} = g_m R_D$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2(0.5 \text{ mA})}{0.6} = 1.7 \text{ mA/V}$$

$$\therefore R_D = 5,882 \Omega$$

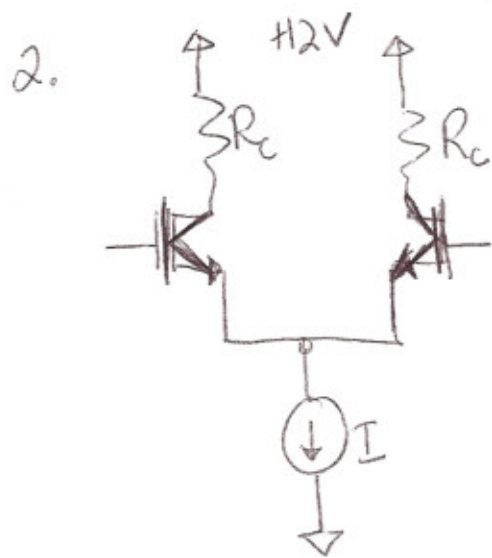c.  $V_{o1} = V_{o2} = 5 - (0.5 \text{ m})(5.882 \text{ k}) = 2.1 \text{ V}$



$$R_{id} = 20k = 2r_{\pi}$$

$$r_{\pi} = 10k\Omega = \beta / g_m = \frac{\beta \cdot V_T}{I_c}$$

$$\therefore I_c = \frac{100 \cdot 25m}{10k} = 250\mu A$$

$$I = 0.5mA$$

$$A_d = 150V/V = g_m R_c$$

$$g_m = \frac{I_c}{V_T} = \frac{250\mu}{25m} = 10mA/V$$

$$\therefore R_c = 15k\Omega$$

3.  $\frac{v_o}{v_{id}} = 100V/V$

Refer to Fig. 7.28(a)

Note that  $r_o$  only gives a single-ended gain  $\Rightarrow A_d = \frac{1}{2} g_m r_o = \frac{1}{2} \cdot \frac{2I_D}{V_{ov}} \cdot \frac{V_A}{I_D}$

$$A_d = \frac{V_A}{V_{ov}}$$

$$100 = \frac{30}{V_{ov}} \Rightarrow V_{ov} = 0.3V$$

Note that the output node has a summation of  $2I_D$  (see page. 729)

$$I = 2I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{ov})^2 = \frac{1}{2} (3m)(0.3)^2$$


$$I = 135\mu A$$

4. Refer to Fig. 7.32(a)

$$G_m = \frac{I/2}{V_T} = 4 \text{ mA/V}$$

$$I = 0.2 \text{ mA}$$
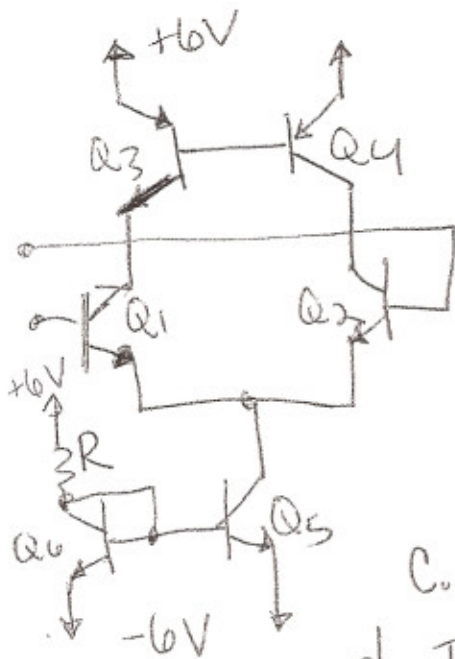
$$R = \frac{6 - (-6) - V_{BE}}{I} = \frac{11.3}{.2 \text{ m}} = \underline{\underline{56.5 \text{ k}\Omega}}$$



$$a. R_{id} = (\beta + 1) 2r_e$$

$$r_e = \frac{V_T}{I/2} = \frac{25 \text{ mV}}{0.1 \text{ mA}} = 250$$

$$R_{id} = \underline{\underline{50.5 \text{ k}\Omega}}$$


$$b. R_o = \frac{r_o}{2} = \frac{V_A}{2I_C} = \frac{80}{2(0.1 \text{ mA})} = \underline{\underline{400 \text{ k}\Omega}}$$

$$c. A_d = g_m R_o = 4 \text{ m}(400 \text{ k}) = \underline{\underline{1,600 \text{ V/V}}}$$

$$d. I_B = \frac{I/2}{(\beta + 1)} = \frac{0.2 \text{ mA}/2}{101} \approx \underline{\underline{1 \mu\text{A}}}$$
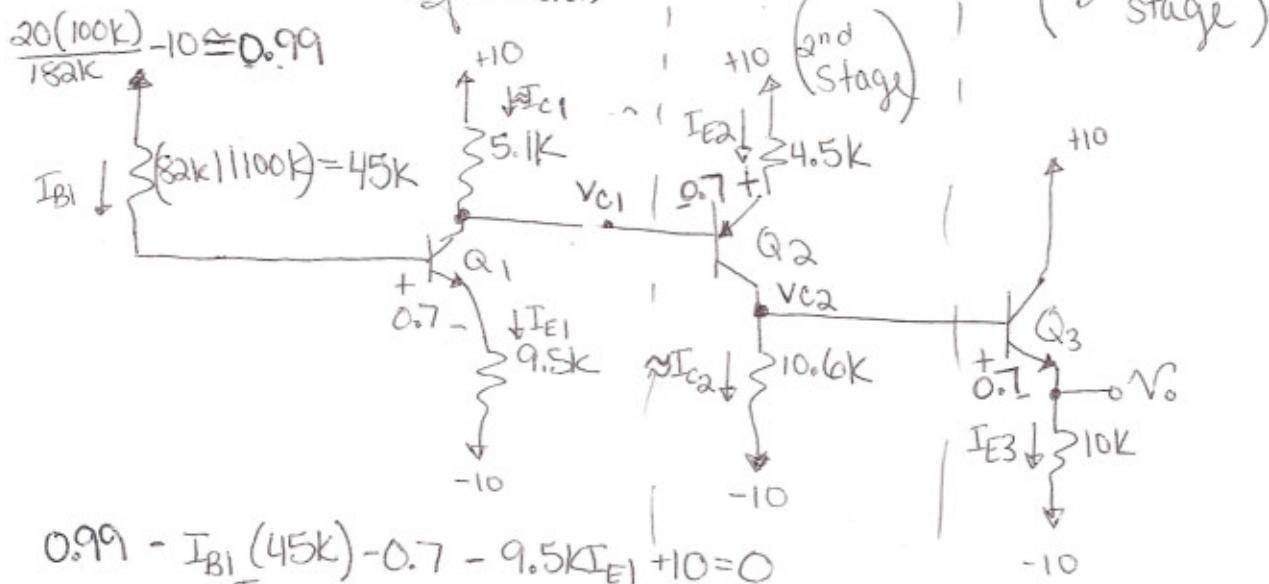
## 5. DC Analysis:

1st stage  $\Rightarrow$  (Thevenin equivalent)



$$0.99 - I_{B1}(45k) - 0.7 - 9.5kI_{E1} + 10 = 0$$

$$I_{B1} = \frac{I_{E1}}{(\beta+1)}$$

$$10.99 - 0.7 = \left[ 9.5k + \frac{45k}{(\beta+1)} \right] I_{E1} \Rightarrow I_{E1} = \frac{10.29}{9.8k} = 1.05 \text{ mA}$$

$$I_{C1} = \alpha I_{E1} = \boxed{1.04 \text{ mA}}$$

$$V_{C1} \approx 10 - (1.04 \text{ mA})(5.1k) = 4.7 \text{ V} \Rightarrow V_{E2} = 4.7 + 0.7 = 5.4 \text{ V}$$

$$I_{E2} = \frac{10 - 5.4}{4.5k} = 1.02 \text{ mA} \Rightarrow I_{C2} = \boxed{1.01 \text{ mA}}$$

$$V_{C2} \approx I_{C2}(10.6k) - 10 = 0.7 \text{ V}$$

$$V_{Ooc} = V_{C2} - 0.7 = \boxed{0 \text{ V}}$$


will vary up to 1 V. based on current value.

$$I_{E3} = \frac{0 - (-10)}{10k} = \boxed{1 \text{ mA}}$$

Note: All transistors are operating at approximately  $I_C \approx 1 \text{ mA}$

5. (cont.)

small-signal model  
(stage 1)

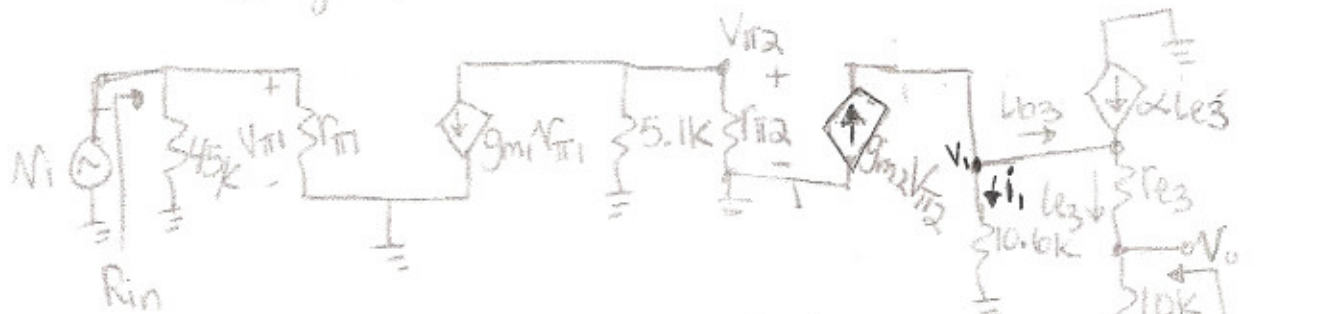

$$R_{in} = 45k \parallel r_{\pi 1} \quad \text{where} \quad r_{\pi 1} = \frac{\beta V_T}{I_{c1}} = \frac{150(25m)}{1.04m} = 3.6k\Omega$$

$$R_{in} \approx 3.3k\Omega$$

$$R_{out} = 10k \parallel (r_{e3} + \frac{10.6k}{\beta}) \Rightarrow r_{e3} = \frac{V_T}{I_{E3}} = \frac{25m}{1m} = 25\Omega$$

$$R_{out} \approx 94\Omega$$

$$v_o = i_{e3} \cdot 10k$$

$$\begin{aligned} -i_{e3} + \alpha i_{e3} + g_{m2} v_{i2} - i_1 &= 0 \\ i_1 = \frac{v_1}{10.6k} &= \frac{(g_{m2} v_{i2} + \alpha i_{e3})(10.6k \parallel (r_{e3} + 10k))}{10.6k} \\ +(\alpha - 1) i_{e3} + g_{m2} v_{i2} - g_{m2} v_{i2} \frac{10.6k \parallel (r_{e3} + 10k)}{10.6k} & \\ -2 i_{e3} \frac{10.6k \parallel (r_{e3} + 10k)}{10.6k} &= 0 \end{aligned}$$

$$v_{i2} = -g_{m1} r_{\pi 1} (5.1k \parallel r_{\pi 2})$$

$$v_{i2} = v_i$$

$$g_{m1} = \frac{I_{c1}}{V_T} = \frac{1.04m}{25m} = 41.6mA/V$$

$$g_{m2} = \frac{I_{c2}}{V_T} = \frac{1.01m}{25m} = 40.4mA/V$$

$$\begin{aligned} i_{e3} (.49) &= +20.8m v_{i2} \\ i_{e3} &= 42.4m v_{i2} \end{aligned}$$

$$\frac{v_o}{v_i} = 10k [42.4m] (-g_{m1} r_{\pi 1} (5.1k \parallel r_{\pi 2}))$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{c2}} = 3713$$

$$\frac{v_o}{v_i} = (10k)(42.4m)(-89.4) = 37.9k V/V$$