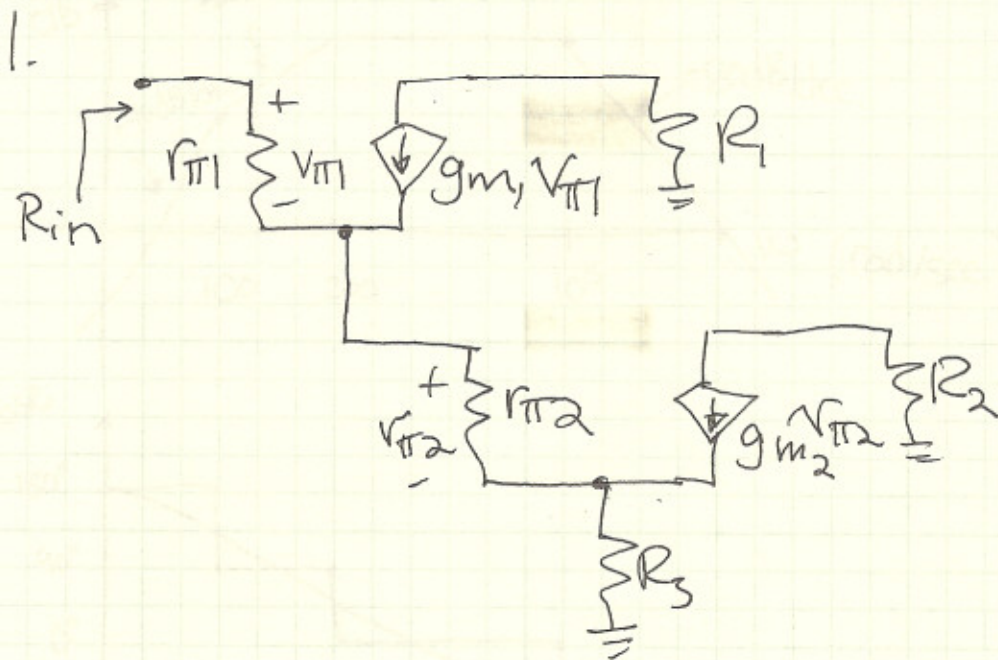


# HW #4 sol'n



$$R_{in} = r_{\pi 1} + r_{\pi 2}(\beta + 1) + R_3(\beta + 1)^2$$

or

$$R_{in} = (\beta + 1)r_{e1} + r_{e2}(\beta + 1)^2 + R_3(\beta + 1)^2$$


2.

$$H(s) = \frac{10 \cdot s \cdot s \cdot 100 \cdot 200}{\frac{s}{200} \cdot \frac{s}{100} (1 + \frac{100}{s}) (1 + \frac{200}{s}) (\frac{s}{10^5} + 1)}$$

$$= \frac{200,000}{(1 + \frac{100}{s}) (1 + \frac{200}{s}) (\frac{s}{10^5} + 1)}$$

pole frequencies: 100, 200 rad/sec.  
 zero frequencies: 2 at origin (0)  
 midband gain: (dB)  $20 \log(200,000) = 106 \text{ dB}$

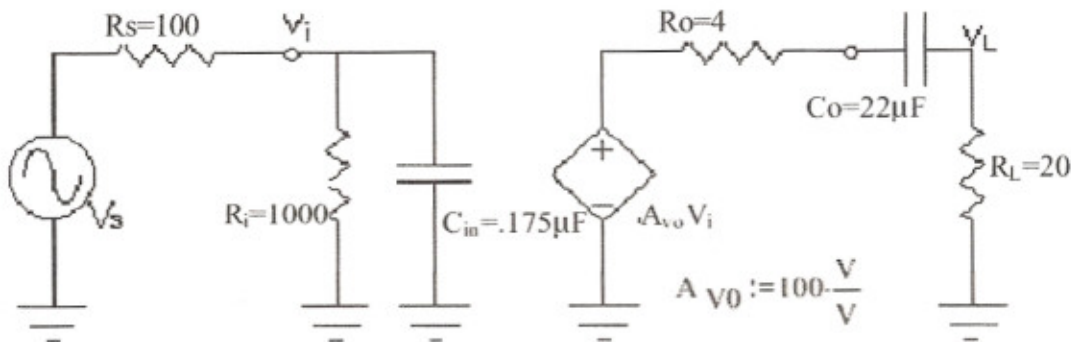3. Analyze the circuit below to find the overall gain:  $V_L/V_s$ . Sketch the Bode plots. Find
- the midband gain  $A_M$
  - the low-frequency 3-dB point  $f_L$
  - the high-frequency 3-dB point  $f_H$




4. For the circuit shown below, derive symbolic expressions for:

- the midband gain  $A_M$
- the low-frequency 3-dB point  $f_L$
- the high-frequency 3-dB point  $f_H$

Next, state the actual value for all 3 expressions.

- Sketch the Bode magnitude plot
- State the phase angle at a very, very high frequency

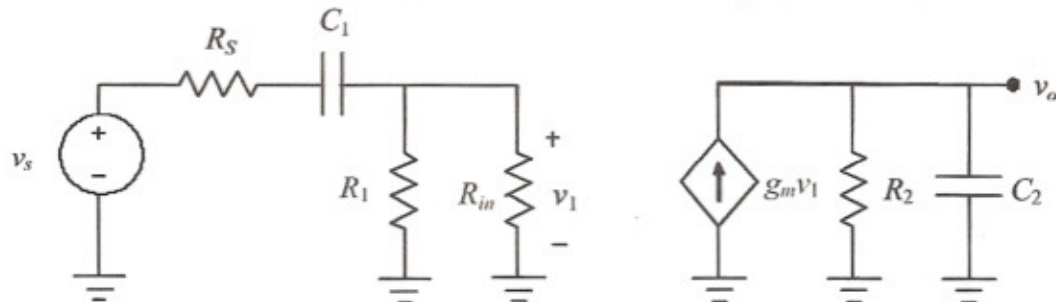To keep the expressions readable, express in parallel resistances as  $(R_A \parallel R_B)$  for example, *not*  $R_A R_B / (R_A + R_B)$ .





Let  $g_m = 1\text{mA/V}$ ,  $R_S = 100$ ,  $C_1 = 10\mu\text{F}$ ,  $R_1 = 100\text{k}\Omega$ ,  $R_{in} = 100\text{k}\Omega$ ,  $R_2 = 1\text{k}\Omega$ ,  $C_2 = 1\mu\text{F}$ .

3. (cont.)

$$\frac{v_L}{v_S} = \frac{0.44 \cdot s}{8 \cdot 5.81m \left(1 + \frac{1}{528\mu s}\right) (1 + 16\mu s)}$$

poles  $\Rightarrow$  1894, 62,500

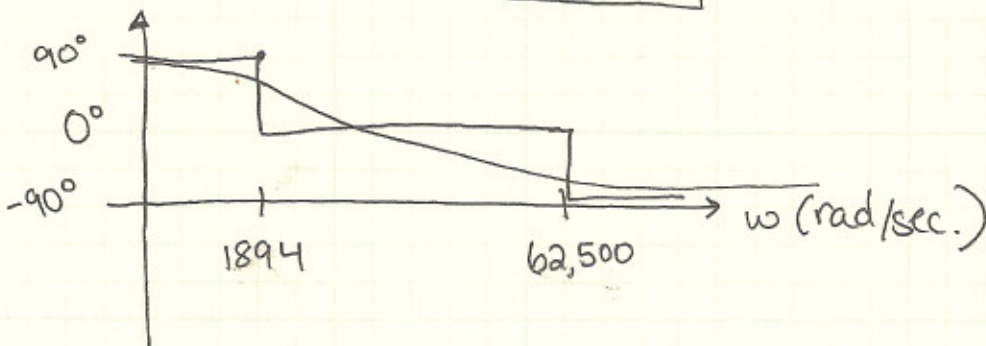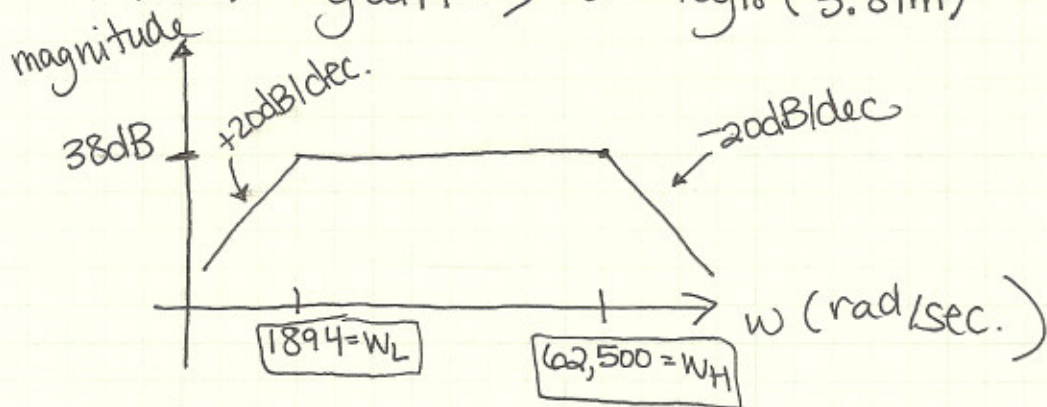midband gain  $\Rightarrow 20 \log_{10} \left(\frac{0.44}{5.81m}\right) \approx 38dB$



- phase at midband  $\approx 0^\circ$
- $-90^\circ$  at very high freq.

$$4. \quad v_o = g_m v_i (R_2 \parallel \frac{1}{C_2 \cdot s}) = g_m v_i \frac{R_2 \cdot \frac{1}{C_2 \cdot s}}{R_2 + \frac{1}{C_2 \cdot s}} = \frac{g_m v_i R_2}{R_2 \cdot C_2 \cdot s + 1}$$

$$v_i = \left[ \frac{v_s (R_1 \parallel R_{in})}{(R_1 \parallel R_{in}) + R_s + \frac{1}{C_1 \cdot s}} \right] \cdot \frac{C_1 \cdot s}{C_1 \cdot s}$$

$$v_i = \frac{v_s (R_1 \parallel R_{in}) \cdot C_1 \cdot s}{[(R_1 \parallel R_{in}) + R_s] \cdot C_1 \cdot s + 1}$$



$$v_i = \frac{v_s (R_1 \parallel R_{in}) C_1 \cdot s}{[(R_1 \parallel R_{in}) + R_s] C_1 \cdot s \left[ 1 + \frac{1}{[(R_1 \parallel R_{in}) + R_s] C_1 \cdot s} \right]}$$

$$\frac{v_o}{v_s} = \frac{g_m R_2 (R_1 \parallel R_{in}) \cdot v_s}{\underbrace{(R_2 C_2 \cdot s + 1)}_{\text{High}} \left[ 1 + \frac{1}{\underbrace{[(R_1 \parallel R_{in}) + R_s] C_1 \cdot s}_{\text{Low}}} \right] [(R_1 \parallel R_{in}) + R_s]}$$

midband gain =  $20 \log_{10} \left[ \frac{g_m R_2 (R_1 \parallel R_{in})}{(R_1 \parallel R_{in}) + R_s} \right]$   
 $= 20 \log_{10} [0.998] = \boxed{-0.017 \text{ dB}}$

$$\omega_L \cong 2 \text{ rad/sec} = \frac{1}{[(R_1 \parallel R_{in}) + R_s] C_1}$$
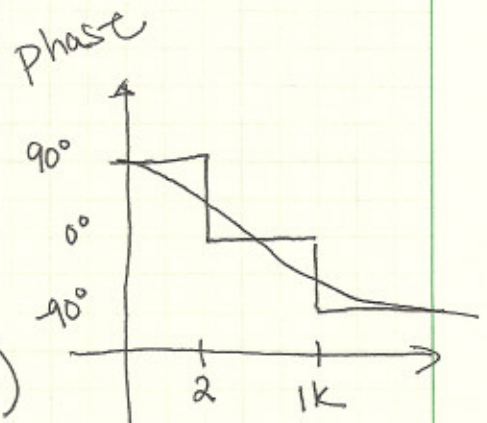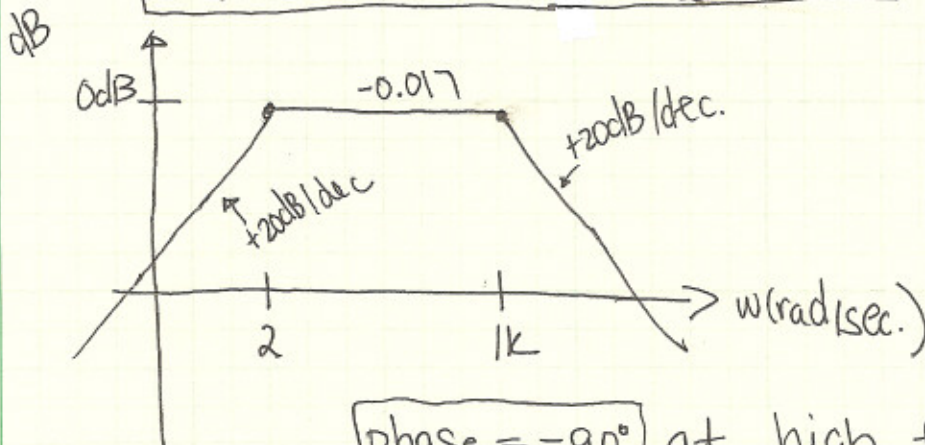
$$\omega_H = 1 \text{ K rad/sec} = \frac{1}{R_2 C_2}$$




$\boxed{\text{phase} = -90^\circ}$  at high freq.

(Due Sept. 21 by 6pm in homework locker)

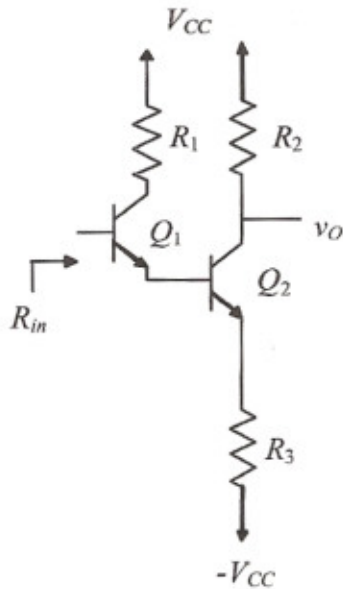1. Assume the transistors below have a finite  $\beta$  and an infinite Early voltage.

Write an expression for the input resistance  $R_{in}$  in the circuit shown below. Your expression should include *only* real resistances ( $R_1$ ,  $R_2$ ,  $R_3$ , or a subset of these) and possibly  $\beta$ ,  $r_{e1}$ , and  $r_{e2}$ . (Assume both transistors have the same  $\beta$ .) Circle your answer. *Hint: Use Resistance-Reflection rule*





2. An amplifier has the following transfer function:

$$H(s) = \frac{10s^2}{(s/100 + 1)(s/200 + 1)(s/10^5 + 1)}$$


- List the pole frequencies
- List the zero frequencies
- State the midband gain in dB
- Sketch the Bode plots for this system, labeling frequencies, gains, and slopes of interest.

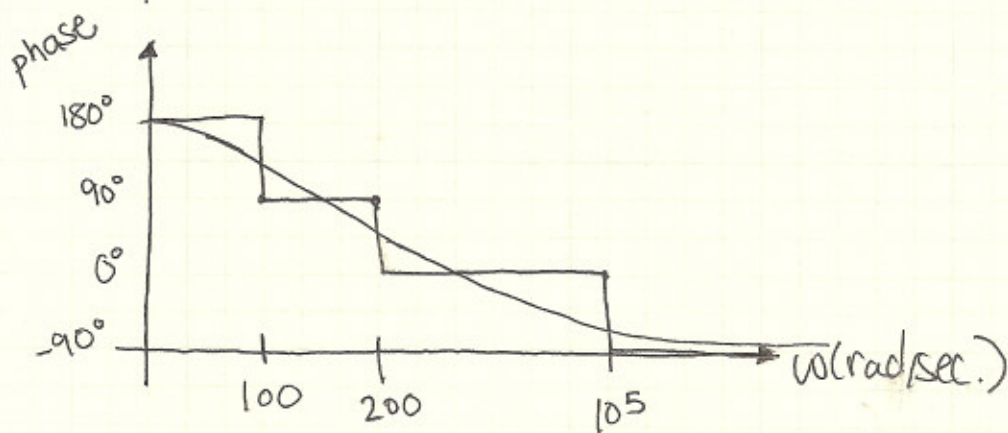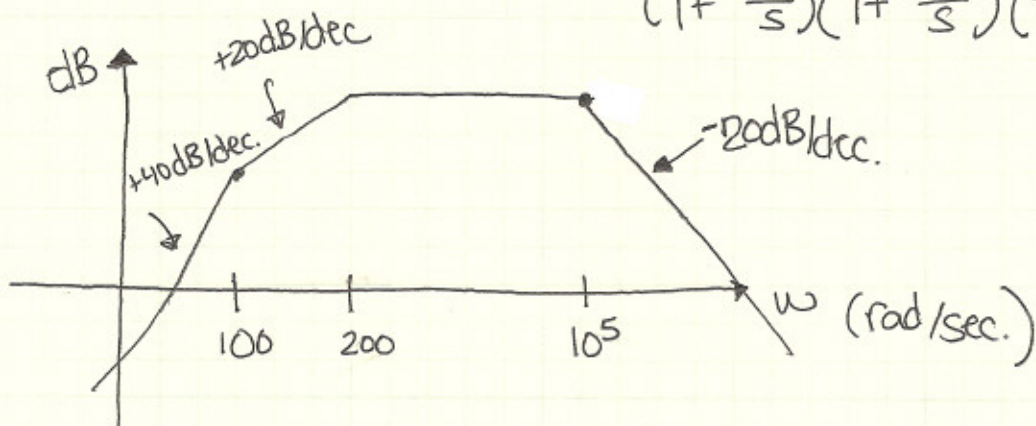2. (cont.)

$$H(s) = \frac{200,000}{\left(1 + \frac{100}{s}\right)\left(1 + \frac{200}{s}\right)\left(\frac{s}{10^5} + 1\right)}$$



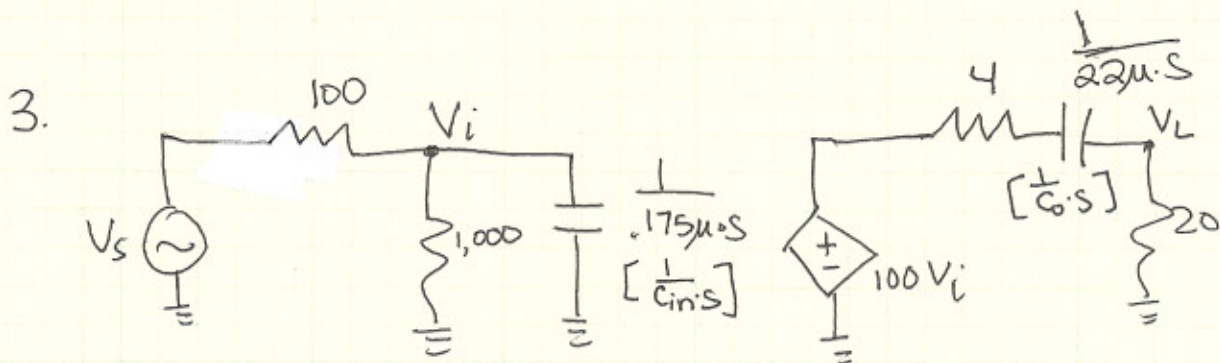There is no phase shift during the midband gain. There is a  $-90^\circ$  shift at high frequencies.



$$V_L = \frac{20 \cdot 100 \cdot V_i}{20 + 4 + \frac{1}{C_0 \cdot s}} = \frac{2000 \cdot 22 \mu \cdot s \cdot V_i}{(24 \cdot 22 \mu \cdot s + 1)}$$

$$V_L = \frac{44 \text{ m} \cdot s \cdot V_i}{528 \mu \cdot s + 1}$$

$$V_i = \frac{[1,000 \parallel \frac{1}{C_0 \cdot s}] \cdot V_s}{[1,000 \parallel \frac{1}{C_0 \cdot s}] + 100}$$

$$[1,000 \parallel C_0 \cdot s] = \frac{[1,000 \cdot \frac{1}{C_0 \cdot s}]}{(1,000 + \frac{1}{C_0 \cdot s})} = \frac{C_0 \cdot s \cdot 1,000}{(1,000 \cdot C_0 \cdot s + 1)}$$

$$V_i = \frac{1,000 \cdot V_s}{(1,000 C_0 \cdot s + 1)} = \frac{1,000 \cdot V_s}{1,000 + 100,000 C_0 \cdot s + 100}$$

$$\frac{1,000 \cdot V_s}{1,000 + 100(1,000 C_0 \cdot s + 1)}$$

$$\frac{1,000 \cdot V_s}{(1,000 C_0 \cdot s + 1)}$$

$$V_i = \frac{100 \cdot 10 \cdot V_s}{100(11 + 1,000 C_0 \cdot s)} = \frac{10 \cdot V_s}{(11 + 175 \mu \cdot s)}$$

$$\frac{V_L}{V_s} = \frac{44 \text{ m} \cdot V_s \cdot 10 \cdot s}{(528 \mu \cdot s + 1)(11 + 175 \mu \cdot s)} = \frac{0.44 \cdot s}{528 \mu \cdot s (1 + \frac{1}{528 \mu \cdot s}) \cdot 11 \cdot (1 + \frac{175 \mu \cdot s}{11})}$$

$\downarrow$   
 pole = 1894  
 $\uparrow$   
 $\therefore$  Low

$\downarrow$   
 pole  $\approx$  63K  
 $\uparrow$   
 High